

## **VHDL and FPGA Design Workshop**

**Nasser Alaraje, PhD**  
**Michigan Tech University**  
**Associate Professor, Program Chair, Electrical Engineering**  
**Technology**  
**E-mail: [alaraje@mtu.edu](mailto:alaraje@mtu.edu)**


**Aleksandr Sergeyev, PhD**  
**Michigan Tech University**  
**Assistant Professor, Electrical Engineering Technology**  
**E-mail: [avsergue@mtu.edu](mailto:avsergue@mtu.edu)**

**Fred Scheu**  
**College of Lake County**  
**Instructor, Program Chair, Electrical Engineering**  
**Technology**  
**E-mail: [fscheu@clcollinois.edu](mailto:fscheu@clcollinois.edu)**

**Carl Seidel**  
**EET Student, Senior**  
**Michigan Tech University**  
**E-mail: [csseidel@mtu.edu](mailto:csseidel@mtu.edu)**

# MichiganTech

Sponsored by  
National Science Foundation  
Advanced Technological Education  
Award No. DUE-1003389




## VHDL and FPGA Design Workshop

**Nasser Alaraje, PhD**  
Michigan Tech University  
Associate Professor, Program Chair, Electrical Engineering Technology  
E-mail: [alaraje@mtu.edu](mailto:alaraje@mtu.edu)

**Aleksandr Sergeyev, PhD**  
Michigan Tech University  
Assistant Professor, Electrical Engineering Technology  
E-mail: [avsergue@mtu.edu](mailto:avsergue@mtu.edu)

**Fred Scheu**  
College of Lake County  
Instructor, Program Chair, Electrical Engineering Technology  
E-mail: [fscheu@clcollinois.edu](mailto:fscheu@clcollinois.edu)

**Carl Seidel**  
EET Student, Senior  
Michigan Tech University  
E-mail: [csseidel@mtu.edu](mailto:csseidel@mtu.edu)



# MichiganTech

## Syllabus

<u>Day 1</u>	
• 9:00 am	Introduction
• 9:15 am	What is an FPGA
• 9:45 am	FPGA Design Techniques
• 1:00 pm	Lab 1 – Introduction to Altera's Quartus
• 2:30 pm	Introduction to VHDL
• 3:30 am	Lab 2 - Introduction to VHDL
<u>Day 2</u>	
• 9:00 am	Lab 3 - VHDL Testbench Lab
• 10:00 am	Advanced VHDL
• 11:00 am	Lab 4 – Advanced VHDL
• 1:00 pm	Final Project (using DE2)
• 3:00 pm	Support System (Software/hardware)
• 3:30 pm	Implementation / Adaption Plan / Issues at schools
• 4:00 pm	Conclusions / Feedback / Survey

# **MichiganTech**

## Introductions

- Your Name
- Your Affiliations
- Experience with VHDL and FPGA
- Your intended learning goals
- Pre-test / Pre-Survey

# **MichiganTech**

## Workshop Goals:

- Participants will:
  - Be able to identify the importance of teaching engineering technology students relevant skills in hardware modeling and FPGA design
  - Demonstrate the understanding of the fundamental concepts of hardware description languages and gain knowledge on programmable logic devices (PLD)
  - Gain hands-on expertise on the hardware and software necessary to establish a re-configurable lab at their respective institutions
  - Gain hands-on lab experience by practicing modeling basic building blocks of digital systems and learn the FPGA design flow
  - Develop potential curricular resources to be used at their respective institutions

# **MichiganTech**

## **Introduction**

- FPGA-based re-programmable logic design became more attractive as a design medium during the last decade
- only 19.5 % of 4-year and 16.5 % of 2-year electrical and computer engineering technology programs at US academic institutions currently have a curriculum component in hardware description language and programmable logic design
- Curriculum has not yet “caught up” to industry needs. industry must be driving the curriculum development.

5

# **MichiganTech**


## **Research Background**

- Respond to the Market needs of Skilled FPGA Engineers
- Historically, electrical engineering technology Associate and Baccalaureate programs have included a traditional logic design course. These topics are far from most current industry practice in logic design.
- EET two-year and four-year programs must teach digital logic using VHDL and FPGA [3] and students must be equipped with design skills that are current, relevant, and widely used in industry
- The major objectives of this curriculum shift are to give technology students at Michigan Technological and College of Lake County the opportunity to learn and experience logic design using FPGA

6

# MichiganTech

## FPGA

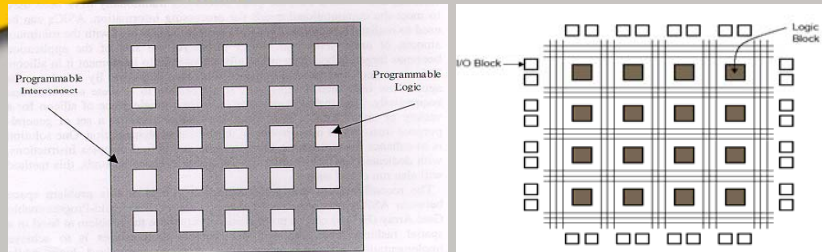

- Introduced by Xilinx in mid 1980 for implementing digital logic  
**F**ield  
**P**rogrammable  
**G**ate  
**A**rray
- FPGA Can be visualized as a set of programmable logic blocks embedded in programmable interconnect
- Interconnect architecture provides the connectivity between logic blocks
- Programming Technology determines the method of storing configuration

7

# MichiganTech

## FPGA Re-programmable Logic Applications

- When FPGA first introduced, it was considered as another form of gate array
- SRAM-FPGA in-circuit reprogrammability feature provides a more than just a standard gate array
- FPGAs have gained rapid acceptance and growth over the past decade because they can be applied to a very wide range of applications
  - random logic
  - Custom computing machine
  - device controllers
  - communication encoding and filtering
- programmable logic becomes the dominant form of digital logic design and implementation

8

# MichiganTech

## FPGA design flow

- Design Flow is the step-by-step methodology to go through the process of FPGA design
- The design flow can be divided into 6 basic steps

Design Entry  
Functional Verification and Simulation  
FPGA Synthesis  
FPGA Place & Route  
Circuit Analysis (Timing, Power ...)  
Programming FPGA devices

9

# MichiganTech

## FPGA Design Flow

Implementation Path

design entry (VHDL)

FPGA Synthesis

FPGA Place and Route

Download to FPGA

Analysis Path

FUNCTIONAL  
VERIFICATION  
& SIMULATION

CIRCUIT ANALYSIS  
(Timing)

10

# MichiganTech

## Description of Design steps

- Design Entry – describes the design that has to be implemented onto FPGA
- Functional Verification and Simulation – checks logical correctness of design
- FPGA synthesis – converts design entry into actual gates/blocks needed
- FPGA Place & Route – selects the optimal position and minimizes length of interconnections on device
- Time Analysis – determines the speed of the circuit which has been completely placed and routed
- Programming to FPGA – downloads bitstream codes onto FPGA devices


11

# MichiganTech
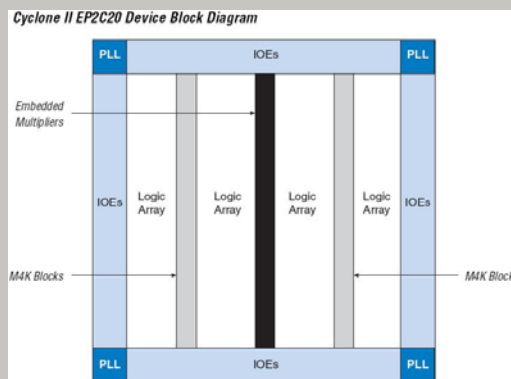
## Cyclone II FPGA Architecture

The Cyclone II FPGA has up to:

- 68,416 logic elements in the logic arrays.
- 150 18x18-bit embedded multipliers.
- 250 M4K RAM blocks
- 622 I/O element pins
- Four phased-locked loops



# MichiganTech

## What projects are FPGAs good for

- Aerospace & Defense**  
 Radiation-tolerant FPGAs along with intellectual property for image processing, waveform generation, and partial reconfiguration for SDRs.
- Automotive**  
 Automotive silicon and IP solutions for gateway and driver assistance systems, comfort, convenience, and in-vehicle infotainment.
- Broadcast**  
 Solutions enabling a vast array of broadcast chain tasks as video and audio finds its way from the studio to production and transmission and then to the consumer.
- Consumer**  
 Cost-effective solutions enabling next generation, full-featured consumer applications, such as converged handsets, digital flat panel displays, information appliances, home networking, and residential set top boxes.
- Industrial/Scientific/Medical**  
 Industry-compliant solutions addressing market-specific needs and challenges in industrial automation, motor control, and high-end medical imaging.
- Storage & Server**  
 Data processing solutions for Network Attached Storage (NAS), Storage Area Network (SAN), servers, storage appliances, and more.
- Wireless Communications**  
 RF, base band, connectivity, transport and networking solutions for wireless equipment, addressing standards such as WCDMA, HSDPA, WiMAX and others.
- Wired Communications**  
 End-to-end solutions for the Reprogrammable Networking Linecard Packet Processing, Framing/MAC, serial backplanes, and more.

# MichiganTech

## Who uses them

www.fpgajobs.com

The screenshot shows the homepage of www.fpgajobs.com, a job search portal for FPGA professionals. The page is displayed in a Windows Internet Explorer browser window. On the left, there is a sidebar with filters for job type (Design, Test/Dev, FAE, Marketing, Sales, Validation, Verification) and job type (Full-time, Part-time, Contract, Seasonal, Permanent, Temporary, Internship). The main content area is titled "Featured Job Postings from the Web" and lists several job openings with their dates, titles, companies, and locations. The jobs listed include:

- Jun 30 Principal Hardware Engineer FPGA** at Mercury Computer Systems, Chelmsford, MA. Description: Principal Hardware Engineer FPGA Location: Chelmsford, MA Last Updated: 06/...
- Jun 30 Senior Systems Engineer** at DCS, Alexandria, VA. Description: Senior Systems Engineer FPGA Location: Alexandria, VA Last Updated: 06/...
- Jun 30 Software Developer/Engineer** at ERA International, Columbia, MD. Description: Software Developer/Engineer FPGA Location: Columbia, MD Last Updated: 06/...
- Jun 29 FPGA/ASIC Development Engineer** at Carriercomm, Encinitas, CA. Description: FPGA/ASIC Development EngineerCarrierComm is seeking an FPGA/ASIC developme...
- Jun 29 FPGA/ASIC Verification Engineer** at Carriercomm, Encinitas, CA. Description: CarrierComm is seeking a FPGA/ASIC verification engineer to develop and exe ... of...
- Jun 29 Lead/Principal Electrical Engineer - Medical** at Jabal, St Petersburg, FL. Description: CarrierComm is seeking a FPGA/ASIC verification engineer to develop and exe ... of...

## **MichiganTech**

### **Why Help is Needed**

- FPGA's are horrendously complex (much more than computer software)
  - Many tools, coding systems, etc.
  - Analog (non-ideal) timing behavior
  - Many types of devices
  - Code synthesis/Place & Route are not deterministic
- In short a design frequently
  - Is theoretically correct
  - Simulates OK
  - Fails in a real part

## **MichiganTech**

### **Why are they important**

- They have the ability to revolutionize the way that prototyping is done.
- Allows companies to get to market quicker and stay in market longer.

## ***MichiganTech***

### Xilinx

- Largest manufacturer of HW
- Develop hardware and software
- Embedded PowerPC
- University Program

## ***MichiganTech***

### Altera

- Second largest manufacturer
- Develop HW and SW
- University Program

## **MichiganTech**

Which is best?

- It depends
  - Time
  - Existing resources
  - Money
  - Level of effort
  - Preference

## **MichiganTech**

### University Programs

- Major manufacturers want to provide you with the resources to be successful



Xilinx University Program



## **MichiganTech**

### AUP

- Altera University Program
- [SBROWN@altera.com](mailto:SBROWN@altera.com) (Stephen Brown)
- Very aggressive at supporting schools
- Pros
  - Good software and hardware
- Cons
  - have limited educational support material


## **MichiganTech**

### XUP

- Xilinx University Program
- [xup@xilinx.com](mailto:xup@xilinx.com)
- Only give away what they make or have significant investment in
- Pros
  - Give away hardware and software
- Cons
  - Slow and not a positive donation

# MichiganTech

## Altera DE2 Development Board

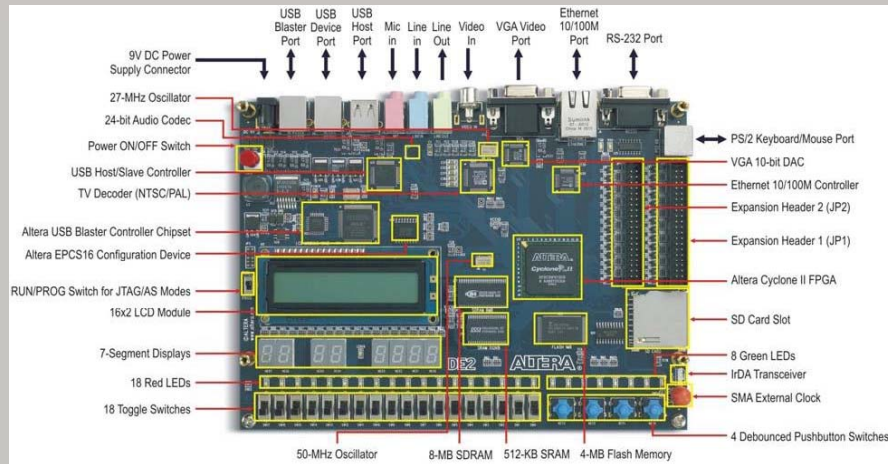

# MichiganTech

What do you really need to start?

- Quartus Software
- DE2 FPGA board

## ***MichiganTech***

Obtaining, licensing and service contract with Altera

- If you decide to go with Altera, we can help you (with currently available resources)
  - Register with AUP
  - Get software

## ***MichiganTech***

Quartus Software

- Quartus is the software used to make the project we are going to complete.
- We will cover this package more in the next slides and during the practical exercise.



## Quartus® II Software Design Series: Foundation



## Objectives

- Create a new Quartus® II project
- Choose supported design entry methods
- Compile a design into an FPGA
- Locate resulting compilation information
- Create design constraints (assignments & settings)
- Manage I/O assignments
- Perform timing analysis & obtain results





## Quartus II Design Software

- Fully-integrated development tool
  - Multiple design entry methods
  - Logic synthesis
  - Place & route
  - Timing & power analysis
  - Simulation (ModelSim-Altera Edition)
  - Device programming

31



## More Features

- MegaWizard® Plug-In Manager & SOPC Builder design tools
- TimeQuest Timing Analyzer
- Incremental compilation feature
- PowerPlay Power Analyzer
- NativeLink® 3rd-party EDA tool integration
- Debugging capabilities - From HDL to device in-system
- 32 & 64-bit Windows & Linux support
- Multi-processor support
- Node-locked & network licensing options

32

# MichiganTech

## Welcome to the Quartus II Software!

### Getting Started With Quartus® II Software



**Start Designing**  
Designing with Quartus II software requires a project

Create a New Project (New Project Wizard)

Open Existing Project

Open Recent Project:

- top
- pipemult
- pipemult
- mult8x8

**Start Learning**  
The audio/video interactive tutorial teaches you the basic features of Quartus II software

Open Interactive Tutorial

Turn on or off in Tools ⇒ Options

Literature Training Online Demos Support

Altera

33  
□ Don't show this screen again

# MichiganTech

## Quartus II Default Operating Environment



**Project Navigator**

**Tasks window**

**Tool View window**

**Messages window**

34

# MichiganTech

The screenshot shows the Quartus II software interface with several callouts pointing to specific features:

- File control**: Points to the File menu.
- Dynamic menus**: Points to the Project menu.
- Pin Planner**: Points to the Pin Planner icon in the toolbar.
- Chip Planner**: Points to the Chip Planner icon in the toolbar.
- Compilation controls**: Points to the Compilation icon in the toolbar.
- Compilation Report**: Points to the Compilation Report icon in the toolbar.
- TimeQuest timing analyzer**: Points to the TimeQuest icon in the toolbar.

**Main Toolbar**

To reset views:

1. Tools ⇒ Customize ⇒ Toolbars ⇒ Reset All
2. Restart Quartus II

35

# MichiganTech

## Tips & Tricks Advisor

The screenshot shows the Quartus II Tips & Tricks Advisor window. The left pane lists various tips, and the right pane displays the details for the selected tip, "Get an Early Timing Estimate".

**Help menu ⇒ Tips & Tricks**

**Get an Early Timing Estimate**

**Recommendation:** You can get an early timing estimate without running a full compilation.

**Description:** You can use the Start Early Timing Estimate command on the Processing menu to get a full timing report based on estimated delays for the design. This command can run the Fitter up to ten times faster than a full fit and produces estimated delays within 20% of what a full compilation can achieve.

**Action:** Use the Start Early Timing Estimate command on the Processing menu to run an early timing estimate. You can specify settings for the early timing estimate in the Settings dialog box when a project is open.

[Open Settings dialog box - Early Timing Estimate page](#)

**Provides useful instructions on using the Quartus II software & links to settings.**

**Available sections include:**

- New features in current release
- Helpful features and project settings available to designers

For Help, press F1

**MichiganTech**

Quartus II Help Version 10.0 - Mozilla Firefox

File Edit View History Bookmarks Tools Help

file:///c:/altera/10.0b/objects/ql... Google

Quartus II Help Version 10.0

Search Contents Index **Forums**

ALTEA

Welcome > Quartus II Introduction

Welcome to the Quartus II Software

The Quartus II development software provides a complete design environment for on-a-programmable-chip (SOPC) design. Regardless of whether you are using a Windows or a Linux workstation, the Quartus II software ensures easy design and programming. The following sections describe the general features of the Quartus II software.

☐ Quartus II Highlights:  
☐ Design Capabilities:  
☐ NativeLink Integration with other EDA Tools

Click any of the following flow icons for more information about the Quartus II design flow:

Design Entry Includes block-based design, system-level design & software development

Help  
 Search  
 Messages  
 Glossary  
 Megafunctions/LPM  
 Devices and Adapters  
 EDA Interfaces

Show All  
 Expand all topics

Web browser-based allows for easy search in page

**Built-In Help System**

**MichiganTech**

QUARTUS II TUTORIAL

Intro

Help menu ⇒ Getting Started Tutorial or from the Getting Started window

Select one of the following tutorial modules:


Module 1: Quartus II Introduction (5 minutes)  
 Module 2: Create a Design (30 minutes)  
 Module 3: Compile a Design (40 minutes)  
 Module 4: Run Timing Analysis (40 minutes)  
 Module 5: Run Timing Simulation (30 minutes)  
 Module 6: Configure a Device (20 minutes)  
 Module 7: Incremental Compilation (40 minutes)  
 Module 8: Sign off to II Logic Analyzer (40 minutes)

**Interactive Tutorial**

Show Me Guide Me Test Me

# MichiganTech

## Detachable Windows

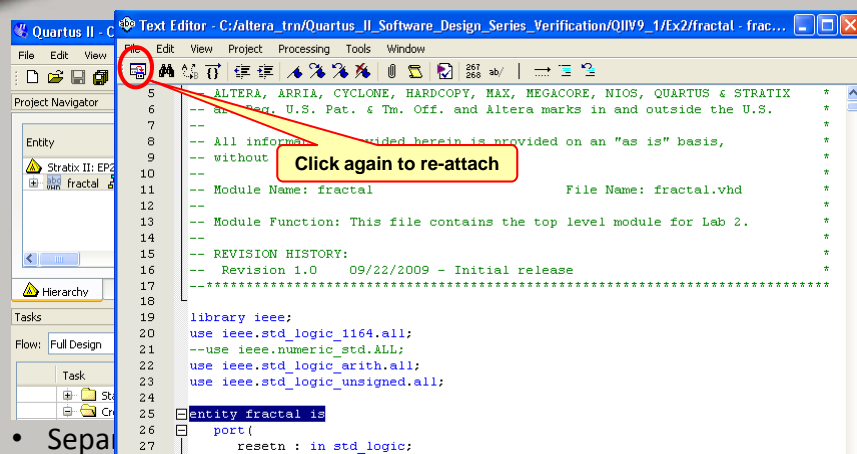


- Separable (Window menu ⇒ Detach/Attach Window)

# MichiganTech


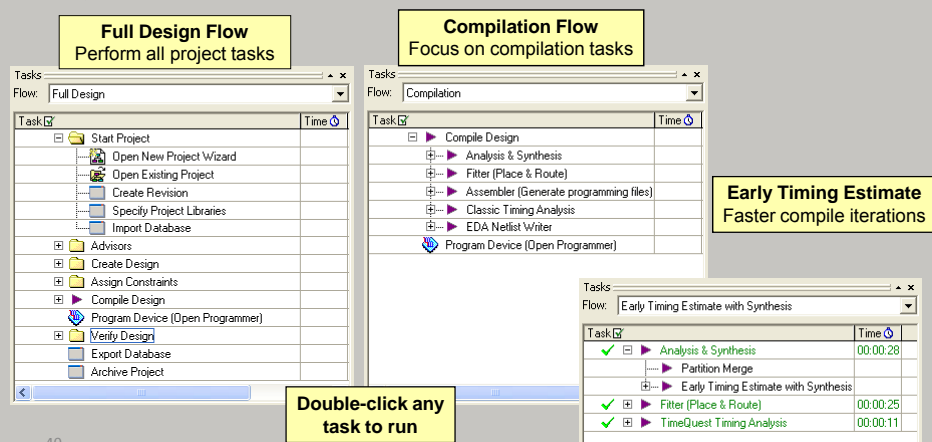
## Tasks Window

- Easy access to most Quartus II functions
- Organized into related tasks within three task flows


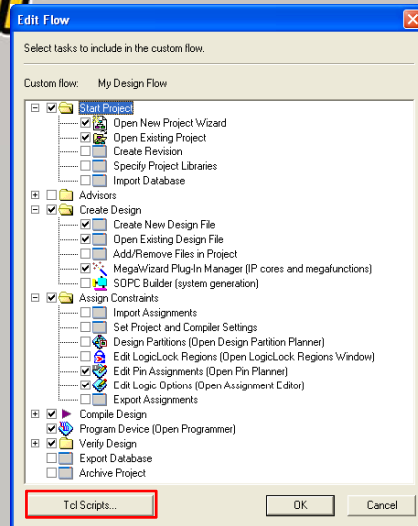 
# MichiganTech

- Customize the Tasks display
- Add Tcl scripts for quick access




## Custom Task Flow

# MichiganTech


 
## Tcl Console Window

- Enter and execute Tcl commands directly in the GUI

View menu ⇒ Utility Windows ⇒ Tcl Console



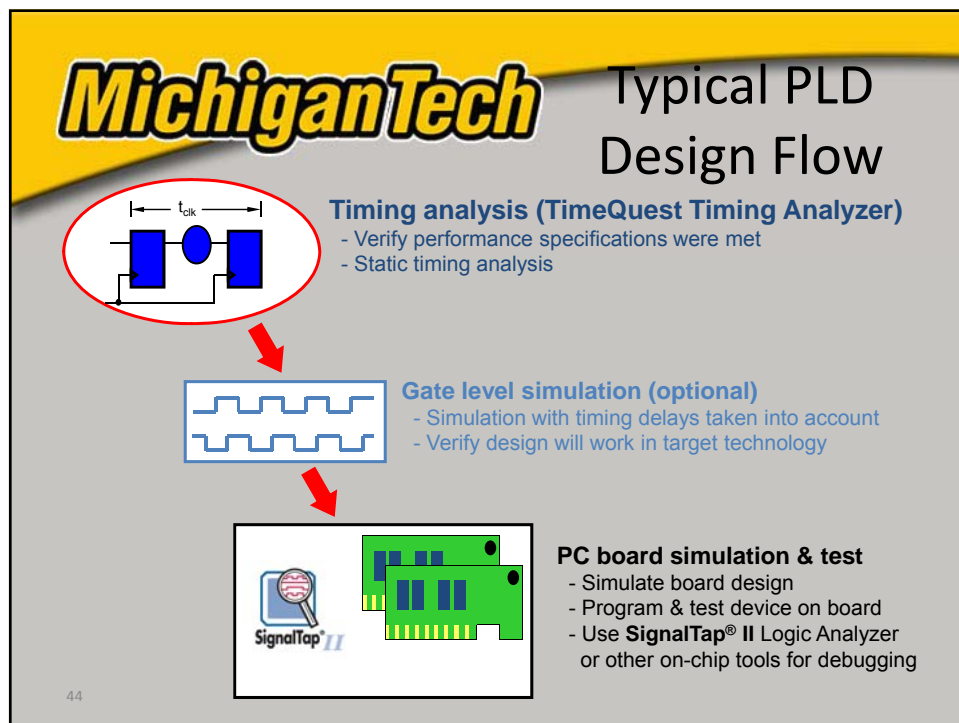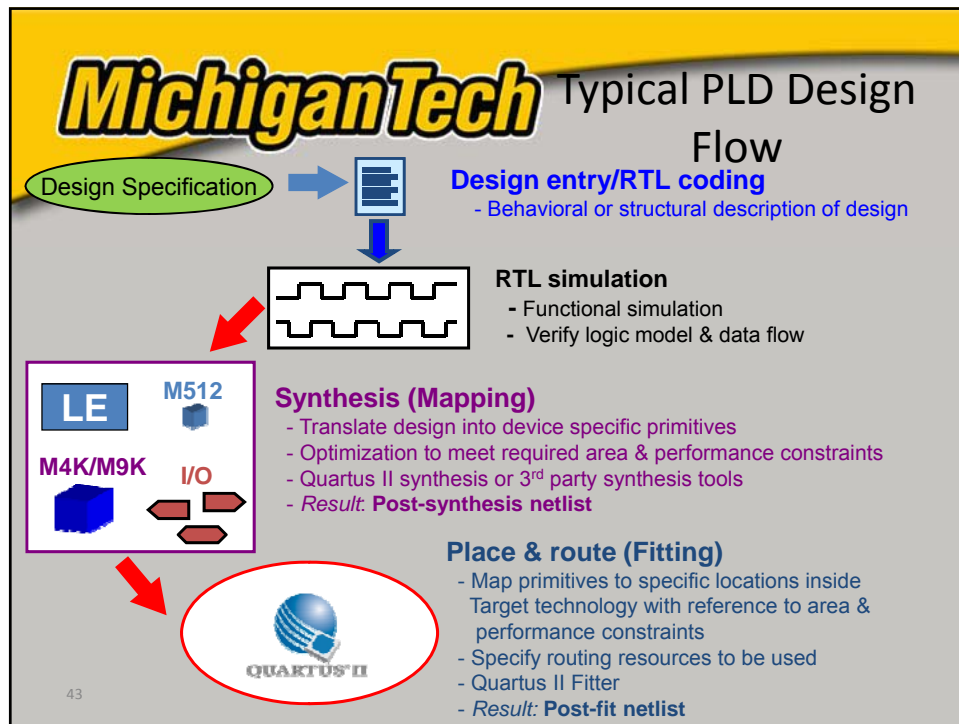- Execute from command-line using Tcl shell
  - quartus\_sh -shell
- Run complete scripts from **Tools** menu ⇒ **Tcl Scripts**



# MichiganTech

## Quartus II Projects

- Description
  - Collection of related design files & libraries
  - Must have a designated top-level entity
  - Target a single device
  - Store settings in Quartus II Settings File (.QSF)
  - Compiled netlist information stored in **db** folder in project directory
- Create new projects with New Project Wizard
  - Can be created using Tcl scripts

45

# MichiganTech

## New Project Wizard

The screenshot shows the Quartus II New Project Wizard interface. The 'File' menu is open, showing options like 'New...', 'Open...', 'New Project Wizard...', 'Open Project...', 'Convert MAX+PLUS II Project...', 'Save Project', and 'Close Project'. The 'Tasks' pane on the right lists tasks such as 'Start Project', 'Open New Project Wizard', 'Open Existing Project', 'Create Revision', 'Specify Project Libraries', and 'Import Database'. The main wizard window is titled 'New Project Wizard' and shows the 'Directory, Name, Top-Level Entity' step. It has three input fields: 'What is the working directory for this project?' (with a path), 'What is the name of this project?' (with 'pipemult'), and 'What is the name of the top-level design entity for this project?' (with 'pipemult'). Annotations with red boxes and yellow text provide additional information:

- File menu**: Points to the 'File' menu.
- Tasks**: Points to the 'Tasks' pane.
- Select working directory**: Points to the first input field.
- Name of project can be any name; recommend using top-level file name**: Points to the second input field.
- Top-level entity does not need to be the same name as top-level file name**: Points to the third input field.

At the bottom, a code block shows the Tcl command: `Tcl: project_new <project_name>`

46


# MichiganTech

## ■ Add design files

- Graphic
- VHDL
- Verilog
- SystemVerilog
- EDIF
- VQM
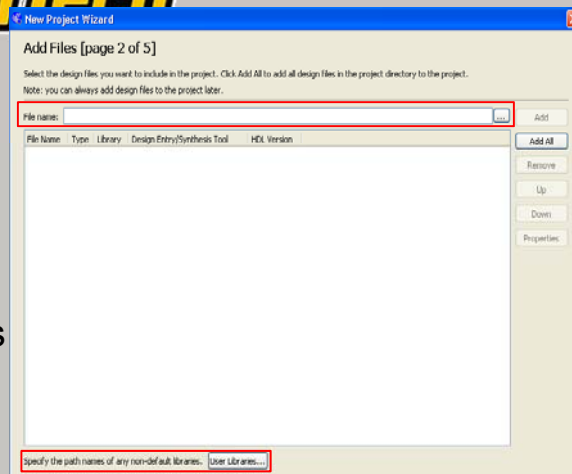
## ■ Add library paths

- User libraries
- MegaCore®/AMPPSM
- Pre-compiled VHDL packages




```
Tcl: set_global_assignment -name VHDL_FILE <filename.vhd>
Tcl: set_global_assignment -name USER_LIBRARIES <library_path_name>
```

## Add Files

# MichiganTech

## Device Selection

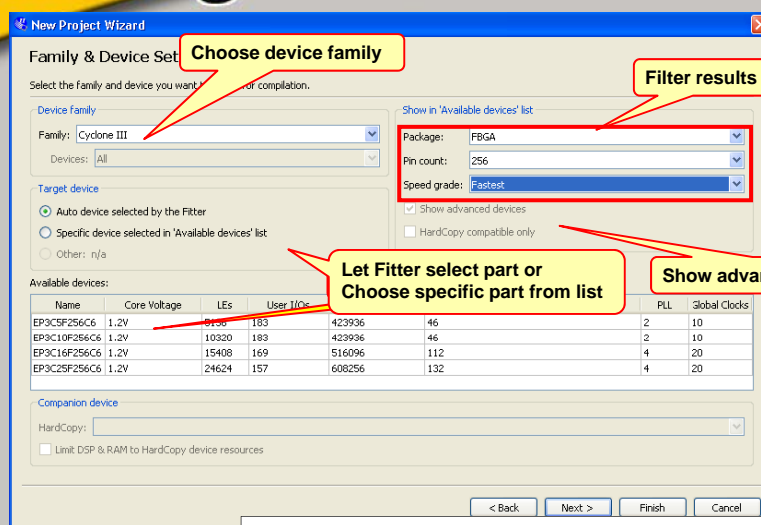

```
Tcl: set_global_assignment -name FAMILY "device family name"
Tcl: set_global_assignment -name DEVICE <part_number>
```

# MichiganTech

## EDA Tool Settings

- Choose EDA tools and file formats
- Settings can be changed or added later

Tool Type	Tool Name	Format(s)	Run Tool Automatically
Design Entry/Synthesis	Synplify Pro	EDIF	<input type="checkbox"/> Run this tool automatically to synthesize the current design
Simulation	ModelSim-Altera	VHDL	<input type="checkbox"/> Run gate-level simulation automatically after compilation
Timing Analysis	<None>	Verilog HDL	<input type="checkbox"/> Run this tool automatically after compilation
Formal Verification	<None>	SystemVerilog HDL	
Board-Level	Timing	<None>	
	Symbol	<None>	
	Signal Integrity	<None>	
	Boundary Scan	<None>	

See handbook for Tcl command format

49

# MichiganTech

Done!

When you click Finish, the project will be created with the following settings:

Project directory:	C:/altera_btm/Quartus_II_Software_Design_Series_Foundation/Q11F10_0/Ex1/Verilog
Project name:	pipemult
Top-level design entity:	pipemult
Number of files added:	1
Number of user libraries added:	0
Device assignments:	
Family name:	Cyclone III
Device:	EP3C5P256C6
EDA tools:	
Design entry/synthesis:	Synplify Pro (EDIF)
Simulation:	ModelSim-Altera (VHDL)
Timing analysis:	<None> (<None>)
Operating conditions:	
VCCINT voltage:	1.2V
Junction temperature range:	0-85 °C


Review results & click Finish

50

# MichiganTech
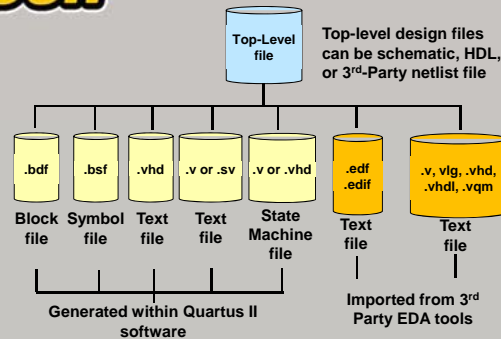
## Quartus II design entry

- Text editor
  - VHDL
  - Verilog or SystemVerilog
- Schematic editor
  - Block Diagram File
- State machine editor
  - HDL from state machine file
- Memory editor
  - HEX
  - MIF






## Design Entry Methods

- 3rd-party EDA tools
  - EDIF 2 0 0
  - Verilog Quartus Mapping (.VQM)
- Mixing & matching design files allowed

51

# MichiganTech

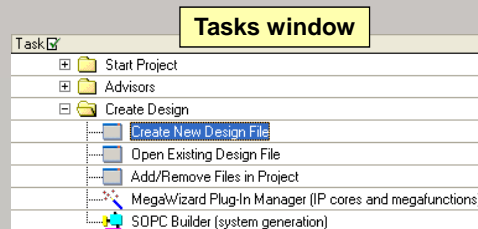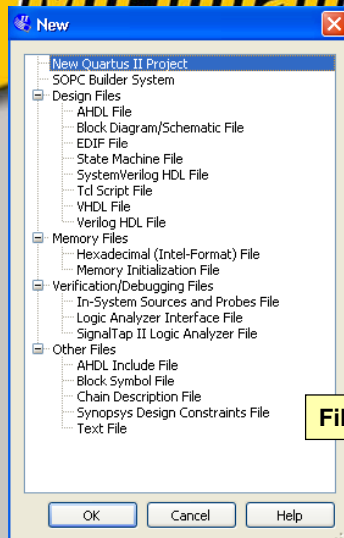

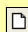File ⇒ New or  in Toolbar

## Creating New Design Files (& Others)

52

## MichiganTech Text Design Entry

- Quartus II Text Editor features
  - Block commenting
  - Line numbering in HDL text files
  - Bookmarks
  - Syntax coloring
  - Find/replace text
  - Find and highlight matching delimiters
  - Function collapse/expand
  - Create & edit .sdc files for TimeQuest timing analyzer (described later)
  - Preview/editing of full design and construct HDL templates
- Enter text description
  - VHDL (.vhd, .vhdI)
  - Verilog (.v, .vlg, .Verilog, .vh)
  - SystemVerilog (.sv)

53

## MichiganTech Verilog & VHDL

- **VHDL** - VHSIC hardware description language
  - IEEE Std 1076 (1987 & 1993) supported
  - Partial IEEE Std 1076-2008 support
  - IEEE Std 1076.3 (1997) synthesis packages supported
- **Verilog**
  - IEEE Std 1364 (1995 & 2001) & 1800 (SystemVerilog) supported
- Use Quartus II integrated synthesis to synthesize
- View supported commands in built-in help

54

# MichiganTech

## Text Editor Features

Find/highlight matching delimiters


Bookmarks (on/off/jump to)

Insert Template (Edit menu)

Collapse/expand functions


Preview window: edit before inserting & save as user template

Save User Template

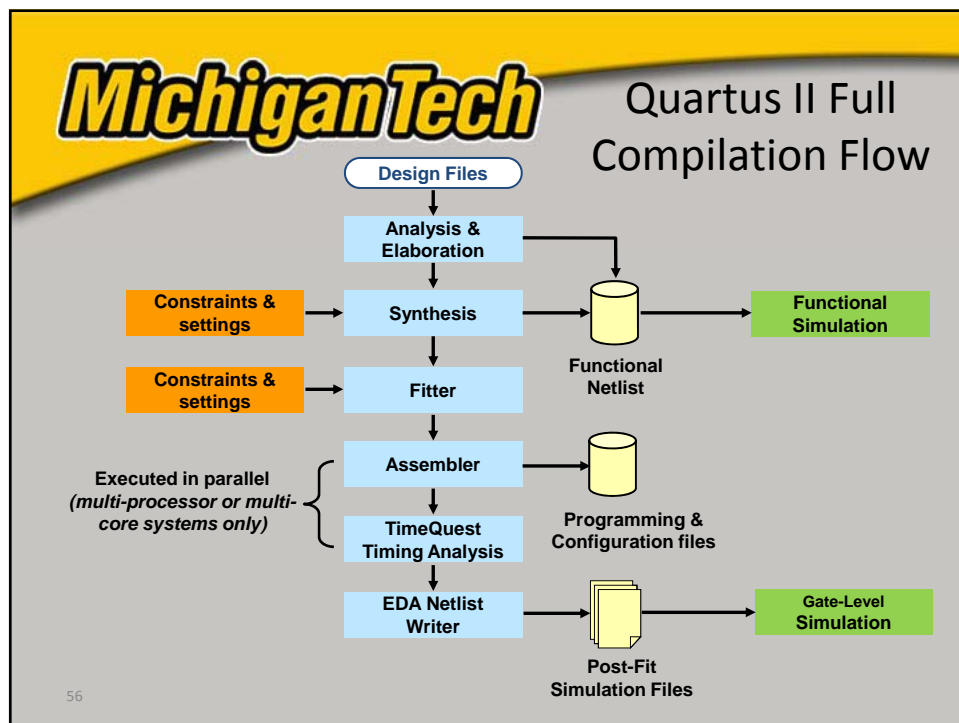
 
## MichiganTech

- Start Compilation (Full)
- Start Analysis & Elaboration
  - Checks syntax & builds hierarchy
  - Performs initial synthesis
- Start Analysis & Synthesis
  - Synthesizes & optimizes code
- Start Fitter
  - Places & routes design
  - Generates output netlists
- Start Assembler
  - Generate programming files
- Analyzers
  - I/O Assignment
  - PowerPlay
  - SSN (Switching Noise)
- Start Design Assistant



Processing Options

57

## MichiganTech

## Compilation Design Flows

- Default “flat” compilation flow
  - Design compiled as a whole
  - Global optimizations performed
- Incremental flow (on by default for new projects)
  - User assigns design partitions
  - Each partition processed separately; results merged
  - Post-synthesis or post-fit netlists for partitions are reused
  - Benefits
    - Decrease compilation time
    - Preserve compilation results and timing performance
    - Enable faster timing closure

58

# MichiganTech

**Status**

Module	Progress %	Time
Full Compilation	49 %	00:00:20
Analysis & Synthesis	100 %	00:00:09
Fitter	96 %	00:00:11
Assembler	0 %	00:00:00
TimeQuest Timing Analyzer	0 %	00:00:00

**Utility Windows**

View menu ⇒ Utility Windows

**Task List**

Task	Time
Compile Design	00:00:57
Analysis & Synthesis	00:00:35
Fitter (Place & Route)	00:00:22
Assembler (Generate programming files)	
TimeQuest Timing Analysis	
EDA Netlist Writer	
Program Device (Open Programmer)	

**Message**

Message window displays informational, warning, & error messages

Manually flag selected messages for later review

**Status & Message Windows**

# MichiganTech

## Compilation Report

**Quartus II - C:/altera\_trn/Quartus\_II\_Software\_Design\_Series\_Foundation/QIIF9\_0/Solutions/Final\_proj...**

**Flow Summary**

Window ⇒ Detach Window to release from Quartus II workspace

Each compiler executable generates separate folder

Flow Status: Successful - Thu Mar 12 19:18:54 2009

Quartus II Version: 9.0 Build 132 02/25/2009 SJ Full Version

Revision Name: pipemult\_ic

Top-level Entity Name: pipemult

Family: Cyclone III

Device: EP3C5F256C6

Timing Models: Final

Met timing requirements: N/A

Total logic elements: 101 / 5,136 ( 2 % )

Total combinational functions: 100 / 5,136 ( 2 % )

Dedicated logic registers: 30 / 5,136 ( < 1 % )

Total registers: 48

Total pins: 44 / 183 ( 24 % )

Total virtual pins: 0

Total memory bits: 512 / 423,936 ( < 1 % )

Embedded Multiplier 9-bit elements: 0 / 46 ( 0 % )

Total PLLs: 0 / 2 ( 0 % )

# MichiganTech

## Netlist Viewers

- RTL Viewer
  - Schematic of design after Analysis and Elaboration
  - Visually check initial HDL before synthesis optimizations
  - Locate synthesized nodes for assigning constraints
  - Debug verification issues
- Technology Map Viewers (Post-Mapping or Post-Fitting)
  - Graphically represents results of mapping (post-synthesis) & fitting
  - Analyze critical timing paths graphically
  - Locate nodes & node names after optimizations (cross-probing)

61

# MichiganTech

## RTL Viewer

Tools menu => Netlist Viewers or Tasks window "Compile Design" tasks

Find in hierarchy

Schematic view


Hierarchy list

Note: Must perform elaboration first (e.g. Analysis & Elaboration OR Analysis & Synthesis)

62
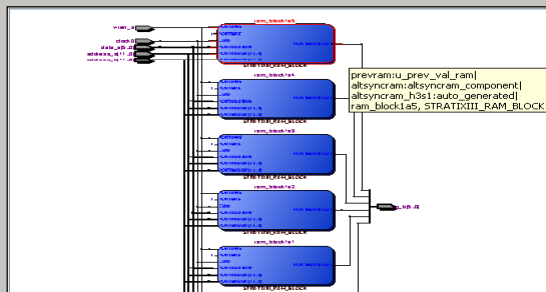
## MichiganTech Schematic View (RTL Viewer)

- Represents design using logic blocks & nets
  - I/O pins
  - Registers
  - Muxes
  - Gates (AND, OR, etc.)
  - Operators (adders, multipliers, etc.)



Place pointer over any element in schematic to see details

- Name
- Internal resource count

63

## MichiganTech Compilation Summary



- Compilation includes synthesis & fitting
- Compilation Report contains detailed information on compilation results
- Use Quartus II software tools to understand how design was processed
  - RTL Viewer
  - Technology Map Viewers
  - State Machine Viewer
  - Chip Planner
  - Resource Property Editors

64

# MichiganTech
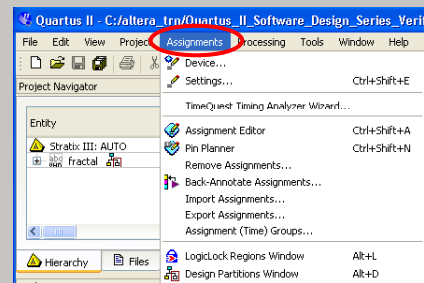 
## Synthesis & Fitting Control

- Controlled using two methods
  - Settings - Project-wide switches
  - Assignments - Individual entity/node controls
- Both accessed in **Assignments** menu or Tasks window
- Stored in QSF file for project/revision



65

# MichiganTech


## Settings

- Project-wide switches that affect entire design
- Examples
  - Device selection
  - Synthesis optimization
  - Fitter settings
  - Physical synthesis
  - Design Assistant
- Located in Settings dialog box
  - Assignments** menu
  - Set Project and Compiler Settings** task in Tasks window

66

# MichiganTech


## Device Settings Dialog Box

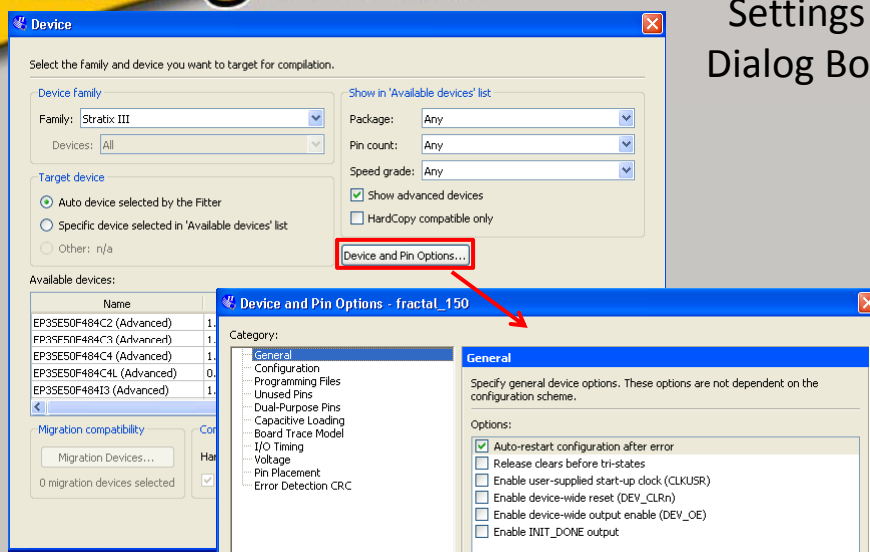

# MichiganTech

- Change settings**
- Top-level entity
  - Add/remove files
  - Libraries
  - Compiler settings
  - EDA tool settings
  - Synthesis settings
  - Fitter settings
  - Timing Analysis settings
  - Power analysis settings
  - SSN Analyzer settings

## Settings Dialog Box

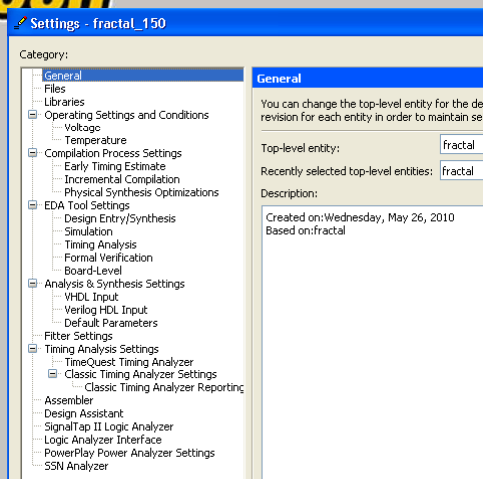

```
Tcl: set_global_assignment -name <assignment_name*> <value>
```

# MichiganTech

## Compilation Process Setting Examples

Category:

- General
- Files
- Libraries
- Operating Settings and Conditions
  - Voltage
  - Temperature
- Compilation Process Settings**
  - Early Timing Estimate
  - Incremental Compilation
  - Physical Synthesis Optimizations
- EDA Tool Settings
  - Design Entry/Synthesis
    - Simulation
    - Timing Analysis
    - Formal Verification
  - Analysis & Synthesis Settings
    - VHDL Input
    - Verilog HDL Input
    - Default Parameters
  - Filter Setup
  - Timing Analysis Settings
    - TimeQuest Timing Analyzer
    - Classic Timing Analyzer Settings
    - Classic Timing Analyzer Reporting
- Assembler
  - Design Assistant
  - SignalTap II Logic Analyzer
  - Logic Analyzer Interface
  - PowerPlay Power Analyzer Settings
  - SSN Analyzer

**Compilation Process Settings**

Specify Compilation Process options.

Parallel compilation

- ☐ Use global parallel compilation setting
- ☐ Use all available processors
- ☒ Maximum processors allowed:

☒ Use smart compilation

☒ Run Assembler during compilation

☐ Run RTL Viewer preprocessing during compilation

☐ Save a node-level netlist of the entire design (This option specifies VQM File name for full compilation and start VQM writer command)

File name:

☒ Export version-compatible database

Export directory:

☐ Save project output files in specified directory

Directory name:

More Settings...

69

Tcl: set\_global\_assignment -name SMART\_RECOMPILE ON

# MichiganTech

## Physical Synthesis

- Optimize during synthesis or re-synthesize based on Fitter output
  - Makes incremental changes that improve results for a given placement
  - Compensates for routing delays from Fitter
  - Apply globally (Settings) or only to specific design entities (Assignment Editor)

Category:

- General
- Files
- Libraries
- Operating Settings and Conditions
  - Voltage
  - Temperature
- Compilation Process Settings**
  - Early Timing Estimate
  - Incremental Compilation
  - Physical Synthesis Optimizations
- EDA Tool Settings
  - Design Entry/Synthesis
    - Simulation
    - Timing Analysis
    - Formal Verification
  - Analysis & Synthesis Settings
    - VHDL Input
    - Verilog HDL Input
    - Default Parameters
  - Filter Setup
  - Timing Analysis Settings
    - TimeQuest Timing Analyzer
    - Classic Timing Analyzer Settings
    - Classic Timing Analyzer Reporting
- Assembler
  - Design Assistant
  - SignalTap II Logic Analyzer
  - Logic Analyzer Interface
  - PowerPlay Power Analyzer Settings
  - SSN Analyzer

**Physical Synthesis Optimizations**

Specify options for performing physical synthesis optimizations during synthesis and fitting. These options can affect VQM or EEP results even if VQSMTS/physical synthesis is disabled.

Optimize for performance (physical synthesis)

- ☒ Perform physical synthesis for combinational logic
- ☒ Perform register retiming

Effort level

- ☐ Fast (optimize during synthesis, minor compilation time increase)
- ☒ Normal (optimize during synthesis and fitting, moderate compilation time increase)
- ☐ Extra (optimize during synthesis and fitting, major compilation time increase)

Other useful optimizations

- ☒ Perform automatic asynchronous signal upkilling
- ☒ Perform negative duplication

Optimize for fitting (physical synthesis for details)

- ☒ Perform physical synthesis for combinational logic
- ☐ Perform logic to memory mapping

# MichiganTech

## Fitter Settings – Fitter Effort

- **Standard Fit**
  - Highest effort
  - Longest compile time
- **Fast Fit**
  - Faster compile
  - Possibly lesser performance
- **Auto Fit**
  - Compile stops after meeting timing
  - Conserves CPU time
  - Will mimic standard fit for hard-to-fit designs
  - Default for new designs
- **One fitting attempt**

71

```
Tcl: set_global_assignment -name FITTER_EFFORT "<Effort Level>"
```

# MichiganTech

## I/O Planning Need

- I/O standards increasing in complexity
- FPGA/CPLD I/O structure increasing in complexity
  - Results in increased pin placement guidelines
- PCB development performed simultaneously with FPGA design
- Pin assignments need to be verified earlier in design cycle
- Designers need easy way to transfer pin assignments into board tools

72

# MichiganTech

## Creating I/O-Related Assignments

- Pin Planner
- Import from spreadsheet in CSV format
- Type directly into QSF file
- Scripting
- Using synthesis attributes in HDL

*Note: Other methods/tools are available in the Quartus II software to make I/O assignments. The above are the most common or recommended.*

73

# MichiganTech

## Pin Planner

- Interactive graphical tool for assigning pins
  - Drag & drop pin assignments
  - Set pin I/O standards
  - Reserve future I/O locations
- Three main sections
  - Package View
  - All Pins list
  - Groups list

Assignments menu ⇒  
Pin Planner or  
“Assign Constraints”  
folder in Tasks window

74

# MichiganTech

## Pin Planner Window (1)

The screenshot shows the Pin Planner Window for a Cyclone III - EP3C5F256C device. The window is divided into several sections:

- Toolbar:** A vertical toolbar on the left side of the window.
- Groups list:** A table listing design groups and their locations.
 

Node Name	Direction	Location
data[7..0]	Input Group	
data[7..0]	Input Group	
data[15..0]	Output Group	
rdaddress[4..0]	Input Group	
rdaddress[4..0]	Input Group	
< new group >		
- Package View (Top or Bottom):** A graphical representation of the chip package pins, showing a grid of pins with their locations and directions.
- All Pins list:** A table listing all I/O pins and their properties.
 

Node Name	Direction	Location	I/O Standard	Reserved	Pin Capacitance
data[7..0]	Input		2.5 V (default)		
data[7..0]	Input		2.5 V (default)		
data[15..0]	Output		2.5 V (default)		
data[15..0]	Output		2.5 V (default)		
data[15..0]	Output		2.5 V (default)		
data[15..0]	Output		2.5 V (default)		
data[15..0]	Output		2.5 V (default)		

75

# MichiganTech

## Pin Planner Window (2)

- Package View
  - Displays graphical representation of chip package
  - Use to make or edit design I/O assignments
  - Use to locate other package pins (power & configuration pins)
- All Pins list
  - Displays I/O pins (signals) in design as indicated by filter
  - Use to edit pin settings/properties directly
- Groups list
  - Similar to All Pins list except displays only groups & buses
  - Use to make bus and group assignments
  - Use to create new user-defined groups

76

## MichiganTech

### Assigning Pin Locations Using Pin Planner

**Drag & drop single pin; tooltips provide pin information**

**Drag & drop multiple highlighted pins or buses**

**Choose one-by-one or pin alignment direction (Pin Planner toolbar or Edit menu)**

Node Name	Direction	Location
1	clk	Input
2	clk2	Input
3	d[7]	Input
4	d[6]	Input
5	d[5]	Input
6	d[4]	Input
7	d[3]	Input
8	d[2]	Input

## MichiganTech

### Assigning Pin Locations Using Pin Planner (2)

**Double-click pin or I/O bank to open Properties dialog box**

**Drag & drop to I/O bank, VREF block, or device edge**

**Filter nodes displayed**

**Pin Properties**

Pin number: PIN\_B16  
 Node name: d[4]  
 I/O standard: 3.3V LVTTTL (default)  
 Reserved:  
 Properties:

Name	Value
I/O Bank	3
General Function	Column I/O
Special Function	DQSn11T
Pad ID	345
VREF Pad ID	N/A

Node Name	Direction	Location	I/O Bank
7	Input	PIN_B19	3
5	Input	PIN_B18	3
6	Input	PIN_B17	3
4	Input	PIN_B16	3
3	Input	IOBANK_3	3
2	Input	IOBANK_3	3
1	Input	IOBANK_3	3
0	Input	IOBANK_3	3

# MichiganTech

## Assigning Pin Locations Using Pin Planner (3)

- Select available locations from list of pins color-coded by I/O bank

Named:  Edit: ☐ ☐ Filter: Pins: all

	Node Name	Direction	Location	I/O Bank	Vref Group	I/O Standard
10	ym_out[6]	Output				3.3-V LVTTTL (default)
11	ym_out[5]	Output				
12	ym_out[4]	Output	PIN_AA17	I/O Bank 8	Column I/O	DQS13B/DQ2B
13	ym_out[3]	Output	PIN_AA18	I/O Bank 8	Column I/O	DQ5n13B
14	ym_out[2]	Output	PIN_AB5	I/O Bank 7	Column I/O	DQ7B
15	ym_out[1]	Output	PIN_AB6	I/O Bank 7	Column I/O	DQ7B
16	ym_out[0]	Output	PIN_AB7	I/O Bank 7	Column I/O	DQ9B
17	<<new node>>		PIN_AB8	I/O Bank 7	Column I/O	DQ9B
			PIN_AB10	I/O Bank 10	Column I/O	PLL6_OUT0p
			PIN_AB13	I/O Bank 8	Column I/O	CLK4p

79

# MichiganTech


## Show Fitter Placements

- View I/O locations automatically selected by Fitter

View ⇒ Show  
or in Toolbar



 
Top View - Wire Bond  
Cyclone II - EP2C5F256C6




80

# MichiganTech

## Back-Annotation

 

Assignments menu

 

Green/brown pattern indicates back-annotation


# MichiganTech

## Verifying I/O Assignments

- I/O Assignment Analysis
  - Checks legality of all I/O assignments without full compilation
- Minimal requirements for running
  - I/O declaration
    - HDL port declaration
    - Reserved pin
  - Pin-related assignments
    - I/O standard
    - Current strength
    - Pin location (pin, bank, edge)
    - PCI clamping diode
    - Toggle rate

Processing menu ⇒ Start ⇒ Start I/O Assignment Analysis or Tasks window

Run from Pin Planner toolbar



# MichiganTech

## I/O Rules Checked

- No internal logic
  - Checks I/O locations & constraints with respect to other I/O & I/O banks
  - Each I/O bank supports a single  $V_{CCIO}$
- I/O connected to logic
  - Checks I/O locations & constraints with respect to other I/O, I/O banks, & internal resources
  - PLL must be driven by a dedicated clock input pin

Note: When working with design files, synthesize design before running I/O Assignment Analysis

83

# MichiganTech

## I/O Assignment Analysis Output

**Compilation Report (Fitter section)**

- Pin-out file
- I/O pin tables
- Output pin loading
- I/O rules checking\*

**Messages on I/O assignment issues**

- Compiler assumptions
- Device & pin migration issues
- I/O bank voltages & standards

84

\*Note: See Appendix for special reports and information generated only for Stratix II, Cyclone III, and newer devices

# **MichiganTech**

*Please go to Lab1 – Introduction to  
Altera's Quartus in the  
Manual*

85

# **MichiganTech**

## Introduction to VHDL

- Implement basic constructs of VHDL
- Implement modeling structures of VHDL

86

# MichiganTech

**V**HSIC (Very High Speed Integrated Circuit)

**H**ardware

**D**escription

**L**anguage

**VHDL**

87

# MichiganTech

## What is VHDL?

- IEEE industry standard hardware description language
- High-level description language for both simulation & synthesis
  - Facilitates portability and productivity as design logic and verification stimulus are both vendor and tool independent

88

## MichiganTech

### Terminology

- HDL – A hardware description language is a software programming language that is used to model a piece of hardware
- Behavioral modeling - A component is described by its input/output response
- Structural modeling - A component is described by interconnecting lower-level components/ primitives

89

## MichiganTech

### Terminology (cont.)

- Register Transfer Level (RTL) - A type of behavioral modeling, for the purpose of synthesis
  - Hardware is implied or inferred
  - Synthesizable
- Synthesis - Translating HDL to a circuit and then optimizing the represented circuit
- Process – Basic unit of execution in VHDL
  - Process executions are converted to equivalent hardware

# MichiganTech

## Digital Systems and HDLs

- Typical digital components per IC
  - 1960s/1970s: 10-1,000
  - 1980s: 1,000-100,000
  - 1990s: Millions
  - 2000s: Billions
- 1970s
  - IC behavior documented using combination of schematics, diagrams, and natural language (e.g., English)
- 1980s
  - Documentation was hundreds of pages for large ICs
    - Imprecise
  - Need for better documentation

Transistors per IC (millions)

1997 2000 2003 2006 2009 2012 2015 2018

Inputs: b; Outputs: x

diagrams

schematics

natural language

"The system has four states. When in state Off, the system outputs 0 and stays in state Off until the input becomes 1. In that case, the system enters state On1, followed by On2, and then On3, in which the system outputs 1. The system then returns to state Off."

91

# MichiganTech

## HDLs for Simulation

- Hardware description languages (HDLs) – Machine-readable textual languages for describing hardware
  - Schematic + documentation in one
  - HDL description became the precise, concise IC documentation
  - Simulator** is a tool that automatically generates outputs values of a hardware module for a given sequence of input values.
  - VHDL originally defined for *simulation* of ICs
    - First, IC was designed
    - Then, IC was described in HDL for documentation

```

...
CombLogic: PROCESS (Currstate, b)
BEGIN
  CASE Currstate IS
    WHEN S_Off =>
      x <= '0';
      IF (b = '0') THEN
        Nextstate <= S_Off;
      ELSE
        Nextstate <= S_On1;
      END IF;
    WHEN S_On1 =>
      x <= '1';
      Nextstate <= S_On2;
    WHEN S_On2 =>
      x <= '1';
      Nextstate <= S_On3;
    WHEN S_On3 =>
      x <= '1';
      Nextstate <= S_Off;
  END CASE;
END PROCESS;
...

```

Simulation

Clk\_s

Rst\_s

b\_s

x\_s

10 20 30 40 50 60 70 80 90 100 10

92

## MichiganTech

### VHDL

- **VHDL: VHSIC Hardware Description Language**
  - VHSIC: Very High Speed Integrated Circuit
    - Project of the U.S. Dept. of Defense
  - VHDL defined in 1980s
  - Syntax: like Ada software programming language
    - Ada also a U.S. DoD creation
  - IEEE adopted VHDL standard ("1076") in 1987
- Other HDLs
  - Verilog: Defined in 1980s / C-like syntax / IEEE standard ("1364") in 1995
    - VHDL & Verilog very similar in capabilities, differ mostly in syntax
  - SystemC: Defined in 2000s by several companies / C++ libraries and macro routines / IEEE standard ("1666") in 2005
    - Excels for system-level; cumbersome for logic level

```

ARCHITECTURE Beh OF DoorOpener IS
BEGIN
  PROCESS(c, h, p)
  BEGIN
    f <= NOT(c) AND (h OR p);
  END PROCESS;
END Beh;

```

```

module DoorOpener(c,h,p,f);
input c, h, p;
output f;
reg f;

always @(c or h or p)
begin
  f <= (~c) & (h | p);
end
endmodule

```

```

#include "systemc.h"
SC_MODULE(DoorOpener)
{
  sc_in<sc_logic> c, h, p;
  sc_out<sc_logic> f;
  SC_CTOR(DoorOpener)
  {
    SC_METHOD(comblogic);
    sensitive << c << h << p;
  }
  void comblogic()
  {
    f.write((~c.read()) & (h.read() |
    p.read()));
  }
};

```

93

## MichiganTech

### VHDL Versions

Version	Comments
VHDL 1987	Initial version accepted by IEEE
VHDL 1993	First major update to language; Increased flexibility and added "missing" constructs & operations
VHDL 2000	Minor update to language
VHDL 2002	Minor update to language
VHDL-2008*	Second major update to language; Check tool for support

\* Course will cover constructs supported by the Quartus II software version 9.1.

94

# MichiganTech

## HDLs for Design and Synthesis

- HDLs became increasingly used for *designing* ICs using **top-down design process**
  - Design: Converting a higher-level description into a lower-level one
  - Describe circuit in HDL, simulate
    - Physical design tools automatically convert to low-level IC design
  - Describe behavior in HDL, simulate
    - e.g., Describe addition as  $A = B + C$ , rather than as circuit of hundreds of logic gates
      - Compact description, designers get function right first
    - Design circuit
      - Manually, or
      - Using **synthesis tools**, which automatically convert HDL behavior to HDL circuit
      - Simulate circuit, should match

95

# MichiganTech

## HDLs for Synthesis


- Use of HDLs for synthesis is growing
  - Circuits are more complex
  - Synthesis tools are maturing
- But HDLs originally defined for simulation
  - General language
  - Many constructs not suitable for synthesis
    - e.g., "wait" statements, pointers, recursive function calls
  - Behavior description may simulate, but not synthesize, or may synthesize to incorrect or inefficient circuit
- Not necessarily synthesis tool's fault!

96

# MichiganTech
 
## HDLs for Synthesis


- HDL language
  - General and complex; many uses
  - But use for *synthesizing circuits* is greatly restricted
    - Synthesis tool understands: *sensitivity lists, if statements, ...*
    - Synthesis tool may not understand: *wait statements, while loops, ...*, even if the HDL simulates correctly
      - If the circuit is bad, don't blame the synthesis tool!
  - We will emphasize use of VHDL for design and synthesis



97
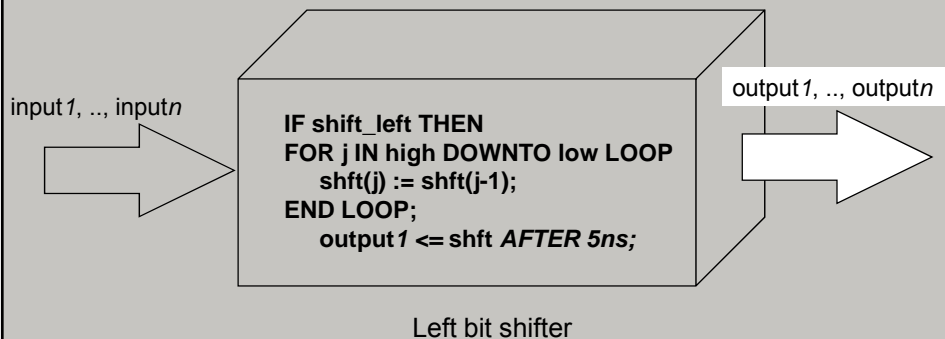
# MichiganTech

- Only the functionality of the circuit, no structure
- No specific hardware intent




## Behavioral Modeling

98
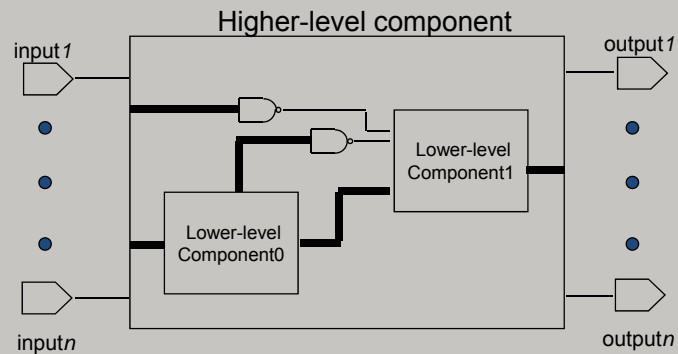
# MichiganTech

- Functionality and structure of the circuit
- Call out the specific hardware



## Structural Modeling

99

# MichiganTech

## VHDL Basics

- Two sets of constructs:
  - Simulation
  - Synthesis & simulation
- The VHDL language is made up of reserved keywords
- The language is, for the most part, **not** CASE sensitive
- VHDL statements are terminated with a ;
- VHDL is white space insensitive
- Comment support
  - -- : End of line (EOL) comment; everything from symbol to EOL is commented
  - /\* \*/ : Delimited comment; everything between symbols is commented
    - Supported in VHDL-2008 only

100

# MichiganTech VHDL Design Units

- **ENTITY**
  - used to define external view of a model. i.e. symbol
- **ARCHITECTURE**
  - used to define the function of the model. i.e. schematic
- **PACKAGE**
  - Collection of information that can be referenced by VHDL models. i.e. **LIBRARY**
  - Consists of two parts: **PACKAGE** declaration and **PACKAGE** body

101

# MichiganTech ENTITY Declaration

```
ENTITY <entity_name> IS
    Port Declarations
END ENTITY <entity_name> ; (1076-1993 version)
```

- Analogy : symbol
  - <entity\_name> can be any alpha/numerical name
- Port declarations
  - Used to describe the inputs and outputs i.e. pins
- Generic declarations
  - Used to pass information into a model
- Close entity in one of 3 ways
  - **END ENTITY** <entity\_name>; -- VHDL '93 and later
  - **END ENTITY**; -- VHDL '93 and later
  - **END**; -- All VHDL versions

102



## ENTITY : Port Declarations

```

ENTITY <entity_name> IS

  PORT (
    SIGNAL clk      : IN  bit;
    --Note: SIGNAL is assumed and is not required
    q             : OUT bit
  );
END ENTITY <entity_name> ;

```

- Structure : <class> object\_name : <mode> <type> ;
  - <class> : what can be done to an object
  - object\_name : identifier (name) used to refer to object
  - <mode> : directional
    - » **IN** (input)                      **OUT** (output)
    - » **INOUT** (bidirectional)    **BUFFER** (output w/ internal feedback)
  - <Type> : what can be contained in the object (discussed later)

103



## ARCHITECTURE

- Analogy : schematic
  - Describes the functionality and timing of a model
- Must be associated with an **ENTITY**
- **ENTITY** can have multiple architectures
- **ARCHITECTURE** statements execute concurrently (processes)
- **ARCHITECTURE** styles
  - Behavioral : how designs operate
    - RTL : designs are described in terms of registers
    - Functional : no timing
  - Structural : netlist
    - Gate/component level
  - Hybrid : mixture of the two styles
- End architecture with
  - **END ARCHITECTURE** <architecture\_name>; -- VHDL '93 & later
  - **END ARCHITECTURE**; -- VHDL '93 & later
  - **END**; -- All VHDL versions

104

## MichiganTech ARCHITECTURE

**ARCHITECTURE** <identifier> **OF** <entity\_identifier> **IS**

--ARCHITECTURE declaration section (list does not include all)

**SIGNAL** temp : INTEGER := 1; -- signal declarations with optional default values

**CONSTANT** load : boolean := true; --constant declarations

--Type declarations (discussed later)

--Component declarations (discussed later)

--Subprogram declarations (discussed later)

--Subprogram body (discussed later)

--Subtype declarations

--Attribute declarations

--Attribute specifications

**BEGIN**

PROCESS statements

Concurrent procedural calls

Concurrent signal assignment

Component instantiation statements

Generate statements

**END ARCHITECTURE** <architecture\_identifier>;

105

## MichiganTech VHDL - Basic Modeling Structure

**ENTITY** *entity\_name* **IS**

port declarations

**END ENTITY** *entity\_name*;

**ARCHITECTURE** *arch\_name* **OF** *entity\_name* **IS**

internal signal declarations

enumerated data type declarations

component declarations

**BEGIN**

signal assignment statements

PROCESS statements

component instantiations

**END ARCHITECTURE** *arch\_name*;

# MichiganTech


## Putting It All Together

```

ENTITY cmpl_sig IS
  PORT (
    a, b, sel  : IN  BIT;
    x, y, z    : OUT BIT
  );
END ENTITY cmpl_sig;

ARCHITECTURE logic OF cmpl_sig IS
BEGIN
  -- simple signal assignment
  x <= (a AND NOT sel) OR (b AND sel);
  -- conditional signal assignment
  y <= a WHEN sel='0' ELSE
    b;
  -- selected signal assignment
  WITH sel SELECT
    z <= a WHEN '0',
          b WHEN '1',
          '0' WHEN OTHERS;
END ARCHITECTURE logic;

```

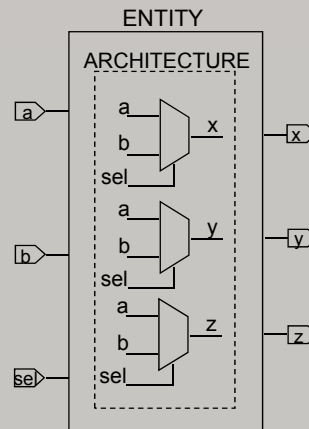

107

# MichiganTech

## Libraries

- A **LIBRARY** is a directory that contains a package or a collection of packages
- Two types of libraries
  - Working library
    - Current project directory
  - Resource libraries
    - **STANDARD** package
    - **IEEE** developed packages
    - Altera component packages
    - Any **LIBRARY** of design units that is referenced in a design

108

# MichiganTech

## Example

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY cmpl_sig IS
PORT ( a, b, sel : IN  STD_LOGIC;
        x, y, z : OUT STD_LOGIC);
END ENTITY cmpl_sig;

ARCHITECTURE logic OF cmpl_sig IS
BEGIN
    -- Simple signal assignment
    X <= (a AND NOT sel) OR (b AND sel);
    -- Conditional signal assignment
    Y <= a WHEN sel='0' ELSE
        B;
    -- Selected signal assignment
    WITH sel SELECT
        Z <= a WHEN '0',
            B WHEN '1',
            '0' WHEN OTHERS;
END ARCHITECTURE logic;
  
```

- **LIBRARY** <name>, <name> ;
  - Name is symbolic and defined by compiler tool
  - ⇒ Note: Remember that WORK and STD do not need to be defined.
- **USE** lib\_name.pack\_name.object;
  - ALL is a reserved word for object name
- Placing the library/use clause first will allow all following design units to access it

109

# MichiganTech

## Types Defined in STANDARD Package

- Type **BIT**
  - 2 logic value system ('0', '1')
  - SIGNAL** a\_temp : **BIT**;
  - Bit\_vector array of bits
  - SIGNAL** temp : **BIT\_VECTOR** (3 **DOWNTO** 0);
  - SIGNAL** temp : **BIT\_VECTOR** (0 **TO** 3);
- Type **BOOLEAN**
  - (False, true)
- Type **INTEGER**
  - Positive and negative values in decimal
  - SIGNAL** int\_tmp : **INTEGER**; -- 32-bit number
  - SIGNAL** int\_tmp1 : **INTEGER RANGE** 0 **TO** 255; --8 bit number

110

# MichiganTech

## Other Types Defined in Standard Package

- Type **NATURAL**
  - Integer with range 0 to  $2^{32}$
- Type **POSITIVE**
  - Integer with range 1 to  $2^{32}$
- Type **CHARACTER**
  - ASCII characters
- Type **STRING**
  - Array of characters
- Type **TIME**
  - Value includes units of time (e.g. ps, us, ns, ms, sec, min, hr)
- Type **REAL**
  - Double-precision floating point numbers

# MichiganTech

## Libraries (cont.)

- **LIBRARY IEEE**
  - Contains the following packages
    - **STD\_LOGIC\_1164** (STD\_LOGIC types & related functions)
    - **NUMERIC\_STD** (unsigned arithmetic functions using standard logic vectors defined as SIGNED and UNSIGNED data type)
    - **STD\_LOGIC\_ARITH\*** (arithmetic functions using standard logic vectors as SIGNED or UNSIGNED)
    - **STD\_LOGIC\_SIGNED\*** (signed arithmetic functions directly using standard logic vectors)
    - **STD\_LOGIC\_UNSIGNED\*** (unsigned arithmetic functions directly using standard logic vectors)
    - **STD\_LOGIC\_TEXTIO\*** (file operations using std\_logic)

*\* Packages actually developed by Synopsys but accepted and supported as standard VHDL by most synthesis and simulation tools*

# MichiganTech

Types Defined in  
STD\_LOGIC\_1164  
Package

- Type **STD\_LOGIC**


- 9 logic value system ('U', 'X', '0', '1', 'Z', 'W', 'L', 'H', '-')
  - '1': Logic high
  - '0': Logic low
  - 'X': Unknown
  - 'Z': (not 'z') Tri-state
  - '-': Don't Care
  - 'U': Undefined
  - 'H': Weak logic high
  - 'L': Weak logic low
  - 'W': Weak unknown
- Resolved type: supports signals with multiple drivers
  - Driving multiple values onto same signal results in known value

- Type **STD\_ULOGIC**


- Same 9 value system as STD\_LOGIC
- Unresolved type: Does not support multiple signal drivers
  - Driving multiple values onto same signal results in error

# MichiganTech

## AND/OR/NOT Gates Entities and Ports

 
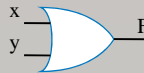
```
ENTITY And2 IS
  PORT (x: IN std_logic;
        y: IN std_logic;
        F: OUT std_logic);
END And2;
```




```
ENTITY Or2 IS
  PORT (x: IN std_logic;
        y: IN std_logic;
        F: OUT std_logic);
END Or2;
```




```
ENTITY Inv IS
  PORT (x: IN std_logic;
        F: OUT std_logic);
END Inv;
```


- **ENTITY** – Declares a new type of component
  - Named “And2” in this example
- **PORT( )** – List of inputs and outputs of entity
  - “x: IN std\_logic” → port “x” is an *input* port of type *std\_logic*
    - *std\_logic* short for “standard logic,” a logical *bit* type (versus say an integer type), which can be '0' or '1' (more later)
  - Ports in list separated by semicolons “;”


114



## AND/OR/NOT Gates Entities and Ports



 

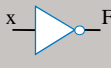


```
ENTITY And2 IS
  PORT (x: IN std_logic;
        y: IN std_logic;
        F: OUT std_logic);
END And2;
```

```
ENTITY Or2 IS
  PORT (x: IN std_logic;
        y: IN std_logic;
        F: OUT std_logic);
END Or2;
```

```
ENTITY Inv IS
  PORT (x: IN std_logic;
        F: OUT std_logic);
END Inv;
```

- VHDL has several dozen reserved words
  - ENTITY, IS, PORT, IN, OUT, and END are reserved words above
  - Our convention: Reserved words are UPPER CASE
  - User cannot use reserved words when naming items like ports or entities
- User-defined names
  - Begin with letter, optionally followed by sequence of letters, numbers, or underscore
    - No two underscores in a row, and can't end in underscore
  - Valid names: *A*, *x*, *Hello*, *JXYZ*, *B14*, *Sig432*, *Wire\_23*, *Index\_counter\_1*, *In1*, *test\_entity*
  - Invalid names: *IN* (reserved word), *Wire\_* (ends in underscore), *Wire\_\_23* (two underscores in a row), *4x1Mux* (doesn't start with a letter), *\_in4* (doesn't start with a letter)
- Note: VHDL is case ***insensitive***. ENTITY, Entity, entity, even EnTiTy, all mean the same

115



## Architecture Modeling Fundamentals

- Constants
- Signals
- Signal Assignments
- Operators
- Processes
- Variables
- Sequential Statements
- Subprograms
- Types

116

# MichiganTech

## Constants

- Associates value to name
- Constant declaration
  - Can be declared in ENTITY, ARCHITECTURE or PACKAGE
- ```
CONSTANT <name> : <DATA_TYPE> := <value>;
```


```
CONSTANT bus_width : INTEGER := 16;
```
- Cannot be changed by executing code
  - Remember generics are constants (parameters) that can be overwritten by passing new values into the entity at compile time, not during code execution
- Improves code readability
- Increases code flexibility

117

# MichiganTech
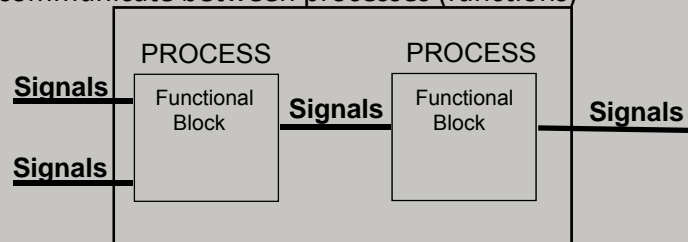
## Signals

- Signals represent physical interconnect (wire) that communicate between processes (functions)



- Signal declaration
  - Can be declared in PACKAGE, ENTITY and ARCHITECTURE

```
SIGNAL temp : STD_LOGIC_VECTOR (7 DOWNTO 0);
```

118

# MichiganTech

## Assigning Values to Signals

**SIGNAL** temp : STD\_LOGIC\_VECTOR (7 DOWNT0 0);

- Signal assignments are represented by <=
- Examples
  - All bits
    - temp <= "10101010";
    - temp <= x"aa" ; (1076-1993)
    - VHDL also supports 'o' for octal and 'b' for binary
  - Bit-slicing
    - temp (7 DOWNT0 4) <= "1010";
  - Single bit
    - temp(7) <= '1';
- Use double-quotes (" ") to assign multi-bit values and single-quotes ( ' ') to assign single-bit values

119

# MichiganTech


## Simple Signal Assignments

■ Format: `<signal_name> <= <expression>;`

■ Example:

```
qa <= r OR t ;
qb <= (qa AND NOT (g XOR h));
```

→ 2 implied processes

 

■ Expressions use VHDL operators to describe behavior

120

# MichiganTech Standard VHDL Operators

| Operator Type               |                 | Operator Name/Symbol                           | Priority                                    |
|-----------------------------|-----------------|------------------------------------------------|---------------------------------------------|
| Logical                     |                 | NOT AND OR<br>NAND NOR XOR XNOR <sup>(1)</sup> | <div>Low</div> <div>↓</div> <div>High</div> |
| Relational                  |                 | = /= < <= > >=                                 |                                             |
| Shifting <sup>(1) (2)</sup> |                 | SLL SRL SLA SRA ROL ROR                        |                                             |
| Arithmetic                  | Addition & Sign | + -                                            |                                             |
|                             | Concatenation   | &                                              |                                             |
|                             | Multiplication  | * / MOD REM                                    |                                             |
| Miscellaneous               |                 | ** ABS                                         |                                             |

\*\* = exponentiation

abs = absolute value

121

(1) Not supported in VHDL '87

(2) Supported in NUMERIC\_STD package for SIGNED/UNSIGNED data types

# MichiganTech

## Arithmetic Function

```

ENTITY opr IS
  PORT (
    a : IN INTEGER RANGE 0 TO 16;
    b : IN INTEGER RANGE 0 TO 16;
    sum : OUT INTEGER RANGE 0 TO 32
  );
END ENTITY opr;

ARCHITECTURE example OF opr IS
  BEGIN
    sum <= a + b;
  END ARCHITECTURE example;

```

The VHDL compiler can understand this operation because an arithmetic operation is defined for the built-in data type **INTEGER**

⇒ Note: remember the library **STD** and the package **STANDARD** do not need to be referenced

122

# MichiganTech

## Conditional Signal Assignments

### Format:


```
<signal_name> <= <signal/value> WHEN <condition_1> ELSE
<signal/value> WHEN <condition_2> ELSE
...
<signal/value> WHEN <condition_n> ELSE
<signal/value>;
```

### Example:

```
q <= a WHEN sela = '1' ELSE
    b WHEN selb = '1' ELSE
    c;
```

123

Implied process

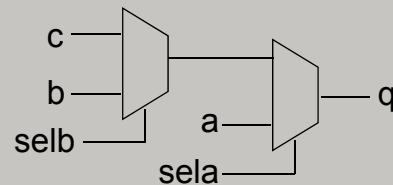

# MichiganTech

## Selected Signal Assignments

### Format:


```
WITH <expression> SELECT
<signal_name> <= <signal/value> WHEN <condition_1>,
<signal/value> WHEN <condition_2>,
...
<signal/value> WHEN OTHERS;
```

### Example:

```
WITH sel SELECT
q <= a WHEN "00",
    b WHEN "01",
    c WHEN "10",
    d WHEN OTHERS;
```

124

Implied process

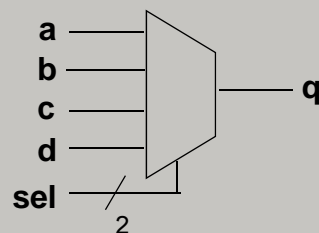




## Selected Signal Assignments

- **All** possible conditions must be considered
- **WHEN OTHERS** clause evaluates all other possible conditions that are not specifically stated

See next slide

 

125



## Selected Signal Assignment

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY cmpl_sig IS
  PORT (
    a, b, sel : IN STD_LOGIC;
    z : OUT STD_LOGIC
  );
END ENTITY cmpl_sig;

ARCHITECTURE logic OF cmpl_sig IS
BEGIN
  -- Selected signal assignment
  WITH sel SELECT
    z <= a WHEN '0',
        b WHEN '1',
        '0' WHEN OTHERS;
END ARCHITECTURE logic;
  
```

sel is of **STD\_LOGIC** data type

- What are the values for a **STD\_LOGIC** data type
- Answer: {'0','1','X','Z'...}
- Therefore, is the **WHEN OTHERS** clause necessary?
- Answer: **YES**

126



## VHDL Model - Concurrent Signal Assignments

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
```


```
ENTITY cmpl_sig is
  PORT (
    a, b, sel : IN STD_LOGIC;
    x, y, z : OUT STD_LOGIC
  );
END ENTITY cmpl_sig;
```

```
ARCHITECTURE logic OF cmpl_sig IS
  BEGIN
    -- Simple signal assignment
    x <= (a AND NOT sel) OR (b AND sel);

    -- Conditional signal assignment
    y <= a WHEN sel='0' ELSE
        b;


    -- Selected signal assignment
    WITH sel SELECT
      z <= a WHEN '0',
          b WHEN '1',
          'X' WHEN OTHERS;
  END ARCHITECTURE logic;
```

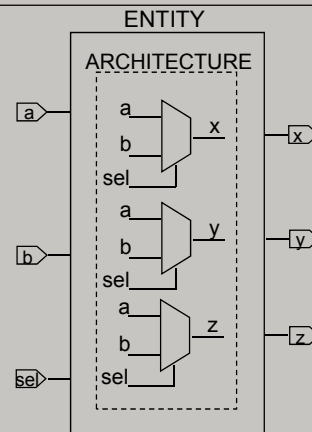- The signal assignments execute in parallel, and therefore the order we list the statements should not affect the outcome



## Process Statements

- Implicit process
  - Types
    - Concurrent signal assignments
    - Component instantiations
  - Process sensitive to all inputs
    - e.g. Read side of signal assignment
- Explicit process
  - PROCESS keyword defines process boundary




## Explicit PROCESS Statement

- Process sensitive to explicit (optional) sensitivity list
  - Events (transitions) on signals in sensitivity list trigger process
    - $0 \rightarrow 1$ ,  $X \rightarrow 1$ ,  $1 \rightarrow Z$ , etc
- Declaration section allows declaration of local objects and names
- Process contents consist of sequential statements and simple signal assignments

```
-- Explicit PROCESS statement
label : PROCESS (sensitivity_list)
    Constant declarations
    Type declarations
    Variable declarations
BEGIN
    Sequential statement #1;
    ...
    Sequential statement #n ;
END PROCESS;
```

129



## Execution of PROCESS Statement

- Process statement is executed infinitely unless broken by a WAIT statement or sensitivity list
- Sensitivity list implies a WAIT statement at the end of the process
  - Due to all processes being executed once at beginning of model execution
- Process can have multiple WAIT statements
- Process can not have both a sensitivity list and WAIT statement


```
PROCESS (a,b)
BEGIN
    Sequential statements
END PROCESS;
```

```
PROCESS
BEGIN
    Sequential statements
    WAIT ON (a,b) ;
END PROCESS;
```

⇒ Note: Logic synthesis places restrictions on the usage of WAIT statements as well as on the usage of sensitivity lists

130

## Multi-Process Architectures

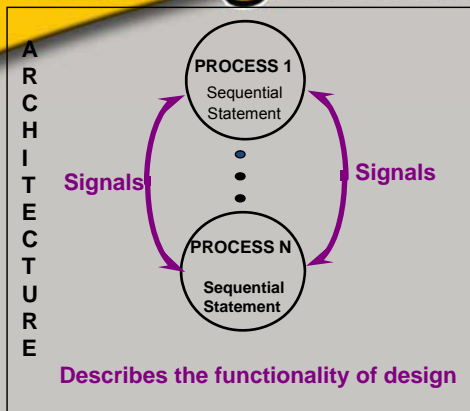

- An architecture can have multiple process statements
- Each process executes in parallel with other processes
  - Order of process blocks does not matter
- Within a process, the statements are executed sequentially
  - Order of statements within a process does matter

131

## YES Equivalent Functions??

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY simp IS
  PORT (
    a, b : IN STD_LOGIC;
    y : OUT STD_LOGIC
  );
END ENTITY simp;

ARCHITECTURE logic OF simp IS
  SIGNAL c : STD_LOGIC;
BEGIN
  c <= a AND b;
  y <= c;
END ARCHITECTURE logic;
  
```

c AND y get executed and updated in parallel at the end of the process within one simulation cycle

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY simp_prc IS
  PORT (
    a,b : IN STD_LOGIC;
    y : OUT STD_LOGIC
  );
END ENTITY simp_prc;

ARCHITECTURE logic OF simp_prc IS
  SIGNAL c : STD_LOGIC;
BEGIN
  process1: PROCESS (a, b)
  BEGIN
    c <= a AND b;
  END PROCESS process1;
  process2: PROCESS (c)
  BEGIN
    y <= c;
  END PROCESS process2;
END ARCHITECTURE logic;
  
```

132

## Equivalent Functions??

### MichiganTech

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY simp IS
  PORT (
    a, b : IN STD_LOGIC;
    y : OUT STD_LOGIC
  );
END ENTITY simp;

ARCHITECTURE logic OF simp IS
  SIGNAL c : STD_LOGIC;
BEGIN
  c <= a AND b;
  y <= c;
END ARCHITECTURE logic;

```

New value of c not available for y until next process execution (requires another simulation cycle or transition on a/b)

**NO**

⊘

### MichiganTech

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY simp_prc IS
  PORT (
    a, b : IN STD_LOGIC;
    y : OUT STD_LOGIC
  );
END ENTITY simp_prc;

ARCHITECTURE logic OF simp_prc IS
  SIGNAL c : STD_LOGIC;
BEGIN
  PROCESS (a, b)
  BEGIN
    c <= a AND b;
    y <= c;
  END PROCESS;
END ARCHITECTURE logic;

```

## IF-THEN Statements

### MichiganTech

■ Format:

```

IF <condition1> THEN
  {sequence of statement(s)}
ELSIF <condition2> THEN
  {sequence of statement(s)}
...
ELSE
  {sequence of statement(s)}
END IF;

```

### MichiganTech

■ Example:

```

PROCESS (sela, selb, a, b, c)
BEGIN
  IF sela='1' THEN
    q <= a;
  ELSIF selb='1' THEN
    q <= b;
  ELSE
    q <= c;
  END IF;
END PROCESS;

```

```

graph LR
    c --> M1
    b --> M1
    selb --> M1
    M1 -- a --> M2
    b --> M2
    sela --> M2
    M2 -- q --> q

```

# MichiganTech

## Sequential Statements

- Indicate behavior and express order
- Must be used inside explicit processes
- Sequential statements
  - IF-THEN statement
  - CASE statement
  - Looping statements
  - WAIT statements

135


# MichiganTech

## IF-THEN Statements

- Similar to conditional signal assignment
 
### Implicit Process

```
q <= a WHEN sela = '1' ELSE
  b WHEN selb = '1' ELSE
  c;
```



### Explicit Process

```
PROCESS (sela, selb, a, b, c)
BEGIN
  IF sela='1' THEN
    q <= a;
  ELSIF selb='1' THEN
    q <= b;
  ELSE
    q <= c;
  END IF;
END PROCESS;
```

136


# MichiganTech CASE Statement

## Format:

```
CASE {expression} IS
  WHEN <condition1> =>
    {sequence of statements}
  WHEN <condition2> =>
    {sequence of statements}
  ...
  WHEN OTHERS => -- (optional)
    {sequence of statements}
END CASE;
```
 
## Example:

```
PROCESS (sel, a, b, c, d)
BEGIN
  CASE sel IS
    WHEN "00" =>
      q <= a;
    WHEN "01" =>
      q <= b;
    WHEN "10" =>
      q <= c;
    WHEN OTHERS =>
      q <= d;
  END CASE;
END PROCESS;
```




# MichiganTech CASE Statement

- Similar to selected signal assignment
 
## Implicit Process

```
WITH sel SELECT
  q <= a WHEN "00",
  q <= b WHEN "01",
  q <= c WHEN "10",
  q <= d WHEN OTHERS;
```



## Explicit Process

```
PROCESS (sel, a, b, c, d)
BEGIN
  CASE sel IS
    WHEN "00" =>
      q <= a;
    WHEN "01" =>
      q <= b;
    WHEN "10" =>
      q <= c;
    WHEN OTHERS =>
      q <= d;
  END CASE;
END PROCESS;
```



## Sequential LOOPS

- **Infinite loop**
  - Loops forever
- **While loop**
  - Loops until conditional test is false
- **For loop**
  - Loops for certain number of iterations
  - Note: Iteration identifier not required to be previously declared
- Additional loop commands (each requires loop label)
  - **NEXT / NEXT WHEN**
    - Skips to next loop iteration
  - **EXIT / EXIT WHEN**
    - Cancels loop execution

### Infinite Loop

```
[Loop_label]: LOOP
--Sequential statement
EXIT loop_label ;
END LOOP;
```

### While Loop

```
WHILE <condition> LOOP
--Sequential statements
END LOOP;
```

### For Loop

```
FOR <identifier> IN <range> LOOP
--Sequential statements
END LOOP;
```

139



## WAIT

## Statements

- Pauses execution of process until WAIT statement is satisfied
- Types
  - WAIT ON <signal>
    - Pauses until signal event occurs

```
WAIT ON a, b;
```
  - WAIT UNTIL <boolean\_expression>
    - Pauses until boolean expression is true

```
WAIT UNTIL (int < 100);
```
  - WAIT FOR <time\_expression>
    - Pauses until time specified by expression has elapsed

```
WAIT FOR 20 ns;
```
  - Combined WAIT
 

```
WAIT UNTIL (a = '1') FOR 5 us;
```

\* Wait statement usage limited in synthesis

140

## Using WAIT Statements

```

stim: PROCESS
  VARIABLE error : BOOLEAN;
BEGIN
  WAIT UNTIL clk = '0';
  a <= (OTHERS => '0');
  b <= (OTHERS => '0');
  WAIT FOR 40 NS;
  IF (sum /= 0) THEN
    error := TRUE;
  END IF;

  WAIT UNTIL clk = '0';
  a <= "0010";
  b <= "0011";
  WAIT FOR 40 NS;
  IF (sum /= 5) THEN
    error := TRUE;
  END IF;

  ...

  WAIT;
END PROCESS stim;

```

Pause execution of the process until clk transitions to a logic 0

Pause execution of the process until the equivalent of 40 ns passes in simulation time

Pause execution of the process indefinitely

## Two Types of RTL Process Statements

- Combinatorial process
  - Sensitive to all inputs read by the process


- Example

```

PROCESS (a, b, sel)
PROCESS (ALL) -- VHDL-2008

```

 Sensitivity list includes all inputs used by the combinatorial logic




- Sequential process
  - Sensitive to select inputs (clock and asynchronous control signals)

- Example

```

PROCESS (clr, clk)

```

 

Sensitivity list does not include the d input, only the clock or/and control signals


# MichiganTech

## DFF

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY dff1 IS
  PORT (
    d : IN STD_LOGIC;
    clk : IN STD_LOGIC;
    q : OUT STD_LOGIC
  );
END ENTITY dff1;
```
 
```
ARCHITECTURE logic OF dff1 IS
BEGIN
  PROCESS (clk)
  BEGIN
    IF clk'EVENT AND clk = '1' THEN
      q <= d;
    END IF;
  END PROCESS;
END ARCHITECTURE behavior;
```



***clk'EVENT AND clk='1'***

- *clk* is the signal name (any name)
- **'EVENT'** is a VHDL attribute, specifying that there needs to be a change in signal value
- *clk='1'* means positive-edge triggered

143

# MichiganTech

## Types

- VHDL has built-in data types to model hardware (e.g. BIT, BOOLEAN, STD\_LOGIC)
- VHDL also allows creation of brand new types for declaring objects (i.e. constants, signals, variables)
- Subtype
- Enumerated Data Type
- Array

144

# MichiganTech

## Subtype

- A constrained type
- Synthesizable if base type is synthesizable
- Use to make code more readable and flexible
  - Place in package to use throughout design

```

ARCHITECTURE logic OF subtype_test IS

  SUBTYPE word IS std_logic_vector (31 DOWNTO 0);
  SIGNAL mem_read, mem_write : word;

  SUBTYPE dec_count IS INTEGER RANGE 0 TO 9;
  SIGNAL ones, tens : dec_count;

BEGIN

```

145

# MichiganTech

## Enumerated Data Type

- Allows user to create data type *name* and *values*
  - Must create constant, signal or variable of that type to use
- Used in
  - Making code more readable
  - Finite state machines
- Enumerated type declaration

```

TYPE <your_data_type> IS
  (data type items or values separated by commas);

```

```

TYPE enum IS (idle, fill, heat_w, wash, drain);
SIGNAL dshwshr_st : enum;

...
drain_led <= '1' WHEN dshwsher_st = drain ELSE '0';

```

146

# MichiganTech

## Array

- Creates multi-dimensional data type for storing values
  - Must create constant, signal or variable of that type
- Used to create memories and store simulation vectors
- Array type Declaration

```
TYPE <array_type_name> IS ARRAY (<integer_range>) OF
<data_type>;
```

array depth

what can be stored in each array address

147

# MichiganTech

## Array Example

**ARCHITECTURE** logic **OF** my\_memory **IS**

```
-- Creates new array data type named mem which has 64
-- address locations each 8 bits wide
```

```
TYPE mem IS ARRAY (0 to 63) OF std_logic_vector (7 DOWNTO 0);
```

```
-- Creates 2 - 64x8-bit array to use in design
```

```
SIGNAL mem_64x8_a, mem_64x8_b : mem;
```

**BEGIN**

```
...
```

```
mem_64x8_a(12) <= x"AF";
```

```
mem_64x8_b(50) <= "11110000";
```


```
...
```

**END ARCHITECTURE** logic;

148
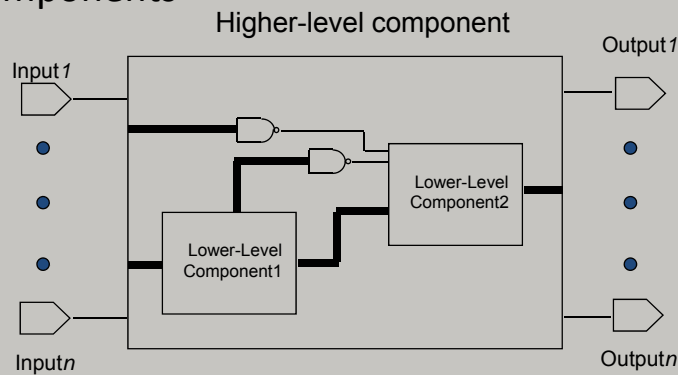
## MichiganTech Recall - Structural Modeling

- Functionality and structure of the circuit
- Call out the specific hardware, lower-level components




149

## MichiganTech
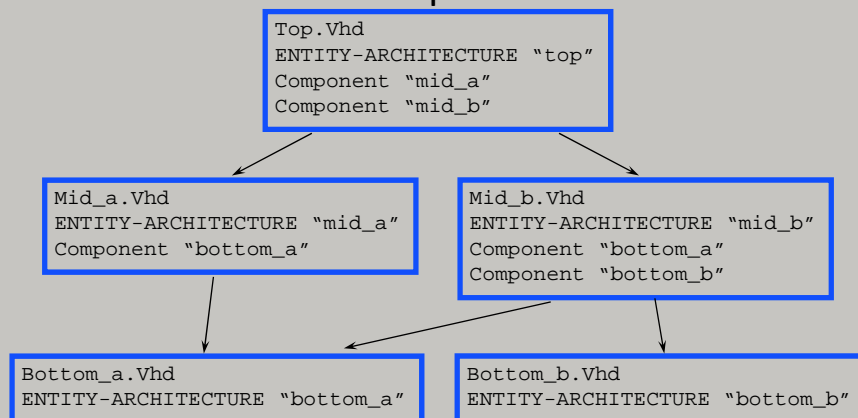
### Design Hierarchically - Multiple Design Files

- VHDL hierarchical design requires component declarations and component instantiations



150

# MichiganTech

## Component Declaration and Instantiation

- **Component declaration** - used to declare the *port types* and the *data types* of the ports for a lower-level design

```
COMPONENT <lower-level_design_name>
  PORT (
    <port_name> : <port_type> <data_type>;
    ...
    <Port_name> : <port_type> <data_type>
  );
END COMPONENT;
```

- **Component instantiation** - used to map the ports of a lower-level design to that of the current-level design


```
<Instance_name> : <lower-level_design_name>
  PORT MAP(<lower-level_port_name> => <current_level_port_name>,
    ..., <lower-level_port_name> => <current_level_port_name>);
```

151

# MichiganTech
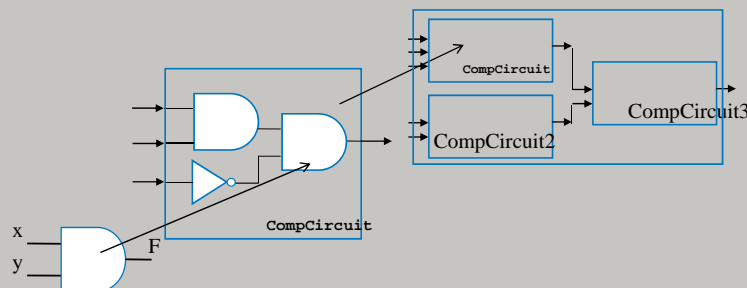
## Hierarchical Circuits Using Entities as Components

- Entity can be used as component in a new entity
  - AND entity used as component in `CompCircuit` entity
  - Can continue: `CompCircuit` entity can be used as component in another entity
    - And so on
- Hierarchy powerful mechanism for managing complexity




152

# MichiganTech

- 4-bit 2x1 mux example

2x1 mux circuit from earlier

 

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Mux2 IS
    PORT (i1, i0: IN std_logic;
          s0: IN std_logic;
          d: OUT std_logic);
END Mux2;

ARCHITECTURE Struct OF Mux2 IS
    COMPONENT And2 IS
        PORT (x, y: IN std_logic;
              F: OUT std_logic);
    END COMPONENT;
    COMPONENT Or2 IS
        PORT (x, y: IN std_logic;
              F: OUT std_logic);
    END COMPONENT;
    COMPONENT Inv IS
        PORT (x: IN std_logic;
              F: OUT std_logic);
    END COMPONENT;

    SIGNAL n1, n2, n3: std_logic;

BEGIN
    Inv_1: Inv PORT MAP (s0, n1);
    And2_1: And2 PORT MAP (i0, n1, n2);
    And2_2: And2 PORT MAP (i1, s0, n3);
    Or2_1: Or2 PORT MAP (n2, n3, d);
END Struct;

```

153


# MichiganTech

## Multifunction Register Behavior

- Now consider register with control inputs, such as load or shift

- Could describe structurally
  - Four flip-flops, four muxes, and some combinational logic (to convert control inputs to mux select inputs)
- We'll describe behaviorally

| Ld | Shr | Shl | Operation                               |
|----|-----|-----|-----------------------------------------|
| 0  | 0   | 0   | Maintain present value                  |
| 0  | 0   | 1   | Shift left                              |
| 0  | 1   | 0   | Shift right                             |
| 0  | 1   | 1   | Shift right – Shr has priority over Shl |
| 1  | 0   | 0   | Parallel load                           |
| 1  | 0   | 1   | Parallel load – Ld has priority         |
| 1  | 1   | 0   | Parallel load – Ld has priority         |
| 1  | 1   | 1   | Parallel load – Ld has priority         |

 

| Ld | shr | shl | Operation      |
|----|-----|-----|----------------|
| 0  | 0   | 0   | Maintain value |
| 0  | 0   | 1   | Shift left     |
| 0  | 1   | X   | Shift right    |
| 1  | X   | X   | Parallel load  |

Compact register operation table,  
clearly showing priorities

154

# MichiganTech

- Use IF statement
  - ELSIF parts ensure correct priority of control inputs
    - Rst has first priority, then Ld, then Shr, and finally Shl
- Shift by assigning each bit
  - Recall that statement order doesn't matter
- Use signal R for storage
  - Can't use port Q because OUT port cannot be read by process
- Use **concurrent signal assignment** to update Q when R changes
  - Equivalent to:
 

```
process(R)
begin
  Q <= R;
end process;
```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY MReg4 IS
  PORT (I: IN std_logic_vector(3 DOWNTO 0);
        Q: OUT std_logic_vector(3 DOWNTO 0);
        Ld, Shr, Shl, Shr_in, Shl_in: IN std_logic;
        Clk, Rst: IN std_logic );
END MReg4;

ARCHITECTURE Beh OF MReg4 IS
  SIGNAL R: std_logic_vector(3 DOWNTO 0);
BEGIN
  PROCESS (Clk)
  BEGIN
    IF (Clk = '1' AND Clk'EVENT) THEN
      IF (Rst = '1') THEN
        R <= "0000";
      ELSIF (Ld = '1') THEN
        R <= I;
      ELSIF (Shr = '1') THEN
        R(3) <= Shr_in; R(2) <= R(3);
        R(1) <= R(2); R(0) <= R(1);
      ELSIF (Shl = '1') THEN
        R(0) <= Shl_in; R(1) <= R(0);
        R(2) <= R(1); R(3) <= R(2);
      END IF;
    END IF;
  END PROCESS;

  Q <= R;
END Beh;

```


| ld | shr | shl | Operation      |
|----|-----|-----|----------------|
| 0  | 0   | 0   | Maintain value |
| 0  | 0   | 1   | Shift left     |
| 0  | 1   | X   | Shift right    |
| 1  | X   | X   | Parallel load  |

155

# MichiganTech
 
## AND Gate Simulation and Testbenches

Idea: Create new "Testbench" entity that provides test vectors to component's inputs



- A **testbench** is a setup for applying test vectors to test a design.
- The setup creates an entity called *Testbench* having no inputs or outputs.
- The setup instantiates a component representing the entity to be simulated, *CompToTest*
- The setup uses a process that writes to signals *x\_s* and *y\_s*, which are connected to the inputs of *CompToTest*.
- The process will contain statements that set the signals with the desired test vectors.

156

# MichiganTech

## • HDL testbench

- Entity with no ports
- Declare component to test
- Declare signal for each port
- Instantiate component, map signals to ports
- Set signal values at desired times

AND/OR/NOT Gates  
Simulation and  
Testbenches

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Testbench IS
END Testbench;

ARCHITECTURE TBarch OF Testbench IS
  COMPONENT And2 IS
    PORT (x: IN std_logic;
          y: IN std_logic;
          F: OUT std_logic);
  END COMPONENT;

  SIGNAL x_s, y_s, F_s: std_logic;

  BEGIN
    CompToTest: And2 PORT MAP (x_s, y_s, F_s);

    PROCESS
    BEGIN
      -- Test all possible input combinations
      y_s <= '0'; x_s <= '0';
      WAIT FOR 10 ns;
      y_s <= '0'; x_s <= '1';
      WAIT FOR 10 ns;
      y_s <= '1'; x_s <= '0';
      WAIT FOR 10 ns;
      y_s <= '1'; x_s <= '1';
      WAIT;
    END PROCESS;
  END TBarch;
```

157

# MichiganTech

- Process has no sensitivity list
  - Executes immediately
- "WAIT FOR 10 ns;"
  - Tells simulator to suspend this process, move simulation time forward by 10 ns before executing next statement
- "WAIT;" - no time clause
  - Waits forever – so process executes only once, doesn't repeat
- Note: Process cannot have both a sensitivity list and WAIT statement(s)

AND Gate  
Simulation and Testbenches

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Testbench IS
END Testbench;

ARCHITECTURE TBarch OF Testbench IS
  COMPONENT And2 IS
    PORT (x: IN std_logic;
          y: IN std_logic;
          F: OUT std_logic);
  END COMPONENT;

  SIGNAL x_s, y_s, F_s: std_logic;

  BEGIN
    CompToTest: And2 PORT MAP (x_s, y_s, F_s);

    PROCESS
    BEGIN
      -- Test all possible input combinations
      y_s <= '0'; x_s <= '0';
      WAIT FOR 10 ns;
      y_s <= '0'; x_s <= '1';
      WAIT FOR 10 ns;
      y_s <= '1'; x_s <= '0';
      WAIT FOR 10 ns;
      y_s <= '1'; x_s <= '1';
      WAIT;
    END PROCESS;
  END TBarch;
```

158

# MichiganTech

## • Component instantiation statement

CompToTest: And2 PORT MAP (x\_s, y\_s, f\_s);

Note: order same as in component declaration (positional)

Connects (maps) component ports to signals

Type of component  
From earlier component declarations

Name of new instance  
Must be distinct

## Combinational Circuits Component Instantiations

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Testbench IS
END Testbench;

ARCHITECTURE TBarch OF Testbench IS
  COMPONENT And2 IS
    PORT (x: IN std_logic;
          y: IN std_logic;
          F: OUT std_logic);
  END COMPONENT;

  SIGNAL x_s, y_s, F_s: std_logic;


BEGIN
  CompToTest: And2 PORT MAP (x_s, y_s, F_s);

  PROCESS
  BEGIN
    -- Test all possible input combinations
    y_s <= '0'; x_s <= '0';
    WAIT FOR 10 ns;
    y_s <= '0'; x_s <= '1';
    WAIT FOR 10 ns;
    y_s <= '1'; x_s <= '0';
    WAIT FOR 10 ns;
    y_s <= '1'; x_s <= '1';
    WAIT;
  END PROCESS;
END TBarch;
```

159
 
# MichiganTech

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY And2 IS
  PORT (x: IN std_logic;
        y: IN std_logic;
        F: OUT std_logic);
END And2;
ARCHITECTURE And2_beh OF And2 IS
BEGIN
  PROCESS(x, y)
  BEGIN
    F <= x AND y;
  END PROCESS;
END And2_beh;
```



Simulator

- Provide testbench file to simulator
  - Simulator generates waveforms
  - We can then check if behavior looks correct

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Testbench IS
END Testbench;

ARCHITECTURE TBarch OF Testbench IS
  COMPONENT And2 IS
    PORT (x: IN std_logic;
          y: IN std_logic;
          F: OUT std_logic);
  END COMPONENT;

  SIGNAL x_s, y_s, F_s: std_logic;

BEGIN
  CompToTest: And2 PORT MAP (x_s, y_s, F_s);

  PROCESS
  BEGIN
    -- Test all possible input combinations
    y_s <= '0'; x_s <= '0';
    WAIT FOR 10 ns;
    y_s <= '0'; x_s <= '1';
    WAIT FOR 10 ns;
    y_s <= '1'; x_s <= '0';
    WAIT FOR 10 ns;
    y_s <= '1'; x_s <= '1';
    WAIT;
  END PROCESS;
END TBarch;
```

## AND Gate Simulation and Testbenches

160

# MichiganTech

*Please go to Lab2  
Introduction to VHDL  
in the Manual*

161

# MichiganTech

## Syllabus

### Day 1

- 9:00 am Introduction
- 9:15 am What is an FPGA
- 9:45 am FPGA Design Techniques
- 1:00 pm Lab 1 – Introduction to Altera's Quartus
- 2:30 pm Introduction to VHDL
- 3:30 am Lab 2 - Introduction to VHDL

### Day 2

- 9:00 am Lab 3 - VHDL Testbench Lab
- 10:00 am Advanced VHDL
- 11:00 am Lab 4 – Advanced VHDL
- 1:00 pm Final Project (using DE2)
- 3:00 pm Support System (Software/hardware)
- 3:30 pm Implementation / Adaption Plan / Issues at schools
- 4:00 pm Conclusions / Feedback / Survey

**MichiganTech**

*Please go to Lab3  
VHDL Testbench  
in the Manual*

163

**MichiganTech**


## **Advanced VHDL Design Techniques**

**FSM**

Writing synthesizable VHDL

Create state machines and control their  
encoding

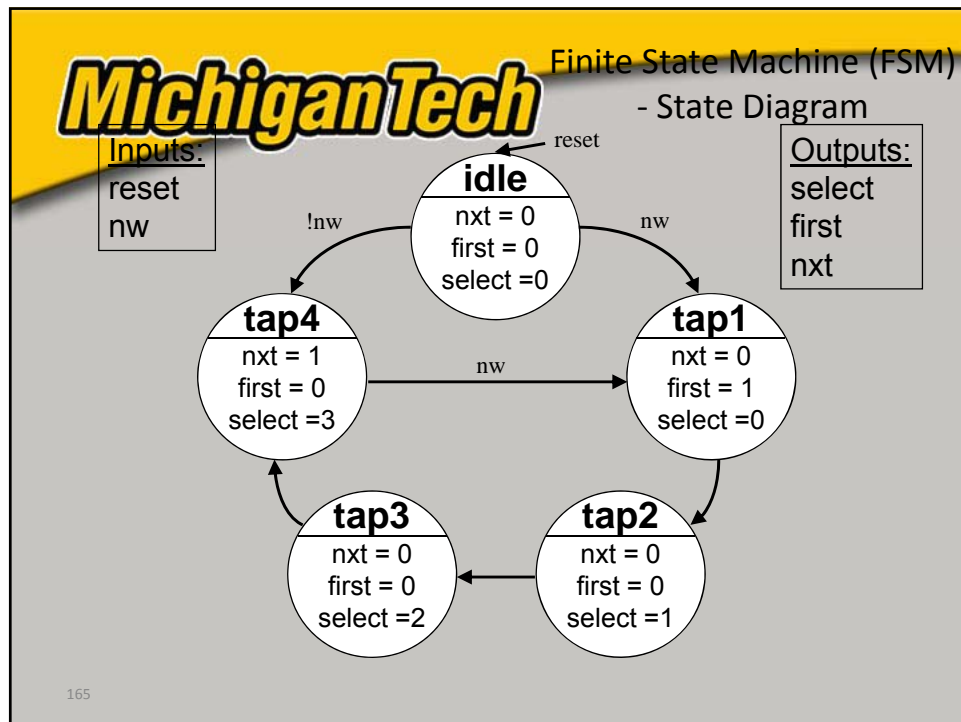Optimize designs to improve resource usage  
and performance



**MichiganTech** Writing VHDL  
Code for FSM

- State machine states must be an enumerated data type:
 

```
TYPE state_type IS (idle, tap1, tap2, tap3, tap4 );
```
- Object which stores the value of the current state must be a **signal** of the user-defined type:
 

```
SIGNAL filter : state_type;
```

166

# MichiganTech

## Writing VHDL Code for FSM (cont.)

- To determine next state transition/logic
  - Use a **CASE** statement inside a sequential process
- Use 1 of 2 methods to determine state machine outputs
  - Use a combinatorial process with a **CASE** statement
  - Use **conditional** and/or **selected** signal assignments for each output

167

# MichiganTech


```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY filter_sm IS
  PORT (
    clk, reset, nw : IN STD_LOGIC;
    select : OUT STD_LOGIC_VECTOR (1 DOWNTO 0);
    nxt, first : OUT STD_LOGIC
  );
END ENTITY filter_sm;
```

```
ARCHITECTURE logic OF filter_sm IS
```

```
  TYPE state_type IS (idle, tap1, tap2, tap3, tap4);
  SIGNAL filter : state_type;
```

```
BEGIN
```

 

Enumerated data type

## FSM VHDL Code - Enumerated Data Type


168

# MichiganTech

```

PROCESS (reset, clk)
BEGIN
  IF reset = '1' THEN
    filter <= idle;
  ELSIF clk' EVENT AND clk = '1' THEN
    CASE filter IS
      WHEN idle =>
        IF nw = '1' THEN
          filter <= tap1;
        END IF;
      WHEN tap1 =>
        filter <= tap2;
      WHEN tap2 =>
        filter <= tap3;
      WHEN tap3 =>
        filter <= tap4;
      WHEN tap4 =>
        IF nw = '1' THEN
          filter <= tap1;
        ELSE
          filter <= idle;
        END IF;
      END CASE;
    END IF;
  END PROCESS;

```

 

## FSM VHDL Code - Next State Logic


169

# MichiganTech

```

output: PROCESS (filter)
BEGIN
  nxt <= '0';
  first <= '0';
  select <= "00";
  CASE filter IS
    WHEN idle =>
      WHEN tap1 =>
        first <= '1';
      WHEN tap2 =>
        select <= "01";
      WHEN tap3 =>
        select <= "10";
      WHEN tap4 =>
        select <= "11";
        nxt <= '1';
      END CASE;
  END PROCESS output;
END ARCHITECTURE logic;

```

 

## FSM VHDL Code - Outputs Using CASE

170

## MichiganTech

```

nxt <= '1' WHEN filter=tap4 ELSE '0';
first <= '1' WHEN filter=tap1 ELSE '0';

WITH filter SELECT
  select <= "00" WHEN tap1,
            "01" WHEN tap2,
            "10" WHEN tap3,
            "11" WHEN tap4,
            "00" WHEN OTHERS;

END ARCHITECTURE logic;

```

### FSM VHDL Code - Outputs Using Signal Assignments

```

graph TD
    reset --> idle
    idle((idle  
nxt = 0  
first = 0  
select = 0)) -- nw --> tap1((tap1  
nxt = 1  
first = 1  
select = 0))
    tap1 -- nw --> tap2((tap2  
nxt = 0  
first = 0  
select = 1))
    tap2 -- nw --> tap3((tap3  
nxt = 0  
first = 0  
select = 2))
    tap3 -- nw --> tap4((tap4  
nxt = 1  
first = 0  
select = 3))
    tap4 -- nw --> idle

```

*Conditional signal assignments*

*Selected signal assignments*

171

## MichiganTech

### Simulation vs. Synthesis

- Simulation
  - Code executed in the exact way it is written
  - User has flexibility in writing
  - Initialization of logic supported
- Synthesis
  - Code is interpreted & hardware created
    - Knowledge of PLD architecture is important
  - Synthesis tools require certain coding to generate correct logic
    - Subset of VHDL language supported
    - Coding style is important for fast & efficient logic
  - Initialization controlled by device
  - Logic implementation can be adjusted to support initialization
- Pre- & post-synthesis logic should operate the same

172



## Writing Synthesizable VHDL

- Synthesizable VHDL Constructs
- Sensitivity lists
- Latches vs. registers
- **IF-THEN-ELSE** structures
- **CASE** statements
- Variables

173



## Some Synthesizable VHDL Constructs

- |                                                                                                                                                                                                                                                                                                                                                                                                                                                |                                                                                                                                                                                                                                                               |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <ul style="list-style-type: none"> <li>• ENTITY</li> <li>• ARCHITECTURE</li> <li>• CONFIGURATION</li> <li>• PACKAGE</li> <li>• Concurrent signal assignments</li> <li>• PROCESS</li> <li>• SIGNAL</li> <li>• VARIABLE (non-shared)</li> <li>• CONSTANT</li> <li>• IF-ELSE</li> <li>• CASE</li> <li>• Loops (fixed iteration)</li> <li>• Multi-dimensional arrays</li> <li>• PORT</li> <li>• GENERIC (constant)</li> <li>• COMPONENT</li> </ul> | <ul style="list-style-type: none"> <li>• Component &amp; direct instantiation</li> <li>• GENERATE</li> <li>• FUNCTION</li> <li>• PROCEDURE</li> <li>• ASSERT (constant false)</li> <li>• WAIT (one per process)</li> <li>• TYPE</li> <li>• SUBTYPE</li> </ul> |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|

– *Synthesis tools may place certain restrictions on supported constructs*

– *See the online help in Quartus II (or your target synthesis tool) for a complete list*

174

# MichiganTech

## Some Non-Synthesizable VHDL Constructs

- ACCESS
- ASSERT
- DISCONNECT
- FILE
- GROUP
- NEW
- Physical delay types
- PROTECTED
- SHARED VARIABLE
- Signal assignment delays

- These are some of the constructs not supported by Quartus II synthesis
- See the online help in Quartus II (or your target synthesis tool) for a complete list

175

# MichiganTech

## Two Types of RTL PROCESS Statements


- **Combinatorial PROCESS**
  - Sensitive to all signals used on right-hand side of assignment statements

- **Example**

```
PROCESS (a, b, sel)
```

Sensitivity list includes all inputs used in the combinatorial logic

```
sel
```

 


- **Sequential PROCESS**

- Sensitive to a clock and control signals

 - **Example**

```
PROCESS (clr, clk)
```

Sensitivity list does not include the d input, only the clock or/and control signals



176

# MichiganTech

## Sensitivity Lists

- Incomplete sensitivity list in combinational PROCESS blocks may result in differences between RTL & gate-level simulations
  - Synthesis tool synthesizes as if sensitivity list complete

```
PROCESS (a, b)
  y <= a AND b AND c;
```

**Incorrect Way** – the simulated behavior is not that of the synthesized 3-input AND gate

```
PROCESS (a, b, c)
  y <= a AND b AND c;
```

**Correct way for the intended AND logic !**

177


# MichiganTech

## Common Pitfall – Missing Inputs from Sensitivity List

- Pitfall – Missing inputs from sensitivity list when describing combinational behavior
  - Results in sequential behavior
  - Wrong 4x1 mux example
    - Has memory
    - No compiler error
      - Just not a mux
 
### Reminder

- Combinational behavior:** Output value is purely a function of the present input values
- Sequential behavior:** Output value is a function of present and past input values, i.e., the system has memory



```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Mux4 IS
  PORT (i3, i2, i1, i0: IN std_logic;
        s1, s0: IN std_logic;
        d: OUT std_logic);
END Mux4;

ARCHITECTURE Beh OF Mux4 IS
  BEGIN
    -- Note: missing i3, i2, i1, i0
    PROCESS (s1, s0)
    BEGIN
      IF (s1='0' AND s0='0') THEN
        d <= i0;
      ELSIF (s1='0' AND s0='1') THEN
        d <= i1;
      ELSIF (s1='1' AND s0='0') THEN
        d <= i2;
      ELSE
        d <= i3;
      END IF;
    END PROCESS;
  END Beh;
```

178



## Latches vs. Registers

- Altera devices have registers in logic elements, not latches
- Latches are implemented using combinatorial logic & can make timing analysis more complicated
  - Look-up table (LUT) devices use LUTs in combinatorial loops
  - Product-term devices use more product-terms
- Recommendations
  - Design with registers (RTL)
  - Watch out for inferred latches
    - Latches inferred on combinatorial outputs when results not specified for set of input conditions
    - Lead to simulation/synthesis mismatches

179



## IF-ELSE Structure

- IF-ELSE (like WHEN-ELSE concurrent assignment) structure implies prioritization & dependency
  - Nth clause implies all N-1 previous clauses not true
    - Beware of needlessly “ballooning” logic

Logical Equation

$$(<cond1> \cdot A) + (<\underline{cond1}>' \cdot <cond2> \cdot B) + (<\underline{cond1}>' \cdot <\underline{cond2}>' \cdot cond3 \cdot C) + \dots$$

- Consider restructuring IF statements
  - May flatten the multiplexer and reduce logic

IF <cond1> THEN  
IF <cond2> THEN



IF <cond1> AND <cond2> THEN

- If sequential statements are mutually exclusive, individual IF structures may be more efficient

180



## When Writing IF-ELSE Structures...

- Cover all cases
  - Uncovered cases in combinatorial processes result in latches
- For efficiency, consider
  - Using don't cares ('-' or 'X') for final ELSE clause (avoiding unnecessary default conditions)
    - Synthesis tool has freedom to encode don't cares for maximum optimization
  - Assigning initial values and explicitly covering only those results different from initial values

181




## Unwanted Latches

- Combinatorial processes that do not cover all possible input conditions generate latches

```

 PROCESS (sel, a, b, c)
BEGIN
  IF sel = "001" THEN
    output <= a;
  ELSIF sel = "010" THEN
    output <= b;
  ELSIF sel = "100" THEN
    output <= c;
  END IF;
END PROCESS;
  
```




182

# MichiganTech
 
## Unwanted Latches Removed

- Close all IF-ELSE structures
  - If possible, assign "don't care's" to else clause for improved logic optimization

```
PROCESS (sel, a, b, c)
BEGIN
  IF sel = "001" THEN
    output <= a;
  ELSIF sel = "010" THEN
    output <= b;
  ELSIF sel = "100" THEN
    output <= c;
  ELSE
    output <= (OTHERS => 'X');
  END IF;
END PROCESS;
```




183

# MichiganTech
 
## Common Pitfall – Output not Assigned on Every Pass

- Pitfall – Failing to assign every output on every pass through the process for combinational behavior
  - Results in sequential behavior
    - Referred to as inferred latch
  - Wrong 2x4 decoder example
    - Has memory
    - No compiler error
      - Just not a decoder



```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Dcd2x4 IS
  PORT (i1, i0: IN std_logic;
        d3, d2, d1, d0: OUT std_logic);
END Dcd2x4;

ARCHITECTURE Beh OF Dcd2x4 IS
BEGIN
  PROCESS(i1, i0)
  BEGIN
    IF (i1='0' AND i0='0') THEN
      d3 <= '0'; d2 <= '0';
      d1 <= '0'; d0 <= '1';
    ELSIF (i1='0' AND i0='1') THEN
      d3 <= '0'; d2 <= '0';
      d1 <= '1'; d0 <= '0';
    ELSIF (i1='1' AND i0='0') THEN
      d3 <= '0'; d2 <= '1';
      d1 <= '0'; d0 <= '0';
    ELSIF (i1='1' AND i0='1') THEN
      d3 <= '1';
    END IF;
    -- Note: missing assignments
    -- to all outputs in last ELSIF
  END PROCESS;
END Beh;
```

184

# MichiganTech

## Common Pitfall – Output not Assigned on Every Pass

- Same pitfall often occurs due to not considering all possible input combinations

```

PROCESS(i1, i0)
BEGIN
  IF (i1='0' AND i0='0') THEN
    d3 <= '0'; d2 <= '0';
    d1 <= '0'; d0 <= '1';
  ELSIF (i1='0' AND i0='1') THEN
    d3 <= '0'; d2 <= '0';
    d1 <= '1'; d0 <= '0';
  ELSIF (i1='1' AND i0='0') THEN
    d3 <= '0'; d2 <= '1';
    d1 <= '0'; d0 <= '0';
  END IF;
END PROCESS;

```

Last "ELSE" missing, so not all input combinations are covered (i.e., i1i0=11 not covered) – no update to the outputs

185

# MichiganTech


## Mutually Exclusive IF-ELSE Latches

- Beware of building unnecessary dependencies
  - e.g. Outputs x, y, z are mutually exclusive, IF-ELSIF causes all outputs to be dependant on all tests & creates latches

```

PROCESS (sel,a,b,c)
BEGIN
  IF sel = "010" THEN
    x <= a;
  ELSIF sel = "100" THEN
    y <= b;
  ELSIF sel = "001" THEN
    z <= c;
  ELSE
    x <= '0';
    y <= '0';
    z <= '0';
  END IF;
END PROCESS;

```

 


186

# MichiganTech
 
## Mutually Exclusive Latches Removed

- Separate IF statements and close

```
PROCESS (sel, a, b, c)
BEGIN
  IF sel = "010" THEN
    x <= a;
  ELSE
    x <= '0';
  END IF;
  IF sel = "100" THEN
    y <= b;
  ELSE
    y <= '0';
  END IF;
  IF sel = "001" THEN
    z <= c;
  ELSE
    z <= '0';
  END IF;
END PROCESS;
```



```
PROCESS (sel, a, b, c)
BEGIN
  x <= '0';
  y <= '0';
  z <= '0';
  IF sel = "010" THEN
    x <= a;
  END IF;
  IF sel = "100" THEN
    y <= b;
  END IF;
  IF sel = "001" THEN
    z <= c;
  END IF;
END PROCESS;
```

# MichiganTech

## Case Statements

- Case statements usually synthesize more efficiently when mutual exclusivity exists
- Define outputs for all cases
  - Undefined outputs for any given case generate latches
- VHDL already requires all case conditions be covered
  - Use **WHEN OTHERS** clause to close undefined cases (if any remain)

# MichiganTech

## Case Statement Recommendations

- Initialize all case outputs or ensure outputs assigned in each case
- Assign initialized or default values to don't cares (X) for further optimization, if logic allows

189

# MichiganTech

## Unwanted Latches - Case Statements

- Conditions where output is undetermined

```

output: PROCESS (filter)
BEGIN
  CASE filter IS
    WHEN idle =>
      nxt <= '0';
      first <= '0';
    WHEN tap1 =>
      sel <= "00";
      first <= '1';
    WHEN tap2 =>
      sel <= "01";
      first <= '0';
    WHEN tap3 =>
      sel <= "10";
    WHEN tap4 =>
      sel <= "11";
      nxt <= '1';
  END CASE;
END PROCESS output;

```

sel missing

nxt missing

nxt missing

nxt &amp; first missing

first missing

- Undetermined output conditions implies memory
- Latch generated for **ALL** 3 outputs

190

# MichiganTech

## Latches Removed - Case Statements

- Conditions where output is determined

```
output: PROCESS(filter)
BEGIN
    first <= '0';
    nxt <= '0';
    sel <= "00";
    CASE filter IS
        WHEN idle =>
            WHEN tap1 =>
                first <= '1';
            WHEN tap2 =>
                sel <= "01";
            WHEN tap3 =>
                sel <= "10";
            WHEN tap4 =>
                sel <= "11";
                nxt <= '1';
    END CASE;
END PROCESS output;
```

← Signals Initialized

*To remove latches & ensure outputs are never undetermined*

- Use signal initialization at beginning of case statement (case statement only deals with changes)
- Use don't cares ('-') for WHEN OTHERS clause, if design allows (for better logic optimization)
- Manually set output in each case

191

# MichiganTech

## Variables

- May synthesize to hardware depending on use
- Advantages vs. signals
  - Variables are a more behavioral construct as they don't have a direct correlation to hardware (like signals) and may lead to more efficient logic
  - Simulate more efficiently as they require less memory
    - Signals not updated immediately, so simulator must store two values (current and next value) for every changing signal
    - Variables updated immediately, so simulator stores single value
- Disadvantages vs. signals
  - Must be assigned to signal before process ends
    - Do not represent physical hardware unless equated with signal
  - Must be handled with care
    - Requires fully understand assigning values to variables and signals in same process and how dataflow is effected

192

# MichiganTech

## Variables & Latches (Recommendations)

- Assign an initial value or signal to a variable unless feedback is desired
- If a variable is not assigned an initial value or signal in a combinatorial process, a latch will be generated
  - This could cause your design to not function as intended

193

# MichiganTech

## Variable Uninitialized


```

ARCHITECTURE logic OF cmb_vari IS
BEGIN
  PROCESS(i0, i1, a)
    VARIABLE val :
      INTEGER RANGE 0 TO 1;
  BEGIN
    IF (a = '0') THEN
      val := val;
    ELSE
      val := val + 1;
    END IF;

    CASE val IS
      WHEN 0 =>
        q <= i0;
      WHEN OTHERS =>
        q <= i1;
    END CASE;
  END PROCESS;
END ARCHITECTURE logic;

```

Variable used without initialization

 

194



## Assign Initial Value to Variable


```

ARCHITECTURE logic OF cmb_vari IS
BEGIN
  PROCESS(i0, i1, a)
    VARIABLE val :
      INTEGER RANGE 0 TO 1;
  BEGIN
    val := 0;
    IF (a = '0') THEN
      val := val;
    ELSE
      val := val + 1;
    END IF;

    CASE val IS
      WHEN 0 =>
        q <= i0;
      WHEN OTHERS =>
        q <= i1;
    END CASE;
  END PROCESS;
END ARCHITECTURE logic;

```

 Assign initial value or  
signal to **variable**




## Synthesizable Subprograms

- Make code more readable/reusable
- Two types
  - Functions
    - Synthesize to combinatorial logic
  - Procedures
    - Can synthesize to combinatorial or sequential logic
      - Signal assignments in procedures called from clocked processes generate registers
      - May test for clock edges
        - » May not be supported by all synthesis tools
    - Must not contain WAIT statements
- Each call generates a separate block of logic
  - No logic sharing
  - Implement manual resource sharing, if possible (discussed later)

# MichiganTech
 
## Combinational Loops

- Common cause of instability
- Behavior of loop depends on the relative propagation delays through logic
  - Propagation delays can change
- Simulation tools may not match hardware behavior



```

PROCESS (clk, clrn)
BEGIN
  IF clrn = '0' THEN
    q <= 0;
  ELSIF rising_edge (clk) THEN
    q <= d;
  END IF;
END PROCESS;

clrn <= (ctrl1 XOR ctrl2) AND q;


```

197

# MichiganTech
 
## Combinational Loops

- All feedback loops should include registers



```

PROCESS (clk, clrn)
BEGIN
  IF clrn = '0' THEN
    q <= 0;
  ELSIF rising_edge (clk)
    q <= d;
  END IF;
END PROCESS;

PROCESS (clk)
BEGIN
  IF rising_edge (clk) THEN
    clrn <= (ctrl1 XOR ctrl2) AND q;
  END IF;
END PROCESS;

```

198

# MichiganTech State Machine Coding

- Enumerated data type is used to define the different states in the state machine
  - Using constants for states may not be recognized as state machine

```
TYPE state_type IS (idle, fill, heat_w, wash, drain);
```

- One or two signals assigned to the name of the state-variable :

```
SIGNAL current_state, next_state : state_type;
```

- Use CASE statement to do the next-state logic, instead of IF-THEN statement
  - Synthesis tools recognize CASE statements for implementing state machines
- Use CASE or IF-THEN-ELSE for output logic

199

# MichiganTech Quartus II Software State Machine Viewer

- Use to verify correct coding of state machine


Tools Menu ⇒  
State Machine Viewer

State Flow Diagram

Use Drop-Down to  
Select State Machine

Highlighting State in State  
Transition Table Highlights  
Corresponding State in State  
Flow Diagram

State Transition/Encoding Table

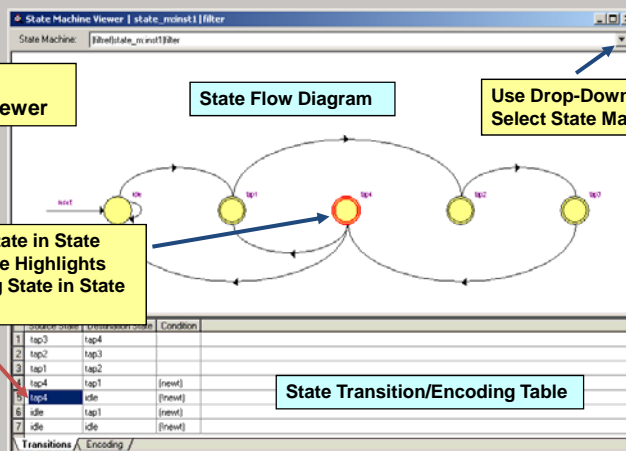

200

# MichiganTech

```

ENTITY wm IS
PORT (
    clk, reset, door_closed, full : in std_logic;
    heat_demand, done, empty : in std_logic;
    water, spin, heat, pump : out std_logic);
END ENTITY wm;


```

```

ARCHITECTURE behave OF wm IS
    TYPE state_type IS
        (idle, fill, heat_w, wash, drain);
    SIGNAL current_state, next_state :
        state_type;
BEGIN

```

## State Declaration

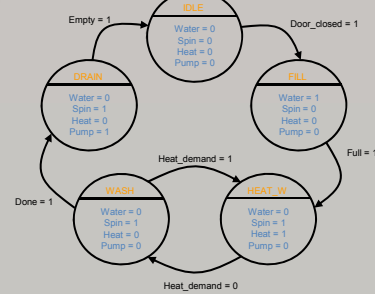

201

# MichiganTech


```

PROCESS (clk, reset)
BEGIN
    IF reset = '1' THEN
        current_state <= idle;
    ELSIF rising_edge(clk) THEN
        current_state <= next_state;
    END IF;
END PROCESS;

PROCESS (current_state, door_closed, full,
        heat_demand, done, empty)
BEGIN
    next_state <= current_state;
    CASE current_state IS
        WHEN idle =>
            IF door_closed = '1' THEN
                next_state <= fill;
            END IF;
        WHEN fill =>
            IF full = '1' THEN
                next_state <= heat_w;
            END IF;
        WHEN heat_w =>
            IF heat_demand = '0' THEN
                next_state <= wash;
            ELSE
                next_state <= heat_w;
            END IF;
        WHEN wash =>
            IF done = '1' THEN
                next_state <= drain;
            ELSE
                next_state <= wash;
            END IF;
        WHEN drain =>
            next_state <= idle;
    END CASE;
END PROCESS;

```

## Next State Logic

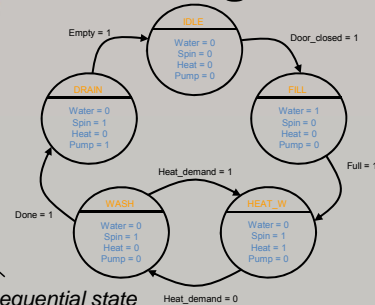

Sequential state transitions

Default next state is current state

Combinatorial next state logic

202

# MichiganTech


```

PROCESS (current_state)
BEGIN
    water <= '0';
    spin <= '0';
    heat <= '0';
    pump <= '0';
    CASE current_state IS
        WHEN idle =>
        WHEN fill =>
            water <= '1';
        WHEN heat_w =>
            spin <= '1';
            heat <= '1';
        WHEN wash =>
            spin <= '1';
        WHEN drain =>
            spin <= '1';
            pump <= '1';
    END CASE;
END PROCESS;

```

*Default output conditions*

## Combinatorial Outputs

 

– Output logic function of current state only

203

# MichiganTech

## State Machine Encoding Styles

| State  | Binary Encoding | Grey-Code Encoding | One-Hot Encoding | Custom Encoding |
|--------|-----------------|--------------------|------------------|-----------------|
| Idle   | 000             | 000                | 00001            | ?               |
| Fill   | 001             | 001                | 00010            | ?               |
| Heat_w | 010             | 011                | 00100            | ?               |
| Wash   | 011             | 010                | 01000            | ?               |
| Drain  | 100             | 110                | 10000            | ?               |


### ■ Quartus II default encoding styles for Altera devices

- One-hot encoding for look-up table (LUT) devices
  - Architecture features lesser fan-in per cell and an abundance of registers
- Binary (minimal bit) or grey-code encoding for product-term devices
  - Architecture features fewer registers and greater fan-in

204

## Quartus II

# Encoding Style

 

**Apply Assignment to State Variable**

Options:

- One-Hot
- Gray
- Minimal Bits
- Sequential
- User-Encoded
- Johnson

205

# MichiganTech

## Undefined States

- Noise and spurious events in hardware can cause state machines to enter undefined states
- If state machines do not consider undefined states, it can cause mysterious “lock-ups” in hardware
- Good engineering practice is to consider these states
- To account for undefined states
  - Explicitly code for them (manual)
  - Use “safe” synthesis constraint (automatic)

206

# MichiganTech

## ‘Safe’ Binary State Machine?

```

TYPE state_type IS
    (idle, full, heat_w, wash, drain);
SIGNAL current_state, next_state : state_type;

PROCESS (current_state, door_closed, full, heat_demand, done, empty)
BEGIN
    next_state <= current_state;
    CASE current_state IS
        WHEN idle =>
            IF door_closed = '1' THEN next_state <= full;
            END IF;
        WHEN full =>
            IF full = '1' THEN next_state <= heat_w;
            END IF;
        WHEN heat_w =>
            IF heat_demand = '0' THEN next_state <= wash;
            END IF;
        WHEN wash =>
            IF heat_demand = '1' THEN next_state <= heat_w;
            ELSIF done = '1' THEN next_state <= drain;
            END IF;
        WHEN drain =>
            IF empty = '1' THEN next_state <= idle;
            END IF;
        WHEN others =>
            next_state <= idle;
    END CASE;
END PROCESS;

```

207

- This code does not consider undefined states
- The “when others” statement only considers other enumerated states
- The states “101”, “110” & “111” are not considered

# MichiganTech

## Creating “Safe” State Machines

- WHEN OTHERS clause does not make state machines “safe”
  - Once state machine is recognized, synthesis tool only accounts for explicitly defined states
  - Exception: Number of states equals power of 2 AND binary/grey encoding enabled
- Safe state machines created using synthesis constraints
  - Quartus II software uses
    - SAFE STATE MACHINE assignment applied project-wide and to individual FSMs
    - VHDL synthesis attribute
  - May increase logic usage

|   | From    | To            | Assignment Name    | Value | Enabled |
|---|---------|---------------|--------------------|-------|---------|
| 1 |         | current_state | Safe State Machine | On    | Yes     |
| 2 | <<new>> | <<new>>       | <<new>>            |       |         |

208

**MichiganTech**

VHDL Logic

Optimization & Performance

- Balancing operators
- Resource sharing
- Logic duplication
- Pipelining

209

**MichiganTech**

Operators

- Synthesis tools replace operators with pre-defined (pre-optimized) blocks of logic
- Designer should control when & how many operators
  - Ex. Dividers
    - Dividers are large blocks of logic
    - Every '/', mod and rem inserts a divider block and leaves it up to synthesis tool to optimize
    - Better resource optimization usually involves cleverly using multipliers or shift operations to do divide

210


# MichiganTech

## Generating Logic from Operators


- Synthesis tools break down code into logic blocks
- They then assemble, optimize & map to hardware

```
IF (sel < 10) THEN
  y <= a + b;
ELSE
  y <= a + 10;
END IF;
```


1 Comparator

 

2 Adders

 

1 Multiplexer

 

211


# MichiganTech

## Balancing Operators

- Use parenthesis to define logic groupings
  - Increases performance
  - May increase utilization
  - Balances delay from all inputs to output
  - Circuit functionality unchanged


### Unbalanced

$$z \leq a * b * c * d$$

 

### Balanced

$$z \leq (a * b) * (c * d)$$

 

212


# MichiganTech

## Balancing Operators: Example

- a, b, c, d: 4-bit vectors

### Unbalanced


$$z \leq a * b * c * d$$

 

213

### Balanced

$$z \leq (a * b) * (c * d)$$

 

# MichiganTech

## Resource Sharing

- Reduces number of operators needed
  - Reduces area
- Two types
  - Sharing operators among mutually exclusive functions
  - Sharing common subexpressions
- Synthesis tools can perform automatic resource sharing
  - Feature can be enabled or disabled


214

# MichiganTech
 
## Mutually Exclusive Operators

```
process(rst, clk)
variable tmp_q : std_logic_vector(7 DOWNT0 0);
begin
  if rst = '0' then
    tmp_q := (OTHERS => '0');
  elsif rising_edge(clk) then
    if updn = '1' then
      tmp_q := tmp_q + 1;
    else
      tmp_q := tmp_q - 1;
    end if;
  end if;
  q <= tmp_q;
end process;
```

- Up/down counter
- 2 adders are mutually exclusive & can be shared (typically IF-THEN-ELSE with same operator in both choices)




215

# MichiganTech
 
## Sharing Mutually Exclusive Operators

```
process(rst, clk)
variable tmp_q : std_logic_vector(7 DOWNT0 0);
variable dir : integer range -1 to 1;
begin
  if rst = '0' then
    tmp_q := (OTHERS => '0');
  elsif rising_edge(clk) then
    if updn = '1' then
      dir := 1;
    else
      dir := -1;
    end if;
    tmp_q := tmp_q + dir;
  end if;
  q <= tmp_q;
end process;
```

- Up/down counter
- Only one adder required



216

# MichiganTech

How Many Multipliers?


$$y \leq a * b * c$$
$$z \leq b * c * d$$

217
 
# MichiganTech

How Many  
Multipliers?  
(Answer)

$$y \leq a * b * c$$
$$z \leq b * c * d$$



4 Multipliers!

218

# MichiganTech

## How Many Multipliers Again?

$$y \leq a * (b * c)$$

$$z \leq (b * c) * d$$


219

# MichiganTech

## How Many Multipliers Again? (Answer)

$$y \leq a * (b * c)$$

$$z \leq (b * c) * d$$

 

**3 Multipliers!**

- This is called sharing common subexpressions
- Some synthesis tools do this automatically, but some don't!
- Parentheses guide synthesis tools
- If  $(b*c)$  is used repeatedly, assign to temporary signal

220

***MichiganTech***

*Please go to Lab4  
Advanced VHDL  
in the Manual*

221

***MichiganTech***

*Please go to  
Final Project  
in the Manual*

222



## Educational Materials Available

- Project Website:  
[http:// www.tech.mtu.edu/NSFATE](http://www.tech.mtu.edu/NSFATE)
  
- Altera University Program website  
<http://www.altera.com/education/univ/unv-index.html>

223



## What do you really need to start?

- Quratus Software
  
- DE2 FPGA board

224

## **MichiganTech**

### SW/HW donation

- Register with Altera website
- Request DE2 Boards

<http://www.altera.com/education/univ/materials/boards/de2-115/unv-de2-115-board.html>

225

## **MichiganTech**

### One More workshop

We will offer one more free two-day workshop

**Time:** Summer 2012

**Date:** TBD

**Location:** College of Lake County - IL

226

**MichiganTech**

Post Test  
survey

227

**MichiganTech**

Thank You ?

Thanks to  
National Science Foundation  
Advanced Technological Education



228

# Lab Manual

---

## for VHDL and FPGA Design Workshop

### **Software Requirements to complete all exercises**

Quartus II software version 9.1 or newer

### **Link to the Quartus II Handbook:**

[http://www.altera.com/literature/hb/qts/quartusii\\_handbook.pdf](http://www.altera.com/literature/hb/qts/quartusii_handbook.pdf)

### **Link to the project web page to download the related lab files:**

<http://www.tech.mtu.edu/NSFATE/>

# Lab 1

---

Introduction to Quartus II

## **Lab 1 – Introduction to Quartus II**

This lab is designed to familiarize you with using many of the common aspects of the Quartus II software through a complete design phase. You will create a new project, create a new vhdl file, use the MegaWizard Plug-In Manager, compile the design, plan and manage I/O assignments, apply timing analysis using the TimeQuest Timing Analyzer, write Synopsys Design Constraint (SDC) files, and program a design onto the Altera DE2 Development Board.

## Task 1: Create a New Project

### 1. Start the Quartus II software.

From the Windows Start Menu, select:

**All Programs → Other Apps → Altera → Quartus II 9.1 → Quartus II 9.1 (32-Bit)**

### 2. Start the New Project Wizard.

If the opening splash screen is displayed, select: **Create a New Project (New Project Wizard)**, otherwise from the Quartus II Menu Bar select: **File → New Project Wizard**.

### 3. Select the Working Directory and Project Name.

|                         |                         |
|-------------------------|-------------------------|
| Working Directory       | H:\Altera_Training\Lab1 |
| Project Name            | Lab1                    |
| Top-Level Design Entity | Lab1                    |

Click **Next** to advance to page 2 of the New Project Wizard.

*Note: A window may pop up stating that the chosen working directory does not exist. Click **Yes** to create it.*

The screenshot shows the 'New Project Wizard: Directory, Name, Top-Level Entity [page 1 of 5]' dialog box. It contains three text input fields with browse buttons (three dots) to the right. The first field is labeled 'What is the working directory for this project?' and contains the text 'H:\Altera\_Training\Lab1'. The second field is labeled 'What is the name of this project?' and contains the text 'Lab1'. The third field is labeled 'What is the name of the top-level design entity for this project? This name is case sensitive and must exactly match the entity name in the design file.' and contains the text 'Lab1'. Below these fields is a button labeled 'Use Existing Project Settings ...'. At the bottom of the dialog are four buttons: '< Back', 'Next >', 'Finish', and 'Cancel'.

4. Click **Next** again as we will not be adding any preexisting design files at this time.
5. **Select the family and Device Settings.**  
 From the pull-down menu labeled **Family**, select **Cyclone II**.  
 In the list of available devices, select **EPC235F672C6**.  
 Click **Next**.

**New Project Wizard: Family & Device Settings [page 3 of 5]**

Select the family and device you want to target for compilation.

Device family:  
 Family: **Cyclone II**  
 Devices: **All**

Target device:  
☐ Auto device selected by the Fitter  
☒ Specific device selected in 'Available devices' list

Show in 'Available device' list:  
 Package: **Any**  
 Pin count: **Any**  
 Speed grade: **Any**  
☒ Show advanced devices  
☐ HardCopy compatible only

Available devices:


| Name                | Core voltage | LEs          | User I/O... | Memor...      | Embed...  |
|---------------------|--------------|--------------|-------------|---------------|-----------|
| EP2C20Q240C8        | 1.2V         | 18752        | 142         | 239616        | 52        |
| EP2C35F484C6        | 1.2V         | 33216        | 322         | 483840        | 70        |
| EP2C35F484C7        | 1.2V         | 33216        | 322         | 483840        | 70        |
| EP2C35F484C8        | 1.2V         | 33216        | 322         | 483840        | 70        |
| EP2C35F484I8        | 1.2V         | 33216        | 322         | 483840        | 70        |
| <b>EP2C35F672C6</b> | <b>1.2V</b>  | <b>33216</b> | <b>475</b>  | <b>483840</b> | <b>70</b> |
| EP2C35F672C7        | 1.2V         | 33216        | 475         | 483840        | 70        |
| EP2C35F672C8        | 1.2V         | 33216        | 475         | 483840        | 70        |
| EP2C35F672I8        | 1.2V         | 33216        | 475         | 483840        | 70        |

Companion device:  
 HardCopy: **None**  
☒ Limit DSP & RAM to HardCopy device resources

< Back   **Next >**   Finish   Cancel

6. Click **Next** again as we will not be using any third party EDA tools.

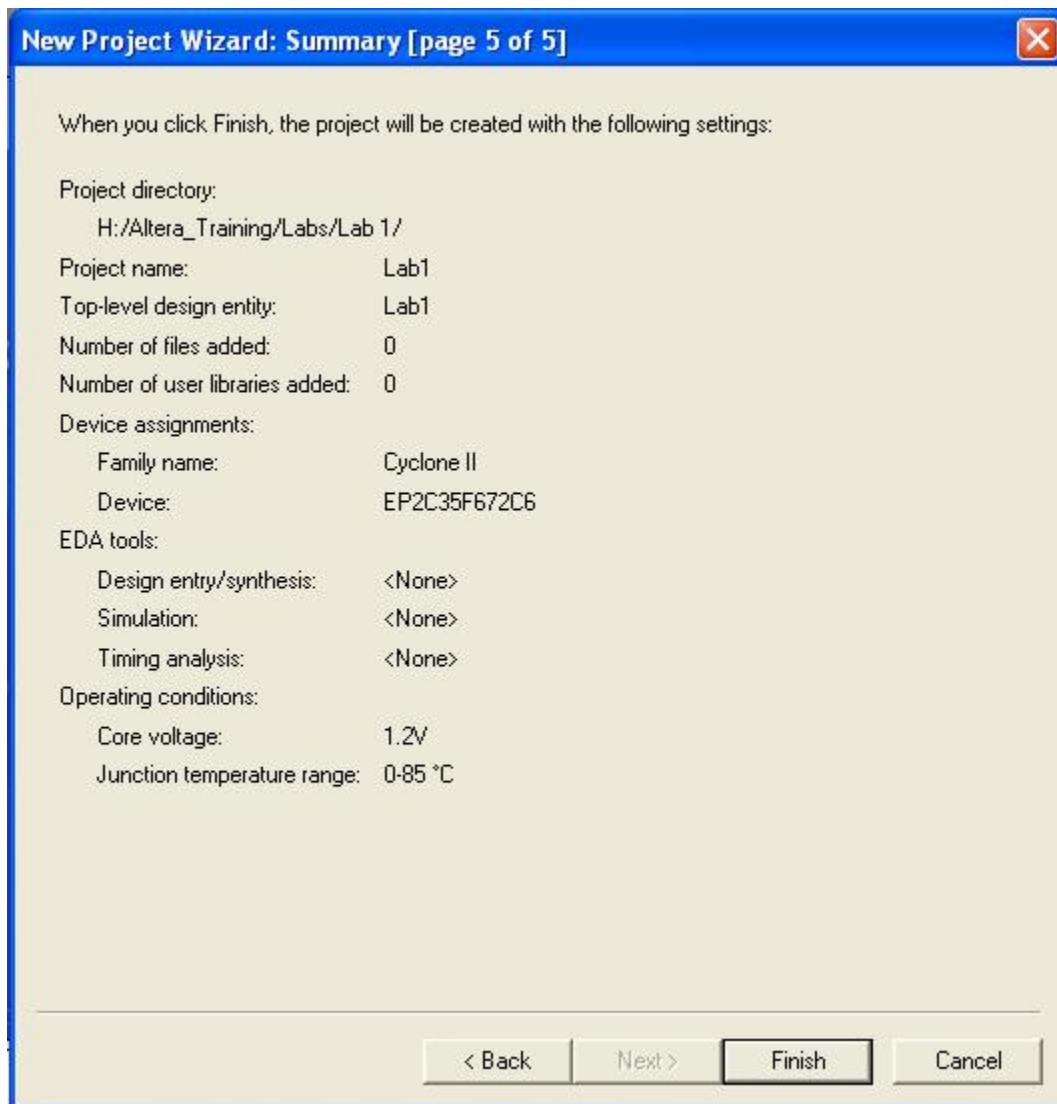7. Click **Finish** to complete the New Project Wizard.




---

## Task 2: Create, Add, and Compile Design Files
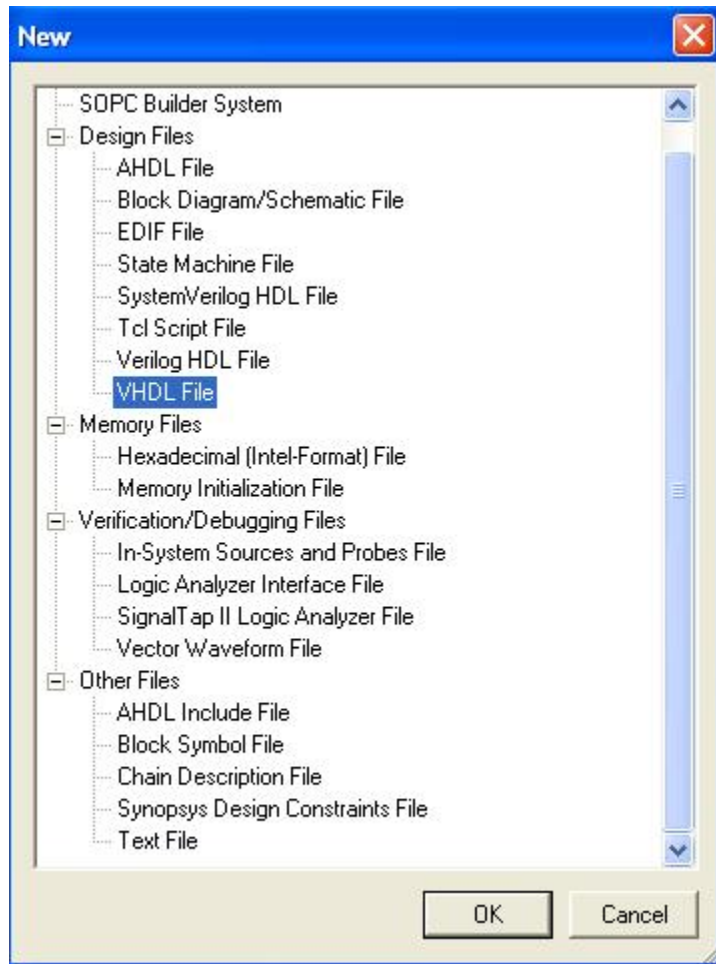
### 1. Create a new Design File.

Select: **File** → **New** from the Menu Bar.

Select: **VHDL File** from the **Design Files** list and click **OK**.



2. Copy and paste the following code into your new VHDL file, then save it by selecting **File** → **Save**. Keep the default file name and click **Save** in the **Save As** dialog box.

| Lab 1 – Introduction to Quartus II – VHDL Code                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                               |
|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <pre>LIBRARY ieee; USE ieee.std_logic_1164.all;  ENTITY Lab1 IS     PORT (clk: IN STD_LOGIC;           input0, input1, input2: IN STD_LOGIC_VECTOR (3 DOWNTO 0);           sel: IN STD_LOGIC_VECTOR (1 DOWNTO 0);           output: OUT STD_LOGIC_VECTOR (3 DOWNTO 0)); END Lab1;  ARCHITECTURE Structure OF Lab1 IS     COMPONENT Mux3x1 IS         PORT (clock: IN STD_LOGIC;               data0x, data1x, data2x: IN STD_LOGIC_VECTOR (3 DOWNTO 0);               sel: IN STD_LOGIC_VECTOR (1 DOWNTO 0);               result: OUT STD_LOGIC_VECTOR (3 DOWNTO 0));     END COMPONENT; BEGIN     MuxOut: Mux3x1 PORT MAP (clk, input0, input1, input2, sel, output); END Structure;</pre> |


3. **Create an 4-Bit 3x1 Multiplexer using the MegaWizard® Plug-in Manager**

Select: **Tools** → **MegaWizard Plug-In Manager**


Select the radio button for **Create a new custom megafunction variation** and click **Next**.



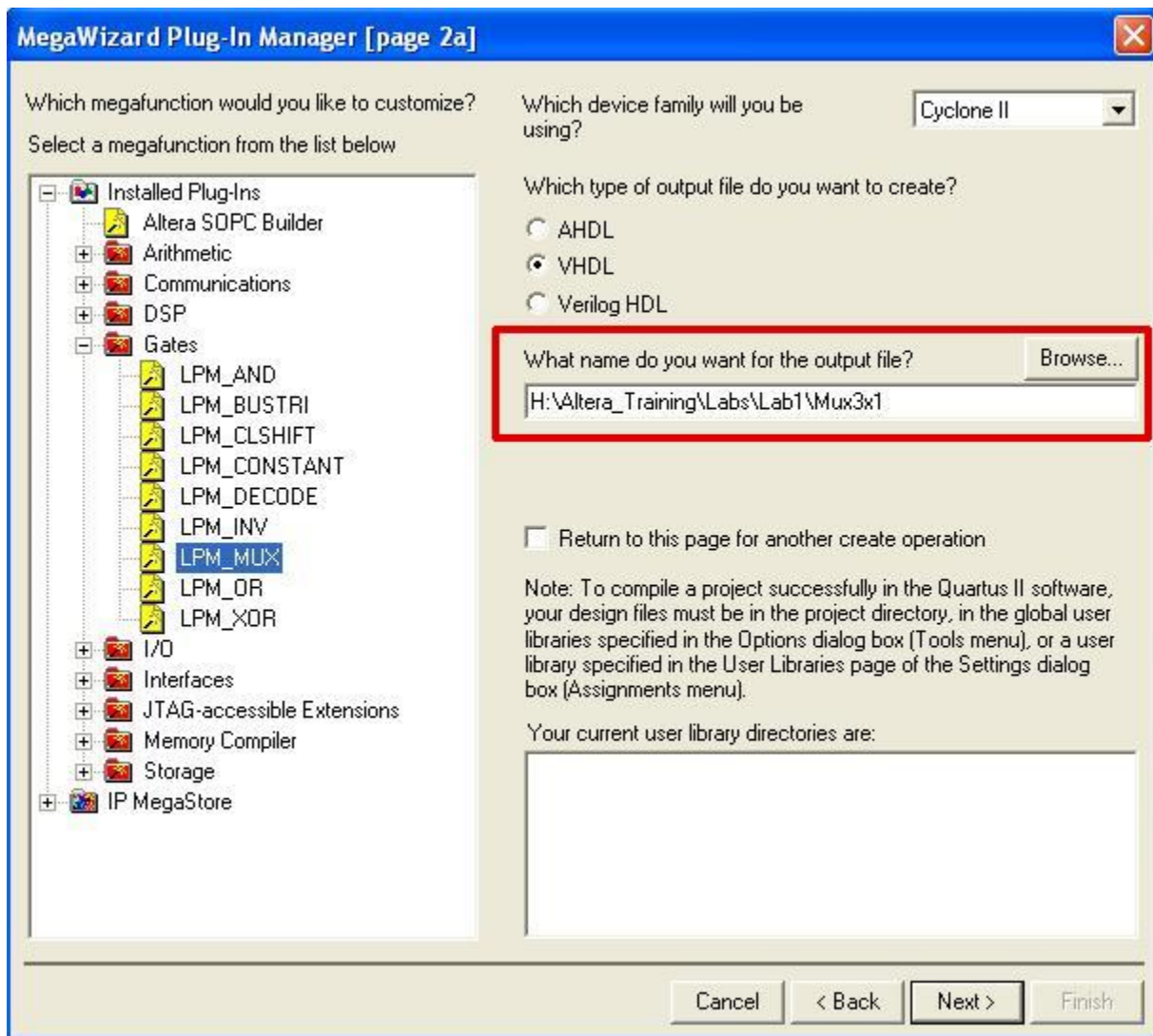4. From the **Gates** menu, select the **LPM\_MUX** subitem and name the file **Mux3x1** and click **Next**.



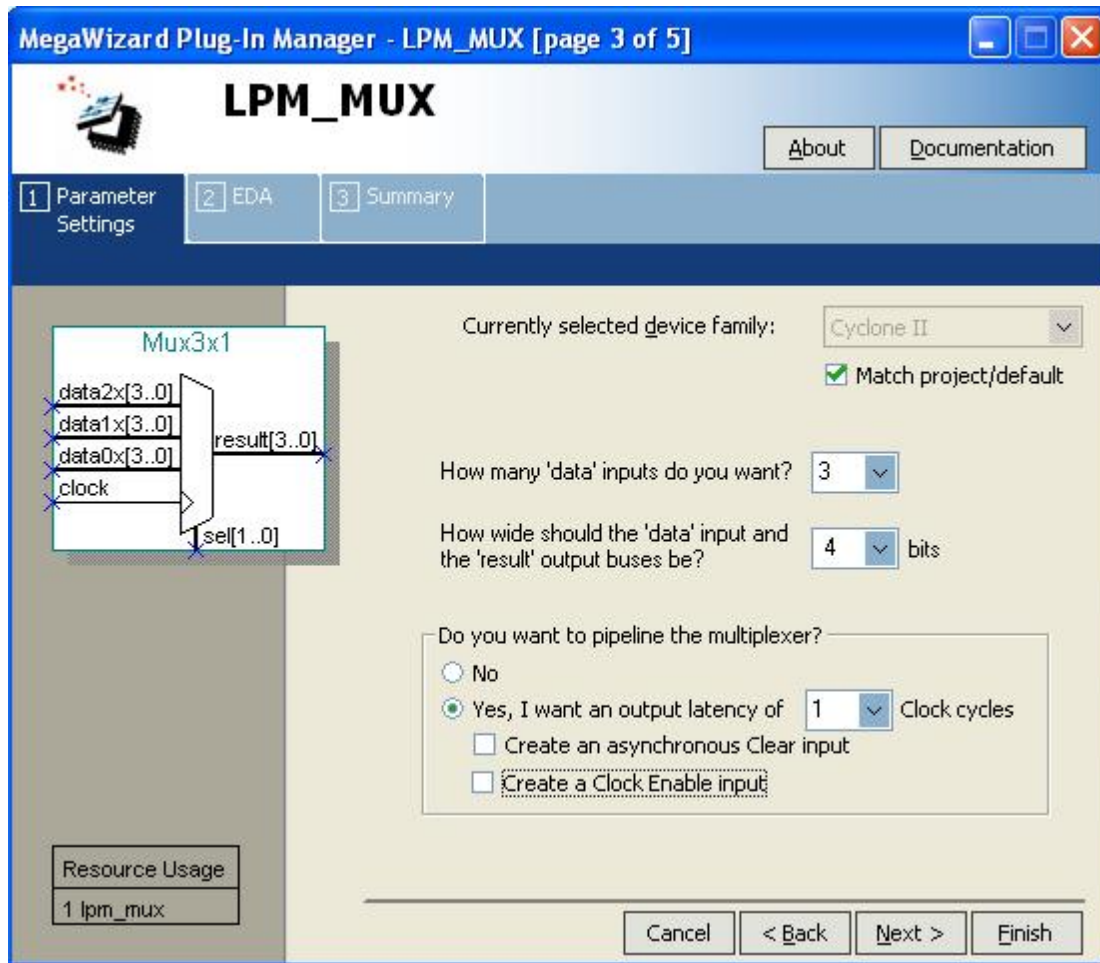
5. Select **3** for the number of data inputs from the drop-down box.  
Select **4** bits for the width of the data input and result output buses from the drop-down box.  
Under **Do you want to pipeline the multiplexer?** Select **Yes** and set the output latency to **1** clock cycle.  
Click **Next**.



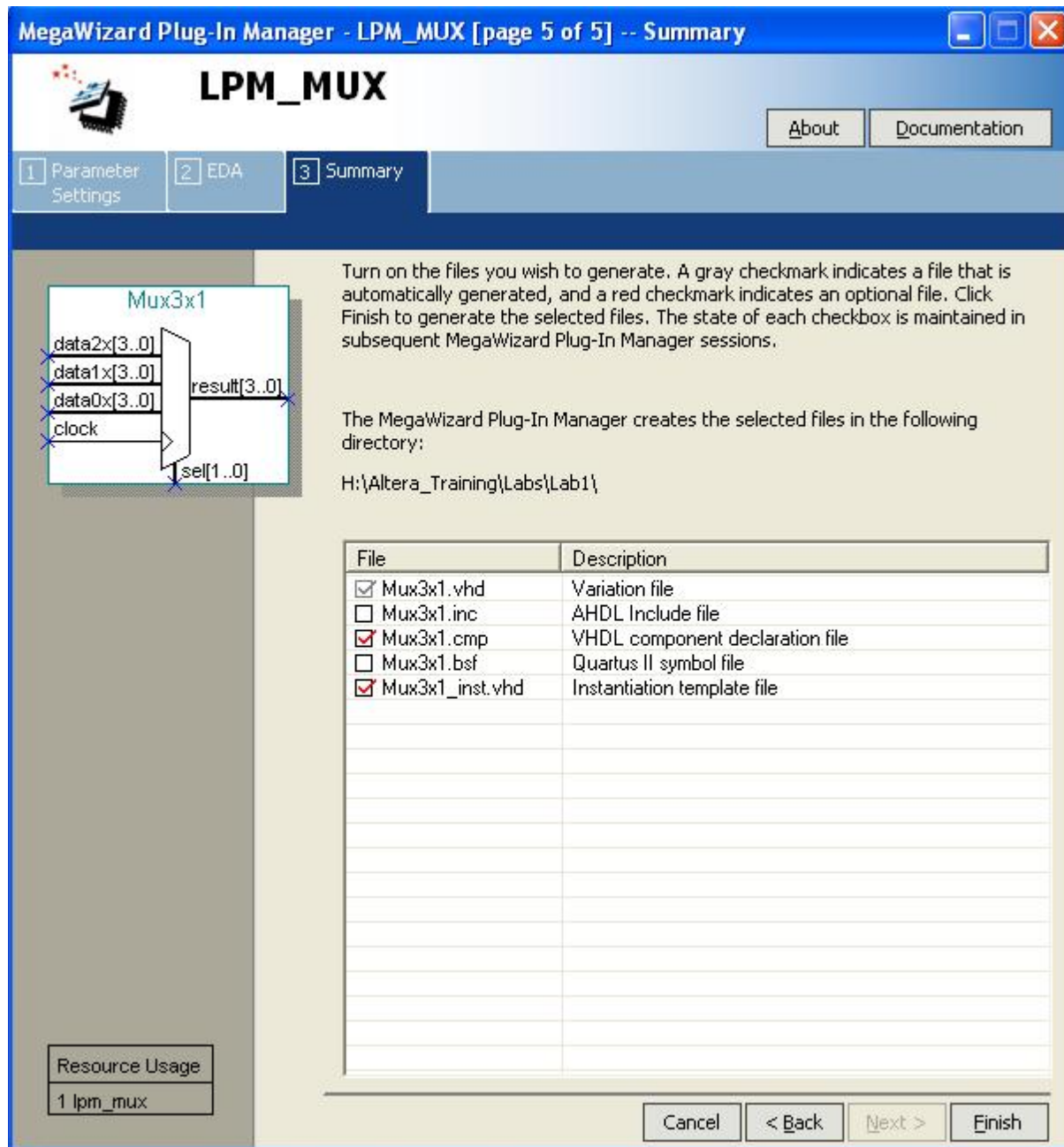6. On page 4 of the MegaWizard Plug-In Manager, click **Next**.


- Verify that **Mux3x1.vhd**, **Mux3x1.cmp**, and **Mux3x1\_inst.vhd** are selected to be created and click **Finish**.

A dialog box may appear about the creation of a Quartus II Ip File. If so, simply click **Yes**.



- ## 8. Compile the Design.


To perform a full compilation select: **Processing** → **Start Compilation**

Alternatively, select the Start Compilation button on the toolbar 

You may ignore any warnings that may appear at this time.

## Task 3: Assign Pins

 
1. From the Menu Bar select: **Assignments** → **Assignment Editor**
2. From the drop-down menu at the top, for **Category**, select **Pin**.



3. Double-click <<new>> in the **To** column and select **input0(0)**. Double-click the adjacent cell under **Location** and type **PIN\_AF14**. Continue to assign the pins as seen in the table below.

|    | To         | Location | DE2 Board Description |
|----|------------|----------|-----------------------|
| 1  | input0(0)  | PIN_AF14 | SW4                   |
| 2  | input0(1)  | PIN_AD13 | SW5                   |
| 3  | input0(2)  | PIN_AC13 | SW6                   |
| 4  | input0(3)  | PIN_C13  | SW7                   |
| 5  | input1(0)  | PIN_A13  | SW9                   |
| 6  | iInput1(1) | PIN_N1   | SW10                  |
| 7  | input1(2)  | PIN_P1   | SW11                  |
| 8  | input1(3)  | PIN_P2   | SW12                  |
| 9  | input2(0)  | PIN_U3   | SW14                  |
| 10 | input2(1)  | PIN_U4   | SW15                  |
| 11 | input2(2)  | PIN_V1   | SW16                  |
| 12 | input2(3)  | PIN_V2   | SW17                  |
| 13 | sel(0)     | PIN_N25  | SW0                   |
| 14 | sel(1)     | PIN_N26  | SW1                   |
| 15 | output(0)  | PIN_AE22 | LEDG0                 |
| 16 | output(1)  | PIN_AF22 | LEDG1                 |
| 17 | output(2)  | PIN_W19  | LEDG2                 |
| 18 | output(3)  | PIN_V18  | LEDG3                 |
| 19 | Clk        | PIN_N2   | 50MHz On Board Clock  |

*Note: A complete list of pin assignments for the DE2 Development Board can be found here:*  
[http://www.terasic.com.tw/attachment/archive/30/DE2\\_Pin\\_Table.pdf](http://www.terasic.com.tw/attachment/archive/30/DE2_Pin_Table.pdf)


4. Save the pin assignments by selecting **File** → **Save** from the Menu Bar, or by clicking the Save button  on the toolbar.
5. **View the Pin Assignments**  
 Select **Assignments** → **Pin Planner** to open the Pin Planner window. Here you can view which pins have been assigned.

6. Select **View → Pin Legend Window** to display the pin legend.  
Close the **Pin Planner**.
7. **Export Pin Assignments**  
With the **Assignment Editor** selected, select **Assignments → Export Assignments** to create a .qsf file containing your pin assignments. This .qsf file can be used for other projects by selecting **Assignments → Import Assignments** when assigning pins.


---

## Task 4: Using the TimeQuest Timing Analyzer

 
1. Select **Assignments → Settings**  
Click the **Timing Analysis Settings** and verify that **Use TimeQuest Timing Analyzer during compilation** is selected for **Timing analysis processing**.  
Click **OK**.



2. **Synthesize the Design**


Select the **Start Analysis & Synthesis** button from the Toolbar   
Click **OK** to continue when the analysis and synthesis is complete.

3. **Open the TimeQuest Timing Analyzer**

Select **Tools → TimeQuest Timing Analyzer**, or use the Toolbar button   
Click **No** when the dialog box pops up asking if you would like to generate an SDC file from the Quartus Settings File.
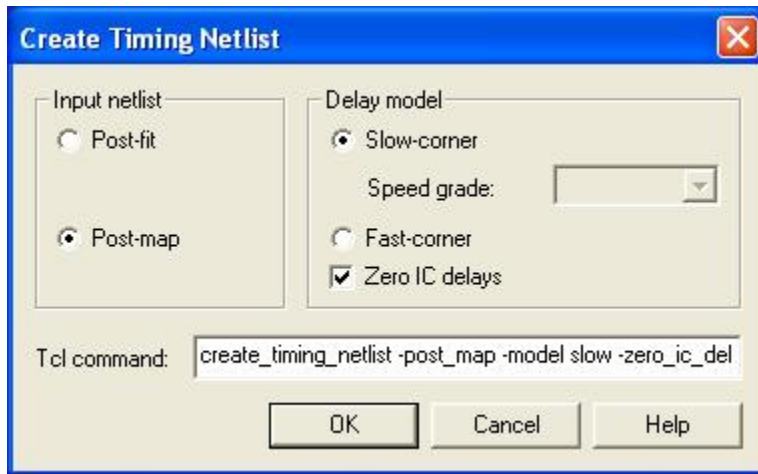
#### 4. Create a Timing Netlist


In the TimeQuest Timing Analyzer window, select **Netlist** → **Create Timing Netlist**.  
Set the **Input netlist type** to **Post-map** and click **OK**.




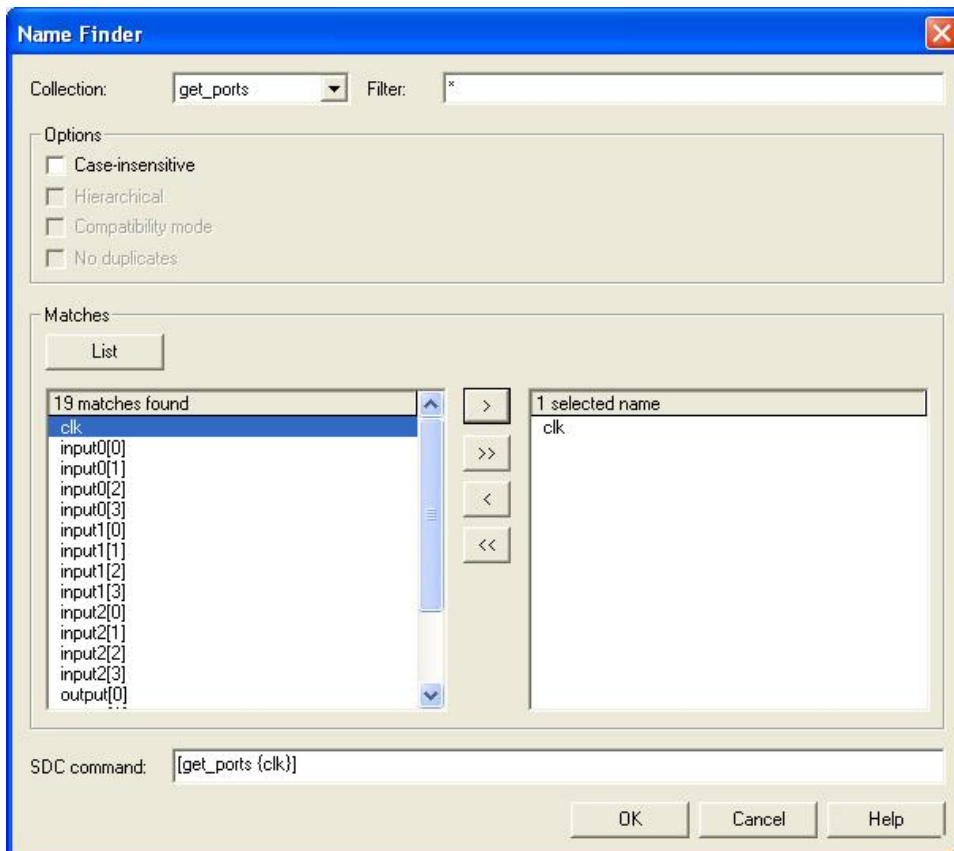
#### 5. Select **Constraints** → **Create Clock...** from the Menu Bar.

Type **clk** for the **Clock name**, and a **Period of 20 ns**.

Double Click **Read SDC File** in the **Tasks** window to read in an SDC file.

Click the ellipses  to select the **Targets**, which opens up the **Name Finder** window.  
Click **List** in the **Matches** field and select **clk**.


Click the single right arrow  to add it to the list of selected names and then click **OK**.  
Click **Run** in the **Create Clock** dialog box to create the clock.




6. Select **Constraints** → **Set Input Delay...** from the Menu Bar.

For **Clock name**: select **clk**.


Make a **Delay value** of **20 ns**.

Click the ellipsis  to select the **Targets**.

Click **List** in the **Matches** field and select all of the **input** and **sel** names.

Click the single right arrow  to add them to the list of selected names and then click **OK**.

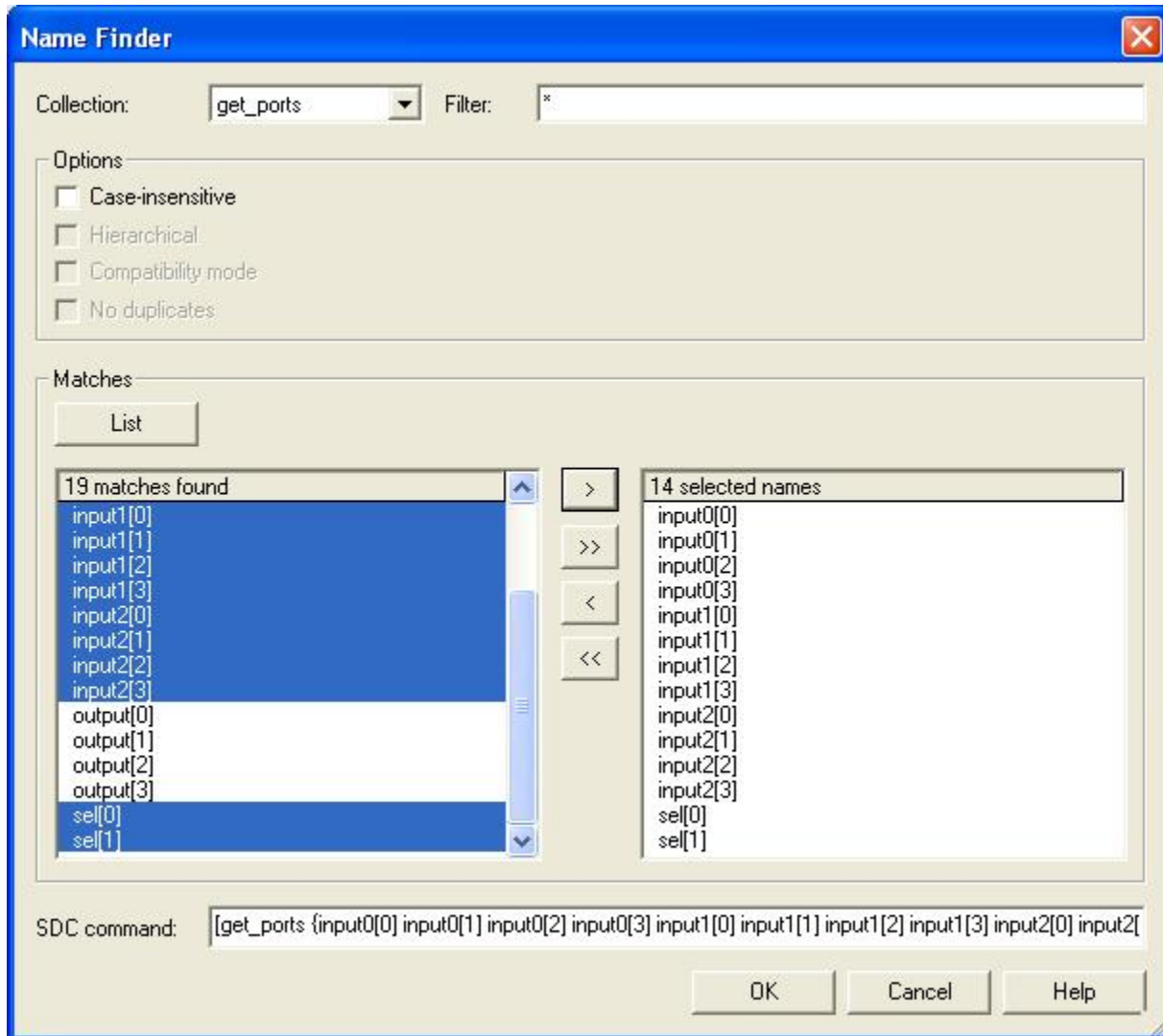Click **Run** in the Set Input Delay window to create the input timing constraints.




7. Select **Constraints** → **Set Output Delay...** from the Menu Bar.

For **Clock name**: select **clk**.


Make a **Delay value** of **20 ns**.

8. Click the ellipses  to select the **Targets**.

Click **List** in the **Matches** field and select all of the **output** names.

Click the single right arrow  to add it to the list of selected names and then click **OK**.

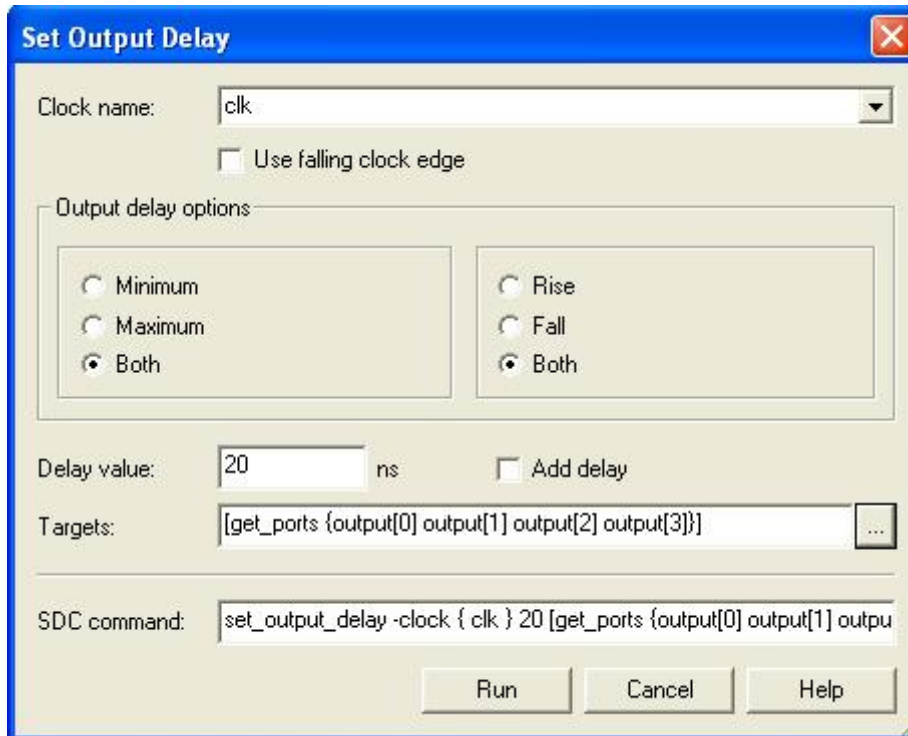Click **Run** in the **Set Input Delay** window to create the output timing constraints.




9. Select **Constraints** → **Write SDC File** from the Menu Bar to save the SDC file.

Click **Save** in the **Save As** dialog box.

10. Close the TimeQuest Timing Analyzer.
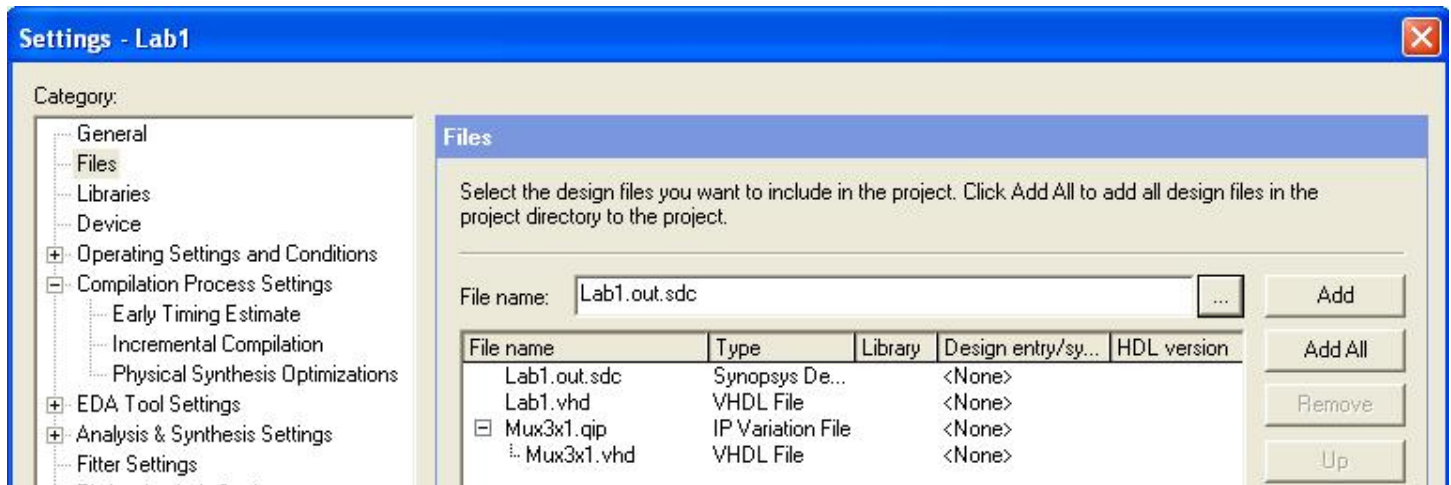
## 11. Add the SDC File to Your Project

In the Quartus II window, select **Project** → **Add/Remove Files in Project...** from the Menu Bar. Click the ellipses next to **File name:** in the **Settings** window that popped up. Select **Script Files** in the drop-down box for **Files of type** in the **Select File** window. Select the **Lab1.out.sdc** file and click **Open**. Click **Add** and then **OK** in the **Settings** window.




12. Compile your design by clicking the Start Compilation button on the toolbar




13. Click the **Critical Warning** tab in the **Messages** window to see that the timing requirements have not been met. This is because of the long input and output delays specified.

 14. Expand the **TimeQuest Timing Analyzer** category in the **Compilation** Report and note that the **Slow Model**, **Fast Model**, and **Multicorner Timing Analysis Summary** reports are in red, indicating that they have failed the timing analysis. Expanding each of the red submenus will show the failures in more detail.



 15. In the **Files** section of the **Project Navigator**, double-click on **Lab1.out.sdc** to directly edit the SDC file.





16. Scroll down in the **Lab1.out.sdc** file to find the **Set Input Delay** and **Set Output Delay** sections. These should be starting on lines 63 and 83 for this example. For each input line that reads similar to:

```
set_input_delay -add_delay -clock [get_clocks {clk}] 20.000 [get_ports {input0[0]}]
```

Change the **20.000** ns delay to **2.000** ns. Repeat this process for all the input and delays.

```
62 # *****
63 # Set Input Delay
64 # *****
65
66 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {input0[0]}]
67 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {input0[1]}]
68 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {input0[2]}]
69 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {input0[3]}]
70 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {input1[0]}]
71 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {input1[1]}]
72 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {input1[2]}]
73 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {input1[3]}]
74 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {input2[0]}]
75 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {input2[1]}]
76 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {input2[2]}]
77 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {input2[3]}]
78 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {sel[0]}]
79 set_input_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {sel[1]}]
80
81
82 # *****
83 # Set Output Delay
84 # *****
85
86 set_output_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {output[0]}]
87 set_output_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {output[1]}]
88 set_output_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {output[2]}]
89 set_output_delay -add_delay -clock [get_clocks {clk}] 2.000 [get_ports {output[3]}]
```

Save the Lab1.out.sdc file by clicking on the **Save** button on the Menu Bar 

17. Compile the design again by clicking the Start Compilation button on the toolbar  and check the TimeQuest Timing Analyzer reports again to see that the design has now passed the timing analysis. Ignore any warnings at this time.

## Task 5: Program the DE2 Development Board

1. On the Altera DE2 Development board, plug the USB Cable into the **USB Blaster Port**. Plug the other end of the USB Cable into the computer.  
Plug the 9v power supply into the **9V DC Power Supply Connector** on the DE2 board, and plug the other end into a 120v wall socket.  
Press the **Power ON/OFF Switch** to power on the DE2 board.  
Make sure that the **RUN/PROG Switch for JTAG/AS Modes** is in the **RUN** position.

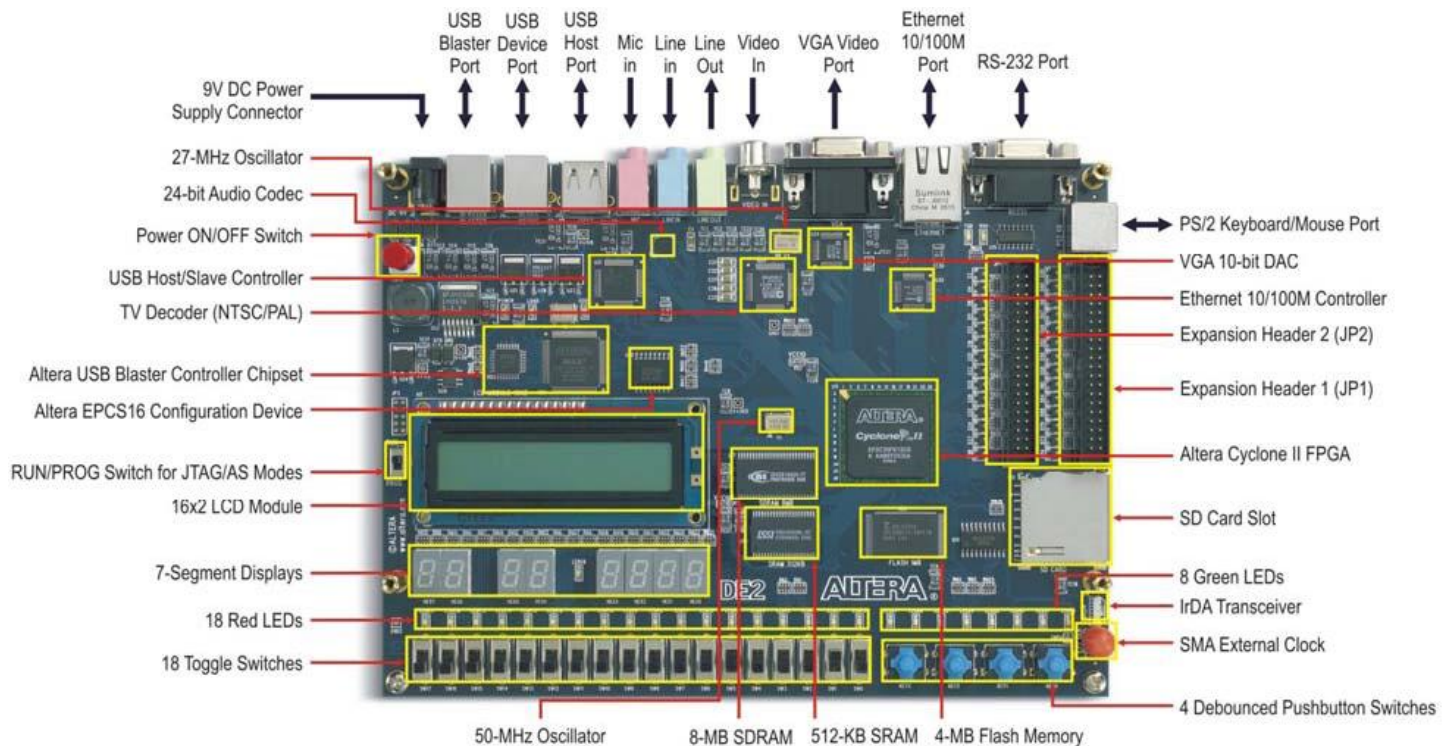

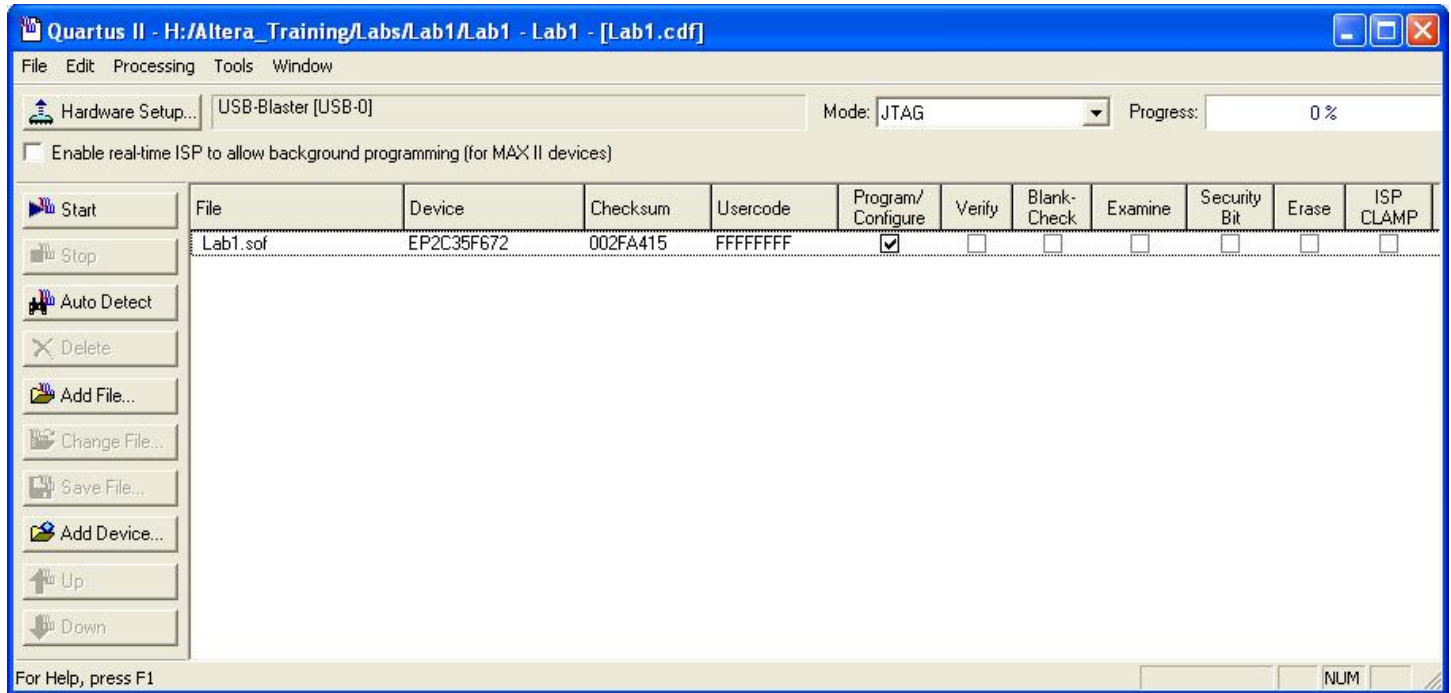


Image Source: DE2 Development and Education Board User Manual version 1.42 , Altera Corporation, 2008

- In the Quartus II window click the **Programmer** button on the Toolbar to open the Programmer window   
The **Hardware Setup...** must be **USB-Blaster [USB-0]**. If not, click the **Hardware Setup...** button and select **USB-Blaster [USB-0]** from the drop-down menu for **Currently selected hardware**. **Mode** should be set to **JTAG**.  
Make sure that the **File** is **Lab1.sof**, **Device** is **EP2C35F672**, and the **Program/Configure** box is checked.



Then click the **Start** button to program the DE2 board.  
When the progress bar reaches 100%, programming is complete.

- You can now test the program on the DE2 board by using the toggle switches located along the bottom of the board.  
SW0 and SW1 are the selector inputs to the multiplexer.  
SW4 through SW7 are the four bits of data for input0.  
SW9 through SW11 are the four bits of data for input1.  
SW13 through SW17 are the four bits of data for input2.  
The output of the multiplexer is displayed on the first four green LEDs located above the blue push buttons on the DE2 board. Their pattern will correspond to the four bits of the selected data stream.


# Lab 2

---


## Introduction to VHDL
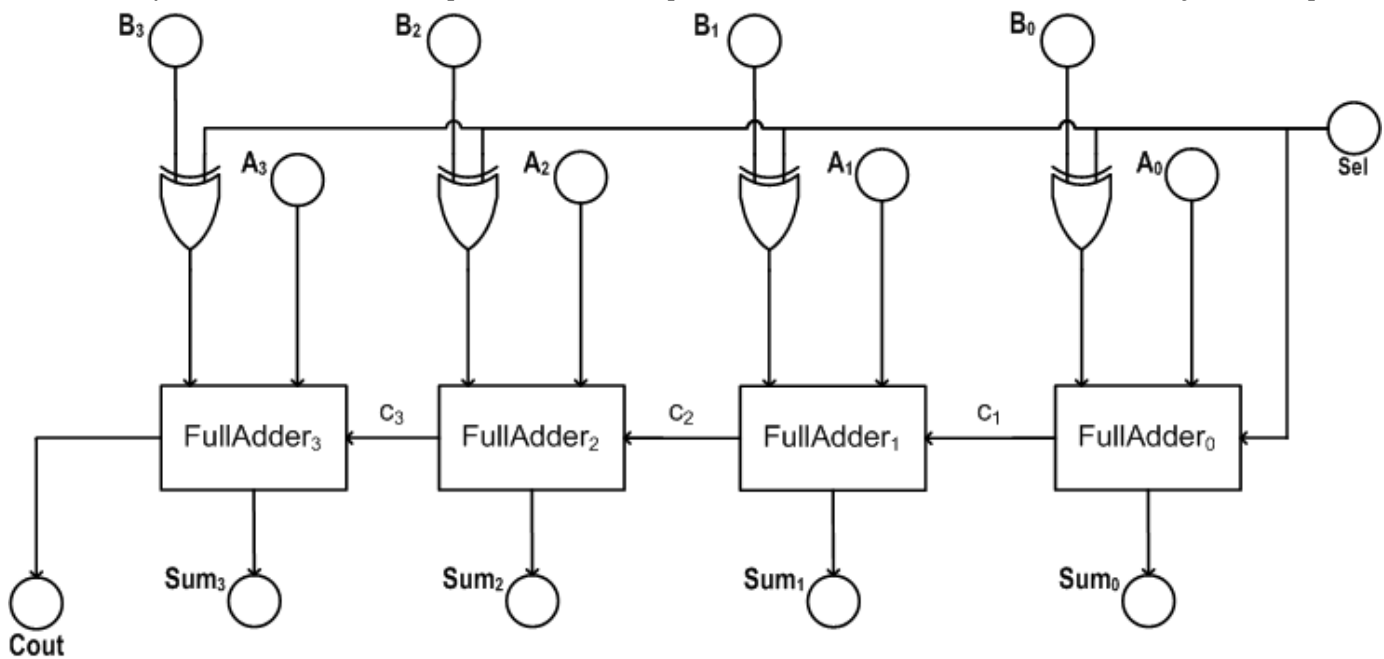
## Lab 2 – Introduction to VHDL

In this lab you will design, test, and simulate a basic logic circuit using the Quartus II development software. The circuit you will create is a ripple-carry four-bit adder/subtractor using both behavioral and structural VHDL coding. Below is a schematic diagram of the complete circuit. The component make-up includes four full adders and four XOR logic gates. The inputs are two four-bit numbers; A and B, and an add/subtract selection input; Sel. The outputs are four-bit sum; Sum, and a carry-out output; Cout.



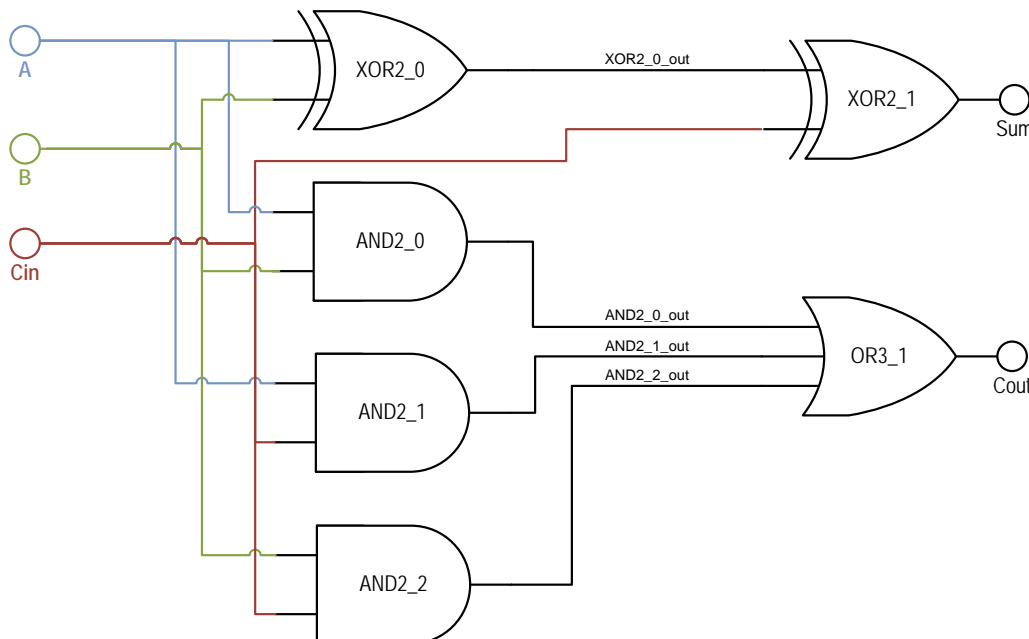Below is a detailed diagram of the full adder circuit used. It consists of three two-input AND gates, two XOR gates, and one three-input OR gate. The individual gates will be coded separately using behavioral style VHDL, and then stitched together using structural style VHDL to create the full adder.



## Task 1: Create a New Project

### 1. Start the Quartus II software.

From the Windows Start Menu, select:

**All Programs → Other Apps → Altera → Quartus II 9.1 → Quartus II 9.1 (32-Bit)**

### 2. Start the New Project Wizard.


If the opening splash screen is displayed, select: **Create a New Project (New Project Wizard)**, otherwise from the Quartus II Menu Bar select: **File → New Project Wizard**.

### 3. Select the Working Directory and Project Name.

|                         |                         |
|-------------------------|-------------------------|
| Working Directory       | H:\Altera_Training\Lab2 |
| Project Name            | Lab2                    |
| Top-Level Design Entity | Lab2                    |

Click **Next** to advance to page 2 of the New Project Wizard.

 *Note: A window may pop up stating that the chosen working directory does not exist. Click **Yes** to create it.*



The screenshot shows the 'New Project Wizard: Directory, Name, Top-Level Entity [page 1 of 5]' dialog box. It contains three text input fields with browse buttons (three dots) to the right. The first field is labeled 'What is the working directory for this project?' and contains the text 'H:\Altera\_Training\Lab2'. The second field is labeled 'What is the name of this project?' and contains the text 'Lab2'. The third field is labeled 'What is the name of the top-level design entity for this project? This name is case sensitive and must exactly match the entity name in the design file.' and contains the text 'Lab2'. Below these fields is a button labeled 'Use Existing Project Settings ...'. At the bottom of the dialog are four buttons: '< Back', 'Next >', 'Finish', and 'Cancel'.

4. Click **Next** again as we will not be adding any preexisting design files at this time.
5. **Select the family and Device Settings.**  
 From the pull-down menu labeled **Family**, select **Cyclone II**.  
 In the list of available devices, select **EPC235F672C6**.  
 Click **Next**.

**New Project Wizard: Family & Device Settings [page 3 of 5]**

Select the family and device you want to target for compilation.

Device family:  
 Family: **Cyclone II**  
 Devices: **All**

Target device:  
☐ Auto device selected by the Fitter  
☒ Specific device selected in 'Available devices' list

Show in 'Available device' list:  
 Package: **Any**  
 Pin count: **Any**  
 Speed grade: **Any**  
☒ Show advanced devices  
☐ HardCopy compatible only

Available devices:


| Name                | Core voltage | LEs          | User I/... | Memor...      | Embed...  |
|---------------------|--------------|--------------|------------|---------------|-----------|
| EP2C20Q240C8        | 1.2V         | 18752        | 142        | 239616        | 52        |
| EP2C35F484C6        | 1.2V         | 33216        | 322        | 483840        | 70        |
| EP2C35F484C7        | 1.2V         | 33216        | 322        | 483840        | 70        |
| EP2C35F484C8        | 1.2V         | 33216        | 322        | 483840        | 70        |
| EP2C35F484I8        | 1.2V         | 33216        | 322        | 483840        | 70        |
| <b>EP2C35F672C6</b> | <b>1.2V</b>  | <b>33216</b> | <b>475</b> | <b>483840</b> | <b>70</b> |
| EP2C35F672C7        | 1.2V         | 33216        | 475        | 483840        | 70        |
| EP2C35F672C8        | 1.2V         | 33216        | 475        | 483840        | 70        |
| EP2C35F672I8        | 1.2V         | 33216        | 475        | 483840        | 70        |

Companion device:  
 HardCopy:   
☒ Limit DSP & RAM to HardCopy device resources

< Back   **Next >**   Finish   Cancel

6. Click **Next** again as we will not be using any third party EDA tools.

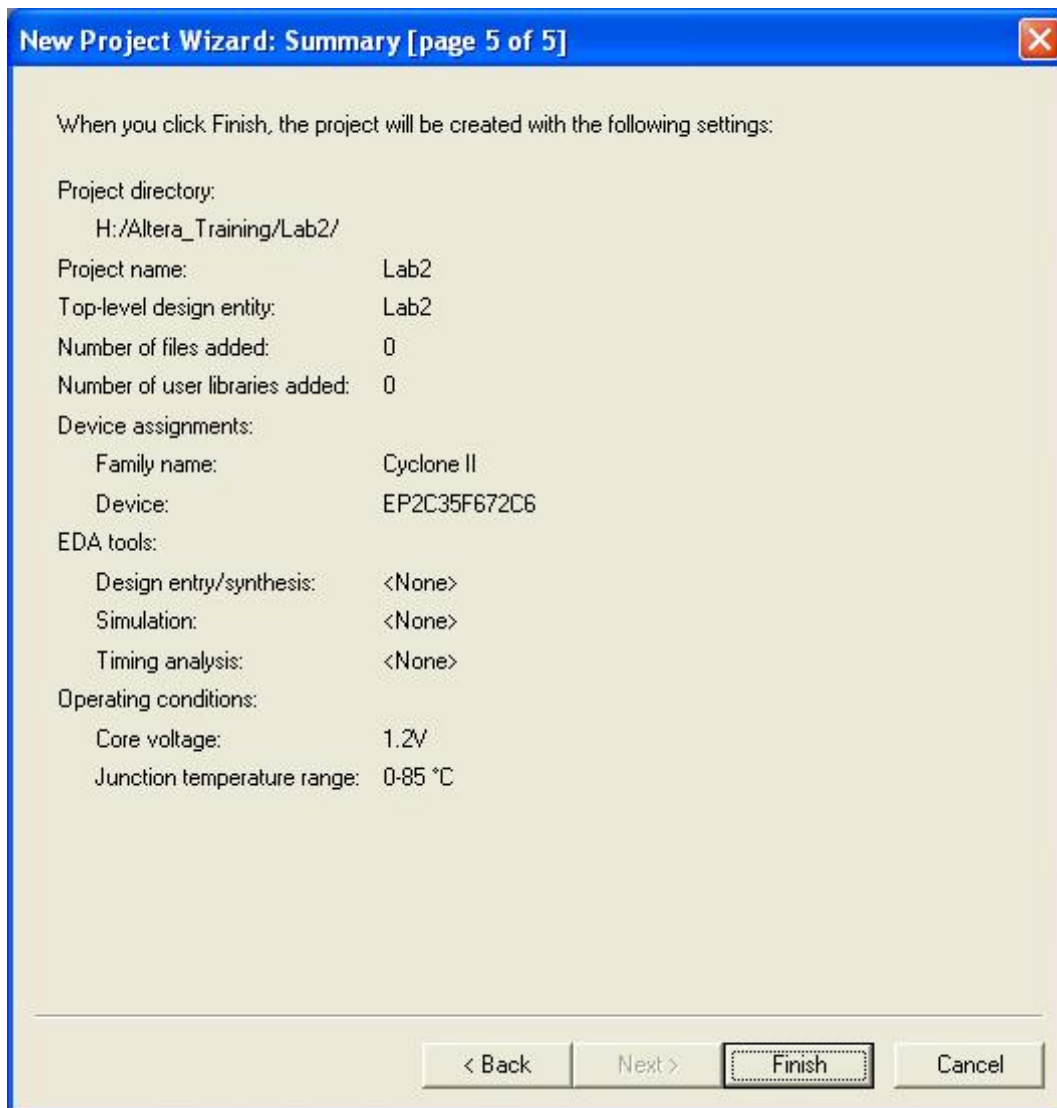7. Click **Finish** to complete the New Project Wizard.




---

## Task 2: Create, Add, and Compile Design Files
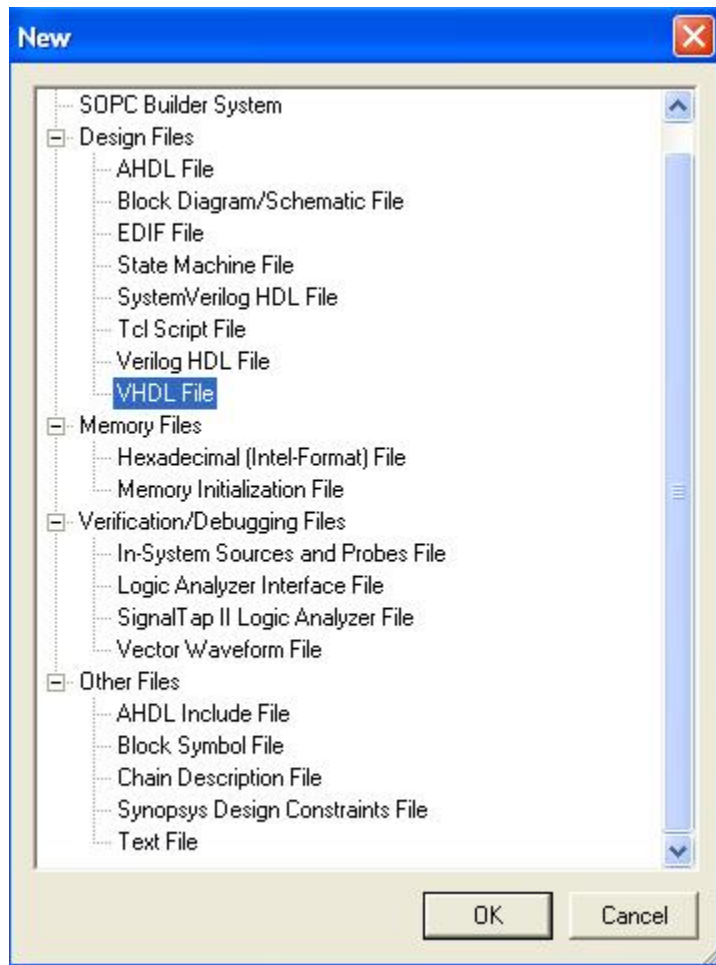
### 1. Create a new Design File.

Select: **File** → **New** from the Menu Bar.

Select: **VHDL File** from the **Design Files** list and click **OK**.



2. Copy and paste the following code into your new VHDL file, then save it by selecting **File** → **Save**. Name the file **And2** and click **Save** in the **Save As** dialog box.

| Lab 2 – Introduction to VHDL – Two-Input AND Gate Behavioral VHDL Code                                                                                                                                                                                                                                                  |
|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <pre>LIBRARY ieee; USE ieee.std_logic_1164.ALL;  ENTITY Gate_And2 IS     PORT (x: IN std_logic;           y: IN std_logic;           F: OUT std_logic); END Gate_And2;  ARCHITECTURE Gate_And2_beh OF Gate_And2 IS BEGIN     PROCESS(x, y)     BEGIN         F &lt;= x AND y;     END PROCESS; END Gate_And2_beh;</pre> |

This is a basic two-input AND Gate, written using Behavioral style VHDL. The AND gate has two inputs, **x** and **y**, which are ANDed together and the result of the logic operation is returned on **F**. The **Process** sensitivity list includes **x** and **y**, so whenever either of the two change in value the process will execute and generate a new result.

3. Create another new VHDL file following the directions in step 1 of task 2.
4. Copy and paste the following code into your new VHDL file, then save it by selecting **File** → **Save**. Name the file **Xor2** and click **Save** in the **Save As** dialog box.

| Lab 2 – Introduction to VHDL – Two-Input XOR Gate Behavioral VHDL Code                                                                                                                                                                                                                                                  |
|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <pre>LIBRARY ieee; USE ieee.std_logic_1164.ALL;  ENTITY Gate_XOR2 IS     PORT (x: IN std_logic;           y: IN std_logic;           F: OUT std_logic); END Gate_XOR2;  ARCHITECTURE Gate_XOR2_beh OF Gate_XOR2 IS BEGIN     PROCESS(x, y)     BEGIN         F &lt;= x XOR y;     END PROCESS; END Gate_XOR2_beh;</pre> |

This is a basic XOR Gate, written using Behavioral style VHDL. Similar to the AND gate we created, the XOR gate has two inputs, **x** and **y**, which are XORed together and the result of the logic operation is returned on **F**. The **Process** sensitivity list includes **x** and **y**, so whenever either of the two change in value the process will execute and generate a new result.

5. Create another new VHDL file following the directions in step 1 of task 2.

6. Copy and paste the following code into your new VHDL file, then save it by selecting **File** → **Save**. Name the file **Or3** and click **Save** in the **Save As** dialog box. This is a three-input OR Gate, written using Behavioral style VHDL.

| Lab 2 – Introduction to VHDL – Three-Input OR Gate Behavioral VHDL Code                                                                                                                                                                                                                                                                              |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <pre>LIBRARY ieee; USE ieee.std_logic_1164.ALL;  ENTITY Gate_OR3 IS     PORT (x: IN std_logic;           y: IN std_logic;           z: IN std_logic;           F: OUT std_logic); END Gate_OR3;  ARCHITECTURE Gate_OR3_beh OF Gate_OR3 IS BEGIN     PROCESS(x, y, z)     BEGIN         F &lt;= x OR y OR z;     END PROCESS; END Gate_OR3_beh;</pre> |

This is a three-input OR Gate, written using Behavioral style VHDL. Similar to the AND gate and XOR gate we created, the OR gate has three inputs, **x**, **y**, and **z**, which are ORed together and the result of the logic operation is returned on **F**. The **Process** sensitivity list includes **x**, **y**, and **z**, so whenever one changes in value the process will execute and generate a new result.

7. Create another new VHDL file following the directions in step 1 of task 2.
8. Copy and paste the following code into your new VHDL file, then save it by selecting **File** → **Save**. Name the file **FullAdder** and click **Save** in the **Save As** dialog box.

| Lab 2 – Introduction to VHDL – Full Adder Structural VHDL Code                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      |
|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <pre> LIBRARY ieee; USE ieee.std_logic_1164.ALL;  ENTITY FullAdder IS     PORT (A: IN std_logic;           B: IN std_logic;           Cin: IN std_logic;           Sum: OUT std_logic;           Cout: OUT std_logic); END FullAdder;  ARCHITECTURE FullAdder_struct OF FullAdder IS      COMPONENT Gate_And2 IS         PORT (x, y: IN std_logic;               f: OUT std_logic);     END COMPONENT;      COMPONENT Gate_XOR2 IS         PORT (x, y: IN std_logic;               f: OUT std_logic);     END COMPONENT;      COMPONENT Gate_OR3 IS         PORT (x, y, z: IN std_logic;               f: OUT std_logic);     END COMPONENT;      SIGNAL XOR2_0_out, AND2_0_out, AND2_1_out, AND2_2_out: std_logic;  BEGIN      XOR2_0: Gate_XOR2 PORT MAP(A, B, XOR2_0_out);     XOR2_1: Gate_XOR2 PORT MAP(XOR2_0_out, Cin, Sum);     AND2_0: Gate_AND2 PORT MAP(A, B, AND2_0_out);     AND2_1: Gate_AND2 PORT MAP(A, Cin, AND2_1_out);     AND2_2: Gate_AND2 PORT MAP(B, Cin, AND2_2_out);     OR3_1: Gate_OR3 PORT MAP(AND2_0_out, AND2_1_out, AND2_2_out, Cout);  END FullAdder_struct; </pre> |

This is an example of structural-style VHDL which utilizes the multiple components we previously created and stitches them together to produce the desired result. In this case there are two instances of the XOR gate used, three AND gates used, and one OR gate to create the full adder. The argument list for each component instance is fashioned in a way to produce the desired connections based on the schematic diagram of the adder/subtractor circuit. A **SIGNAL** declaration is used to define the connections that are internal to the circuit. These signals carry the signal from one component to another.


9. Create another new VHDL file following the directions in step 1 of task 2.
10. Copy and paste the following code into your new VHDL file, then save it by selecting **File** → **Save**. Name the file **Lab2** and click **Save** in the **Save As** dialog box. This is the Full Adder circuit, written using Structural style VHDL.

| Lab 2 - Introduction to VHDL - Adder/Subtractor Structural VHDL Code                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                     |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <pre> LIBRARY ieee; USE ieee.std_logic_1164.ALL;  ENTITY Lab2 IS     PORT (A: IN std_logic_vector(3 DOWNTO 0);           B: IN std_logic_vector(3 DOWNTO 0);           Sel: IN std_logic;           Sum: OUT std_logic_vector(3 DOWNTO 0);           Cout: OUT std_logic); END Lab2;  ARCHITECTURE AddSub_struct OF Lab2 IS      COMPONENT Gate_XOR2 IS         PORT (x, y: IN std_logic;               f: OUT std_logic);     END COMPONENT;      COMPONENT FullAdder IS         PORT (A: IN std_logic;               B: IN std_logic;               Cin: IN std_logic;               Sum: OUT std_logic;               Cout: OUT std_logic);     END COMPONENT;      SIGNAL XOR2_0_out, XOR2_1_out, XOR2_2_out, XOR2_3_out: std_logic;     SIGNAL c1, c2, c3: std_logic;  BEGIN      XOR2_0: Gate_XOR2 PORT MAP(B(0), Sel, XOR2_0_out);     XOR2_1: Gate_XOR2 PORT MAP(B(1), Sel, XOR2_1_out);     XOR2_2: Gate_XOR2 PORT MAP(B(2), Sel, XOR2_2_out);     XOR2_3: Gate_XOR2 PORT MAP(B(3), Sel, XOR2_3_out);     FullAdder_0: FullAdder PORT MAP(A(0), XOR2_0_out, Sel, Sum(0), c1);     FullAdder_1: FullAdder PORT MAP(A(1), XOR2_1_out, c1, Sum(1), c2);     FullAdder_2: FullAdder PORT MAP(A(2), XOR2_2_out, c2, Sum(2), c3);     FullAdder_3: FullAdder PORT MAP(A(3), XOR2_3_out, c3, Sum(3), Cout);  END AddSub_struct; </pre> |


11. Compile the design by clicking the **Start Compilation** button  on the Toolbar.

## Task 3: Simulate Design using Quartus II
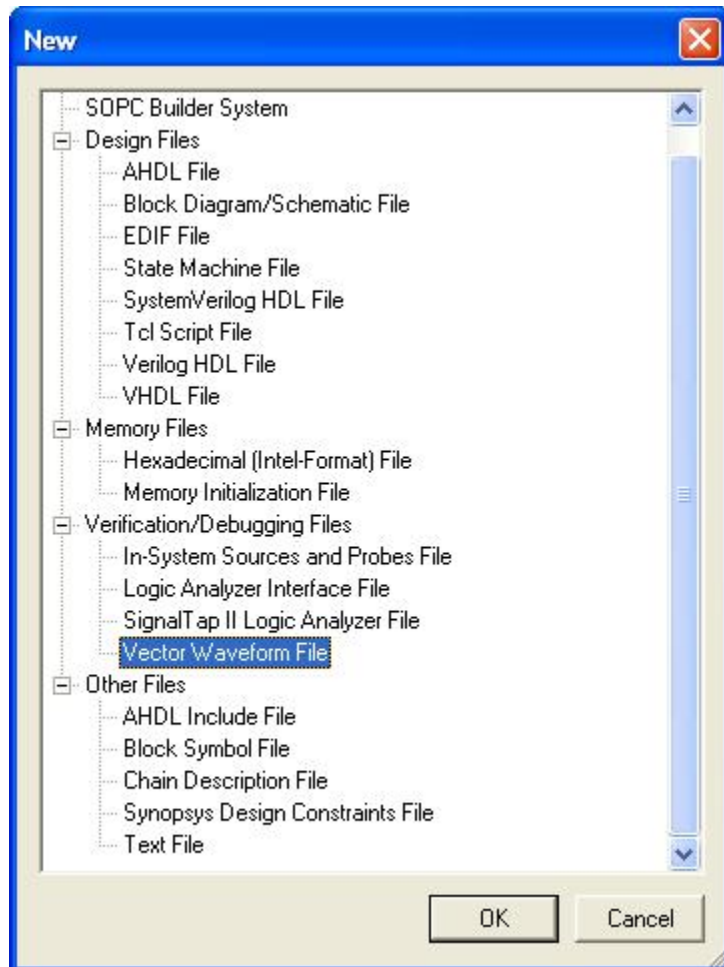
### 1. Create a Vector Waveform File (vwf)


Click the **New File** icon on the Menu Bar 


Select **Vector Waveform File** under the **Verification/Debugging Files** heading.



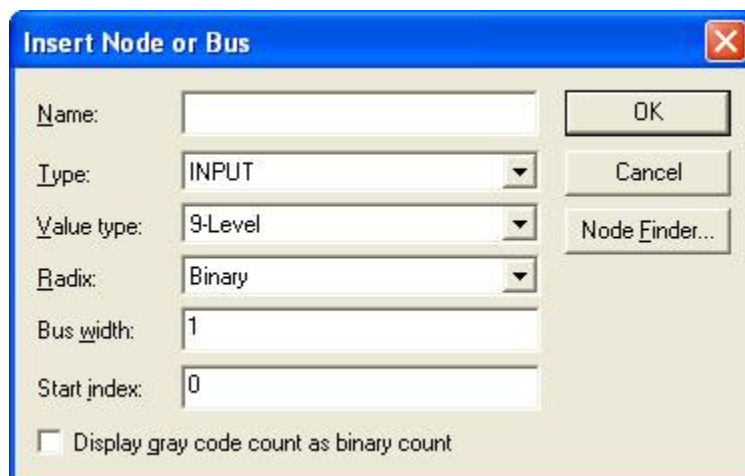
### 2. Add Signals to the Waveform


Select **Edit** → **Insert** → **Insert Node or Bus...** to open the **Insert Node or Bus** window.




- Click the **Node Finder...** button in the **Insert Node or Bus** window to open the **Node Finder** window.  
From the **Filter** drop-down menu, select **Pins: all** and click the **List** button. This will display all the inputs and outputs to the circuit.  
Highlight all the the **Input Groups A**, and **B**, the **Input Sel**, and **Output Group Sum** in the **Nodes Found** window and click the right arrow  to select them.  
Then click **OK** to close the **Node Finder** window.

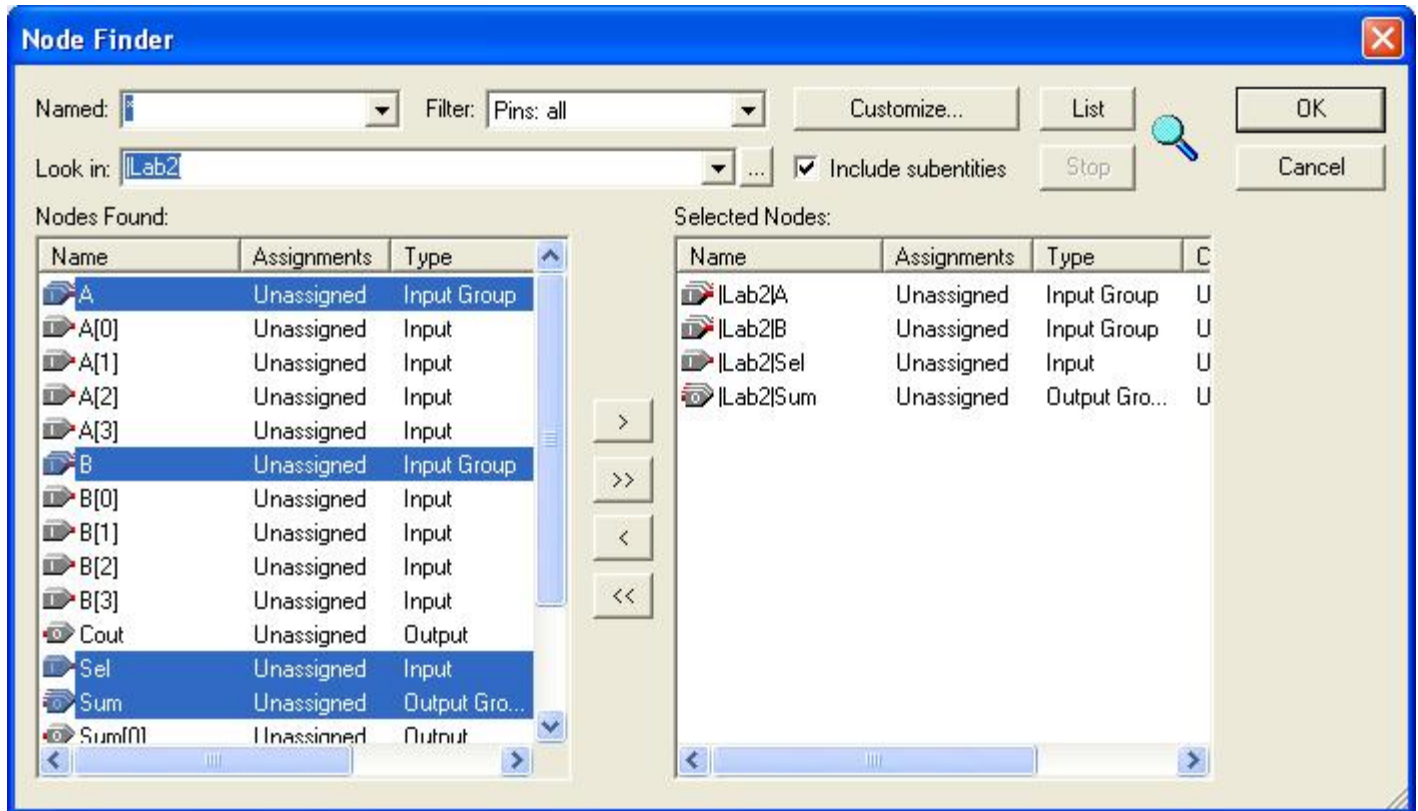

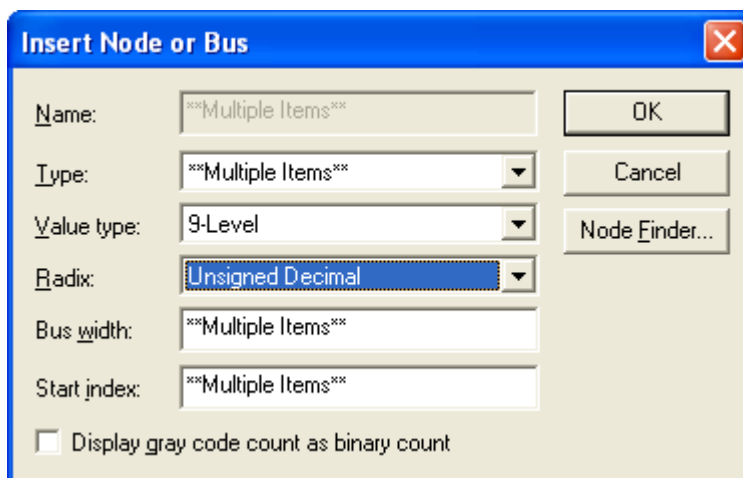- In the **Insert Node or Bus** window, change **Radix** to **Unsigned Decimal**. This will make it easier for us to enter values and interpret the results.



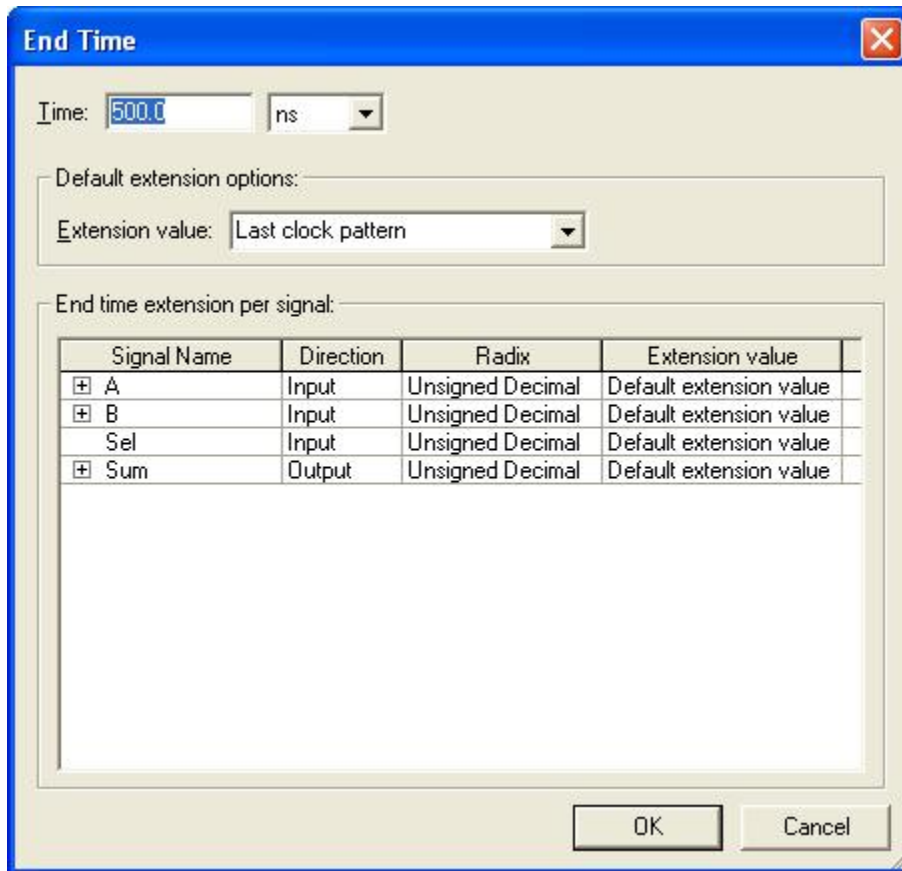5. Select **Edit → End Time...** to open the **End Time** window.  
Change the end time to 500 ns. This is how long the simulated circuit will operate for.  
Click **OK** to exit the **End Time** window.




The **End Time** dialog box has a title bar with a close button. It contains the following fields and controls:

- Time:** A text box containing "500.0" and a dropdown menu set to "ns".
- Default extension options:** A section containing an **Extension value:** dropdown menu set to "Last clock pattern".
- End time extension per signal:** A section containing a table with the following data:
 

| Signal Name | Direction | Radix            | Extension value         |
|-------------|-----------|------------------|-------------------------|
| ⊕ A         | Input     | Unsigned Decimal | Default extension value |
| ⊕ B         | Input     | Unsigned Decimal | Default extension value |
| Sel         | Input     | Unsigned Decimal | Default extension value |
| ⊕ Sum       | Output    | Unsigned Decimal | Default extension value |
- Buttons:** "OK" and "Cancel" buttons at the bottom right.

 6. Click **A** in the **Name** column and press **Ctrl + Alt + B** to open the **Arbitrary Value** window.  
End **40 ns** for the **Start time** and **160 ns** for the **End time**.  
Enter **10** for the **Numeric or named value**.




The **Arbitrary Value** dialog box has a title bar with a close button. It contains the following fields and controls:


- Time range:** A section containing **Start time:** (text box "40", dropdown "ns") and **End time:** (text box "160", dropdown "ns").
- Arbitrary value:** A section containing **Radix:** (dropdown "Unsigned Decimal") and **Numeric or named value:** (dropdown "10").
- Buttons:** "OK" and "Cancel" buttons at the bottom.

Repeat this process for **A** to assign a value of **7** from **160 ns** to **310 ns**.  
Assign **B** the value of **5** from **100 ns** to **230 ns**, and a value of **2** from **230 ns** to **390 ns**.

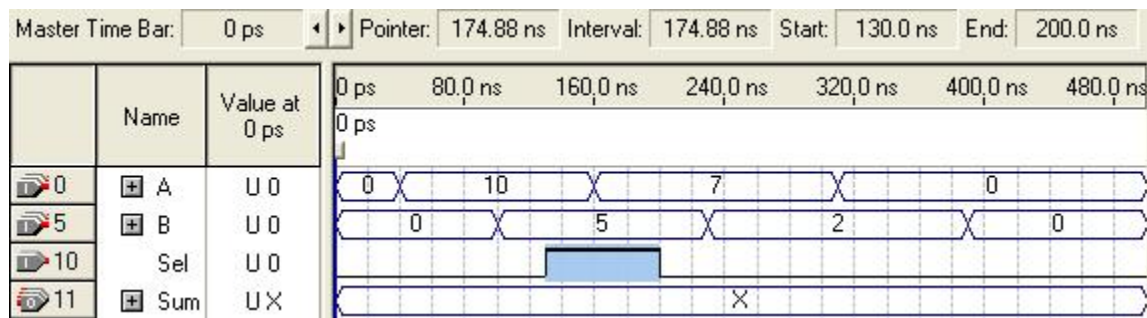
On the waveform row for **Sel**, click and drag to highlight the waveform from **130 ns** to **200 ns**. Press **Ctrl + Alt + 1** to assign this section of the waveform a value of **1**. Repeat this process for the value of **Sel** from **270 ns** to **350 ns**.



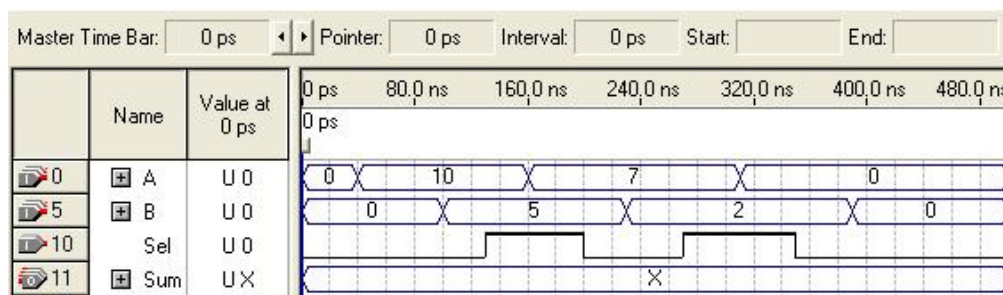
After completing the signal assignments the waveform graph should look similar to the image below:




Leave **Sum** with a value of undefined (X), as values for this will be generated when the simulation runs.


Click the **Save** icon  on the Menu bar and save the vwf file with the filename **Lab2.vwf**.

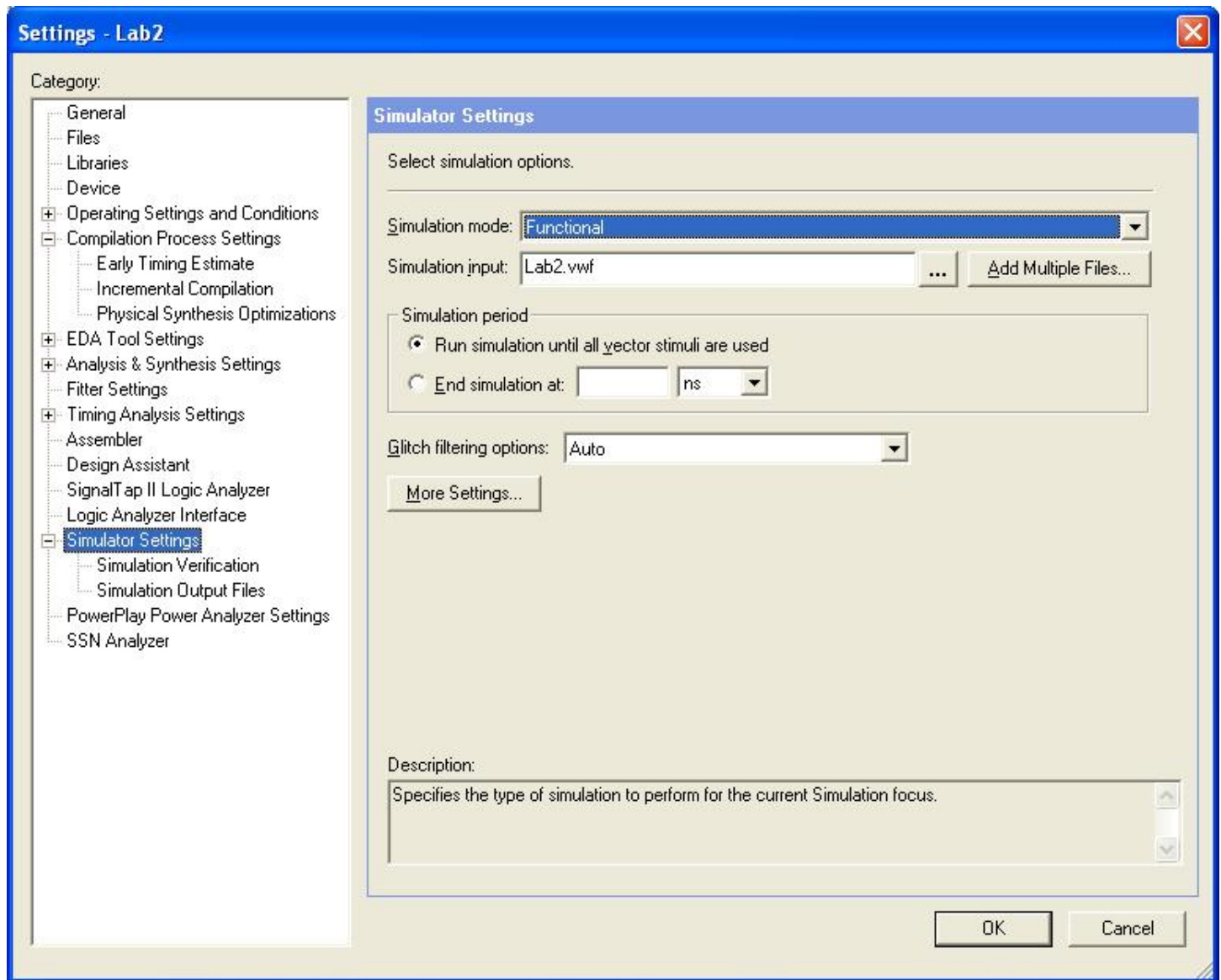7. From the Toolbar, select **Assignments** → **Settings** to open the **Settings** window. Click the **Simulator Settings** heading and set **Simulation Mode** to **Functional**.


**Simulation input** should be the name of your vwf file, **Lab2.vwf**. If not, click the ellipses  and select **Lab2.vwf**.

Click **OK** to save the changes and close the **Settings** window.




8. Click the **Start Compilation** button  on the Menu bar to compile the design. Ignore any warnings generated.

9. Select **Processing** → **Generate Functional Simulation Netlist** and click **OK** when it has completed.

10. Run the simulation by clicking the **Start Simulation** button  on the Toolbar. Click **OK** once the simulator has completed.

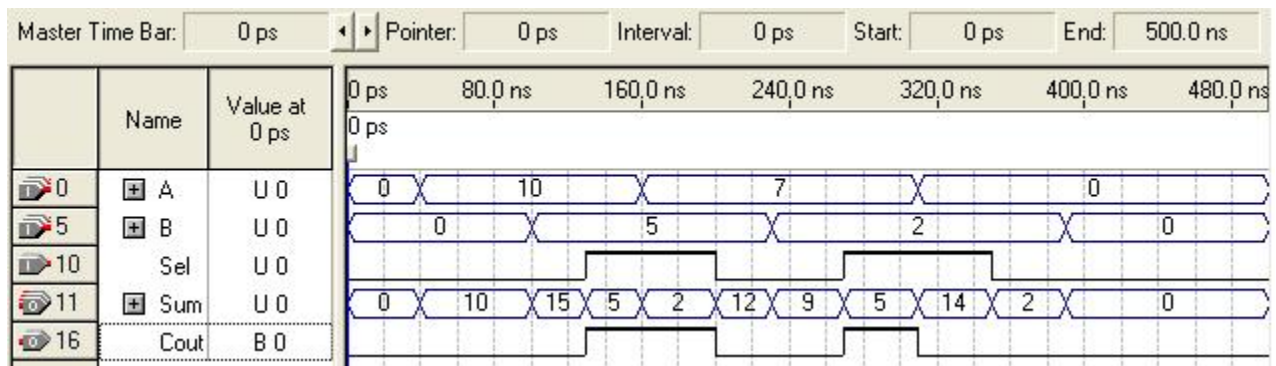11. The output waveforms for **Cout** and **Sum** should look similar to the screen capture below;




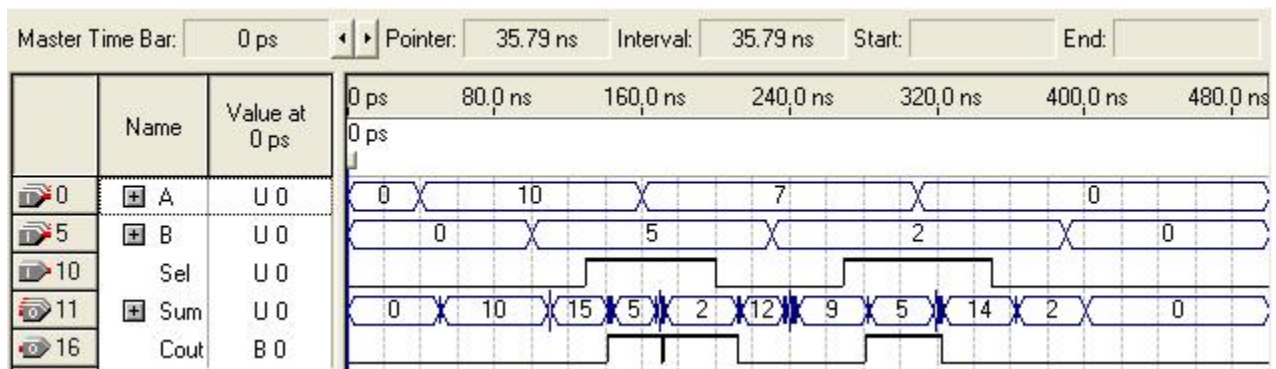
When **Sel** is low, **A** is added to **B** and the result is displayed as the value of **Sum**.

When **Sel** is high, **B** is subtracted from **A** and **Sum** is the result.

12. Change the simulation mode to **Timing** by selecting **Assignments** → **Settings** to open the **Settings** window.

Click the **Simulator Settings** heading and set **Simulation Mode** to **Timing**.

13. Click the **Start Simulation** button  and observe the change in the output waveforms for **Cout** and **Sum**. In Timing mode the simulator uses estimated or actual timing information to test the logical operation and the timing of your design.



## Task 4: Implementing the Design on the DE2 Board

1. From the Menu Bar select: **Assignments** → **Assignment Editor**

2. From the drop-down menu at the top, for **Category**, select **Pin**.





- Double-click <<new>> in the **To** column and select or type **A[0]**. Double-click the adjacent cell under **Location** and type **PIN\_A13**. For a shortcut, you can simply type **A13** and the **Assignment Editor** will find **PIN\_A13** for you. Continue to assign the pins as seen in the table below.


|    | To     | Location | DE2 Board Description |
|----|--------|----------|-----------------------|
| 1  | A[0]   | PIN_A13  | SW9                   |
| 2  | A[1]   | PIN_N1   | SW10                  |
| 3  | A[2]   | PIN_P1   | SW11                  |
| 4  | A[3]   | PIN_P2   | SW12                  |
| 5  | B[0]   | PIN_U3   | SW14                  |
| 6  | B[1]   | PIN_U4   | SW15                  |
| 7  | B[2]   | PIN_V1   | SW16                  |
| 8  | B[3]   | PIN_V2   | SW17                  |
| 9  | Sel    | PIN_N25  | SW1                   |
| 10 | Sum[0] | PIN_AE22 | LEDG0                 |
| 11 | Sum[1] | PIN_AF22 | LEDG1                 |
| 12 | Sum[2] | PIN_W19  | LEDG2                 |
| 13 | Sum[3] | PIN_V18  | LEDG3                 |
| 14 | Cout   | PIN_U18  | LEDG4                 |

*Note: A complete list of pin assignments for the DE2 Development Board can be found here:*

[http://www.terasic.com.tw/attachment/archive/30/DE2\\_Pin\\_Table.pdf](http://www.terasic.com.tw/attachment/archive/30/DE2_Pin_Table.pdf)

- Save the pin assignments by selecting **File** → **Save** from the Menu Bar, or by clicking the Save button  on the toolbar.
- Plug in and power on the DE2 board. Make sure that the **RUN/PROG Switch for JTAG/AS Modes** is in the **RUN** position.

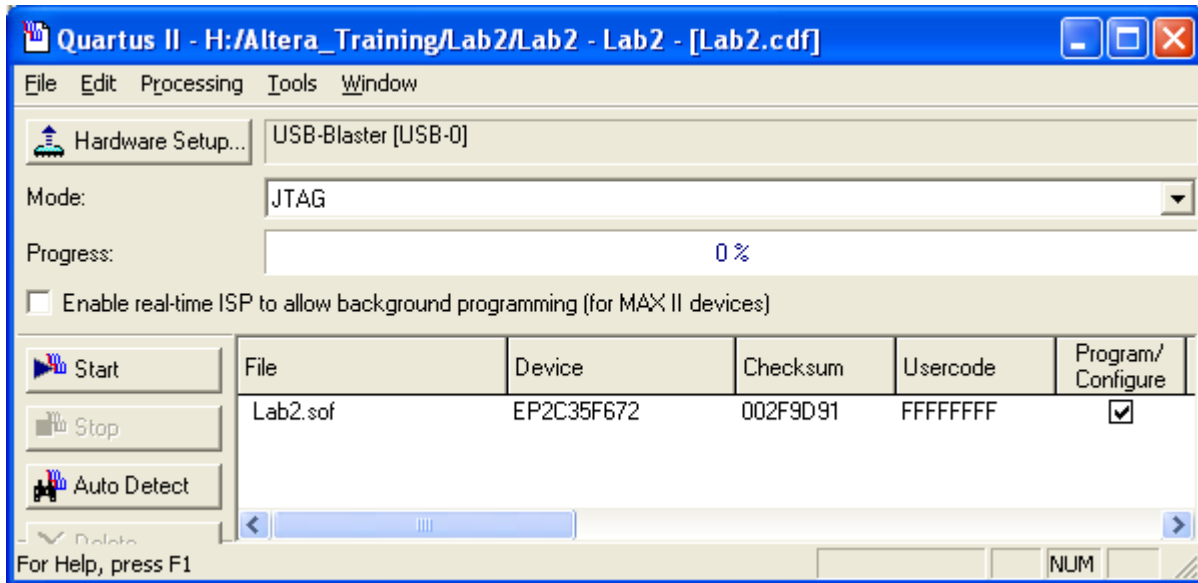6. In the Quartus II window click the **Programmer** button on the Toolbar to open the Programmer window   
The **Hardware Setup...** must be **USB-Blaster [USB-0]**. If not, click the **Hardware Setup...** button and select **USB-Blaster [USB-0]** from the drop-down menu for **Currently selected hardware**. **Mode** should be set to **JTAG**.  
Make sure that the **File** is **Lab2.sof**, **Device** is **EP2C35F672**, and the **Program/Configure** box is checked.



Then click the **Start** button to program the DE2 board.  
When the progress bar reaches 100%, programming is complete.

7. You can now test the program on the DE2 board by using the toggle switches located along the bottom of the board.  
SW0 is the add/subtract selector. Low is for addition.  
SW9 through SW12 are the four bits of data for A.  
SW13 through SW17 are the four bits of data for B.  
The output of the operation is displayed on the first four green LEDs located above the blue push buttons on the DE2 board.  
LEDG4 is the indicator for Cout.

# Lab 3

---

Advanced VHDL

## Lab 3 –Advanced VHDL

This lab will demonstrate many advanced VHDL techniques and how they can be used to your advantage to create efficient VHDL code. Topics include operator balancing, resource sharing, preventing unwanted latches, and state machine encoding schemes.

### Task 1: Create a New Project

#### 1. Start the New Project Wizard

Create a new project using the same procedure from the previous labs.

Set the **Working Directory**, **Project Name**, and **Top-Level Design Entity** as seen in the table below:

|                         |                         |
|-------------------------|-------------------------|
| Working Directory       | H:\Altera_Training\Lab3 |
| Project Name            | Lab3a                   |
| Top-Level Design Entity | Lab3a                   |

*Note: After clicking **Next**, a window may pop up stating that the chosen working directory does not exist. Click **Yes** to create it.*

Continue With the New Project Wizard using the same settings as before.


#### 2. Create a New File


Create a new VHDL file, as discussed previously.

Copy and paste the following code into your new vhd file and save it as Lab3a.vhd:

| Lab 3a – Advanced VHDL – Resource Sharing Code                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                    |  |
|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--|
| <pre>LIBRARY ieee; USE ieee.std_logic_1164.all; USE ieee.std_logic_unsigned.all;  ENTITY Lab3a IS     PORT (w, x, y, z: IN std_logic_vector(7 DOWNTO 0);           result1, result2 : OUT std_logic_vector(23 DOWNTO 0);           CLK: IN std_logic); END;  ARCHITECTURE Lab3a_arch OF Lab3a IS      SIGNAL w_reg, x_reg, y_reg, z_reg: std_logic_vector(7 DOWNTO 0);     SIGNAL temp_w_reg, temp_z_reg: std_logic_vector(7 DOWNTO 0);     SIGNAL temp_xy_reg: std_logic_vector(15 DOWNTO 0);  BEGIN     Mult_Process: PROCESS (clk)     BEGIN         IF RISING_EDGE(clk) THEN             w_reg &lt;= w;             x_reg &lt;= x;             y_reg &lt;= y;             z_reg &lt;= z;             result1 &lt;= w_reg * x_reg * y_reg;             result2 &lt;= x_reg * y_reg * z_reg;             -- temp_w_reg &lt;= w_reg;             -- temp_z_reg &lt;= z_reg;             -- temp_xy_reg &lt;= x_reg * y_reg;             -- result1 &lt;= temp_w_reg * temp_xy_reg;             -- result2 &lt;= temp_xy_reg * temp_z_reg;         END IF;     END PROCESS; END Lab3a_arch;</pre> |  |

## Task 2: Operator Balancing and Resource Sharing

 
1. Compile that code as-is using the **Start Compilation** button . Ignore any warnings at this time.
2. After compilation is complete, observe the **Flow Summary** in the **Compilation Report** that has been generated. Note the **Total logic elements**, **Total combinational functions**, **Dedicated logic registers**, and **Embedded Multiplier 9-bit elements** used in this design.



The screenshot shows the 'Compilation Report - Flow Summary' window. The left pane lists the report contents, and the right pane displays the 'Flow Summary' details.

| Flow Summary                       |                                          |
|------------------------------------|------------------------------------------|
| Flow Status                        | Successful - Wed May 25 08:58:17 2011    |
| Quartus II Version                 | 9.1 Build 222 10/21/2009 SJ Full Version |
| Revision Name                      | Lab3                                     |
| Top-level Entity Name              | Lab3a                                    |
| Family                             | Cyclone II                               |
| Device                             | EP2C35F672C6                             |
| Timing Models                      | Final                                    |
| Met timing requirements            | Yes                                      |
| Total logic elements               | 1 / 33,216 ( < 1 % )                     |
| Total combinational functions      | 1 / 33,216 ( < 1 % )                     |
| Dedicated logic registers          | 0 / 33,216 ( 0 % )                       |
| Total registers                    | 0                                        |
| Total pins                         | 81 / 475 ( 17 % )                        |
| Total virtual pins                 | 0                                        |
| Total memory bits                  | 0 / 483,840 ( 0 % )                      |
| Embedded Multiplier 9-bit elements | 6 / 70 ( 9 % )                           |
| Total PLLs                         | 0 / 4 ( 0 % )                            |

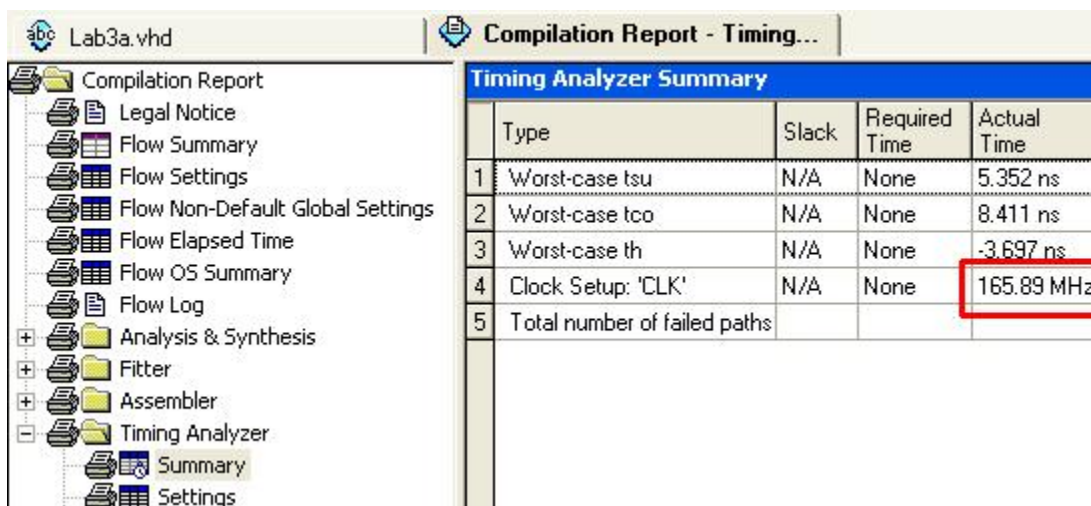
3. In the **Compilation Report**, click on **Timing Analyzer** to display the **Timing Analyzer Summary**. Here you can see that the maximum clock speed of this design is currently 165.89 MHz.



The screenshot shows the 'Compilation Report - Timing Analyzer Summary' window. The left pane lists the report contents, and the right pane displays the 'Timing Analyzer Summary' table.

| Timing Analyzer Summary |                              |       |               |             |
|-------------------------|------------------------------|-------|---------------|-------------|
|                         | Type                         | Slack | Required Time | Actual Time |
| 1                       | Worst-case tsu               | N/A   | None          | 5.352 ns    |
| 2                       | Worst-case tco               | N/A   | None          | 8.411 ns    |
| 3                       | Worst-case th                | N/A   | None          | -3.697 ns   |
| 4                       | Clock Setup: 'CLK'           | N/A   | None          | 165.89 MHz  |
| 5                       | Total number of failed paths |       |               |             |

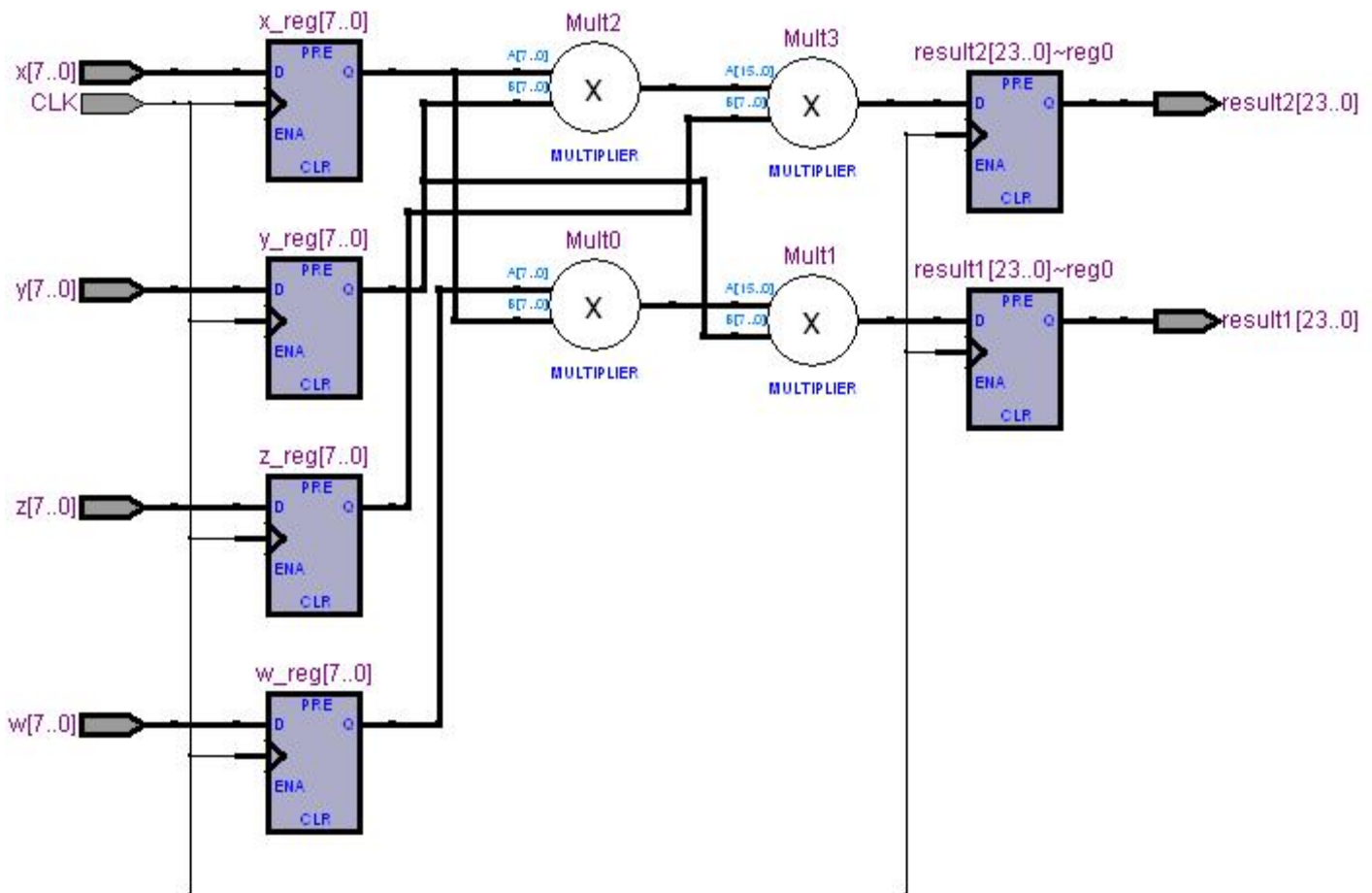4. Select **Tools** → **Netlist Viewers** → **RTL Viewer** to open the **RTL Viewer**. This displays a schematic diagram of the circuit design. Take note of the number of multipliers used.




5. Go to **Lines 21 and 22** in the VHDL code and add parenthesis around **x\_reg \* y\_reg** in each line. This optimizes resource sharing by not having to do the same operation multiple times.

```

14  Mult_Process: PROCESS (clk)
15  BEGIN
16  IF RISING_EDGE(clk) THEN
17    w_reg <= w;
18    x_reg <= x;
19    y_reg <= y;
20    z_reg <= z;
21    result1 <= w_reg * (x_reg * y_reg);
22    result2 <= (x_reg * y_reg) * z_reg;
23  -- temp_w_reg <= w_reg;
24  -- temp_z_reg <= z_reg;
25  -- temp_xy_reg <= x_reg * y_reg;
26  -- result1 <= temp_w_reg * temp_xy_reg;
27  -- result2 <= temp_xy_reg * temp_z_reg;
28  END IF;
29  END PROCESS;


```

 6. Save the changes to **Lab3a.vhd**, then compile the design again and view the results in the **Compilation Report**. Ignore any warnings at this time. This time it can be seen that the number of **Embedded Multiplier 9-bit elements** has been reduced by one, this is due to the resource sharing technique we used.




| Flow Summary                       |                                          |
|------------------------------------|------------------------------------------|
| Flow Status                        | Successful - Wed May 25 09:06:33 2011    |
| Quartus II Version                 | 9.1 Build 222 10/21/2009 SJ Full Version |
| Revision Name                      | Lab3                                     |
| Top-level Entity Name              | Lab3a                                    |
| Family                             | Cyclone II                               |
| Device                             | EP2C35F672C6                             |
| Timing Models                      | Final                                    |
| Met timing requirements            | Yes                                      |
| Total logic elements               | 1 / 33,216 ( < 1 % )                     |
| Total combinational functions      | 1 / 33,216 ( < 1 % )                     |
| Dedicated logic registers          | 0 / 33,216 ( 0 % )                       |
| Total registers                    | 0                                        |
| Total pins                         | 81 / 475 ( 17 % )                        |
| Total virtual pins                 | 0                                        |
| Total memory bits                  | 0 / 483,840 ( 0 % )                      |
| Embedded Multiplier 9-bit elements | 5 / 70 ( 7 % )                           |
| Total PLLs                         | 0 / 4 ( 0 % )                            |

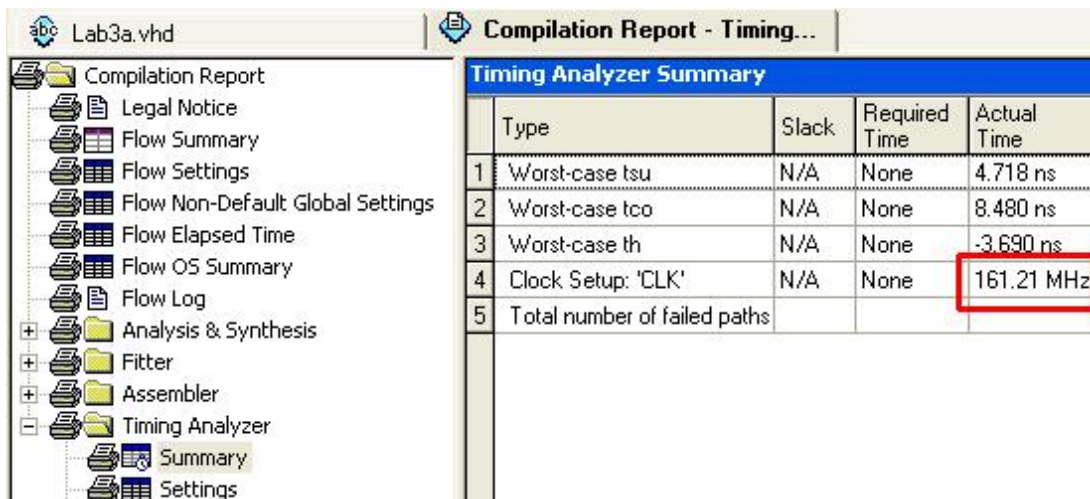
7. View the **Timing Analyzer Summary** to see that although fewer components have been utilized, the clock speed has been reduced slightly.




| Timing Analyzer Summary |                              |       |               |             |
|-------------------------|------------------------------|-------|---------------|-------------|
|                         | Type                         | Slack | Required Time | Actual Time |
| 1                       | Worst-case tsu               | N/A   | None          | 4.718 ns    |
| 2                       | Worst-case tco               | N/A   | None          | 8.480 ns    |
| 3                       | Worst-case th                | N/A   | None          | -3.690 ns   |
| 4                       | Clock Setup: 'CLK'           | N/A   | None          | 161.21 MHz  |
| 5                       | Total number of failed paths |       |               |             |

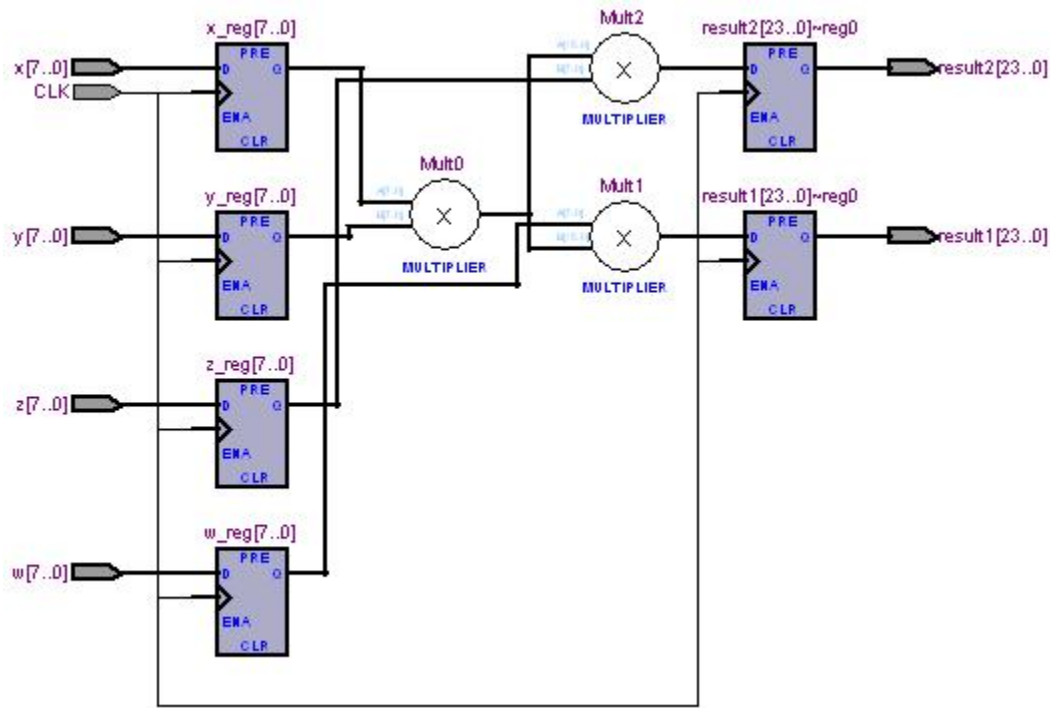8. Open the **RTL Viewer** again to see the new schematic diagram for the circuit design. Compare this schematic diagram to the previous one and you can see that the number of multipliers used has been reduced by one.



9. Go to **Lines 21** and **22** again and highlight both lines by clicking and dragging with the mouse. Then click the **Comment selected text** button on the vertical Text Editor Menu Bar .

 Next, highlight **Lines 23** through **27** and click the **Uncomment selected text** button  which is located below the **Comment selected text** button. The section of code should now look similar to the image below:

```

14  Mult_Process: PROCESS (clk)
15  BEGIN
16  IF RISING_EDGE(clk) THEN
17    w_reg <= w;
18    x_reg <= x;
19    y_reg <= y;
20    z_reg <= z;
21  --result1 <= w_reg * (x_reg * y_reg);
22  --result2 <= (x_reg * y_reg) * z_reg;
23    temp_w_reg <= w_reg;
24    temp_z_reg <= z_reg;
25    temp_xy_reg <= x_reg * y_reg;
26    result1 <= temp_w_reg * temp_xy_reg;
27    result2 <= temp_xy_reg * temp_z_reg;
28  END IF;
29  END PROCESS;

```

The newly uncommented code uses temporary registers to increase clocking speed by pipelining.

10. Save the changes to **Lab3a.vhd**, then compile the design again and view the results in the **Compilation Report**. Ignore any warnings at this time.

The screenshot shows the 'Compilation Report - Flow Summary' window. The left pane displays a tree view of the report contents, including 'Compilation Report', 'Legal Notice', 'Flow Summary', 'Flow Settings', 'Flow Non-Default Global Settings', 'Flow Elapsed Time', 'Flow OS Summary', 'Flow Log', 'Analysis & Synthesis', 'Fitter', 'Assembler', and 'Timing Analyzer'. The right pane shows the 'Flow Summary' details.

| Flow Summary                       |                                          |
|------------------------------------|------------------------------------------|
| Flow Status                        | Successful - Wed May 25 09:10:56 2011    |
| Quartus II Version                 | 9.1 Build 222 10/21/2009 SJ Full Version |
| Revision Name                      | Lab3                                     |
| Top-level Entity Name              | Lab3a                                    |
| Family                             | Cyclone II                               |
| Device                             | EP2C35F672C6                             |
| Timing Models                      | Final                                    |
| Met timing requirements            | Yes                                      |
| Total logic elements               | 17 / 33,216 ( < 1 % )                    |
| Total combinational functions      | 1 / 33,216 ( < 1 % )                     |
| Dedicated logic registers          | 16 / 33,216 ( < 1 % )                    |
| Total registers                    | 16                                       |
| Total pins                         | 81 / 475 ( 17 % )                        |
| Total virtual pins                 | 0                                        |
| Total memory bits                  | 0 / 483,840 ( 0 % )                      |
| Embedded Multiplier 9-bit elements | 5 / 70 ( 7 % )                           |
| Total PLLs                         | 0 / 4 ( 0 % )                            |


The **Compilation Report** indicates that many more logic elements and registers are being used in the design now.

11. Open the **Timing Analyzer Summary** to see that the clock speed has increased due to the pipelining.

The screenshot shows the 'Timing Analyzer Summary' window. The left pane displays a tree view of the report contents, including 'Compilation Report', 'Legal Notice', 'Flow Summary', 'Flow Settings', 'Flow Non-Default Global Settings', 'Flow Elapsed Time', 'Flow OS Summary', 'Flow Log', 'Analysis & Synthesis', 'Fitter', 'Assembler', and 'Timing Analyzer'. The right pane shows the 'Timing Analyzer Summary' table.

| Timing Analyzer Summary |                              |       |               |             |
|-------------------------|------------------------------|-------|---------------|-------------|
|                         | Type                         | Slack | Required Time | Actual Time |
| 1                       | Worst-case tsu               | N/A   | None          | 5.145 ns    |
| 2                       | Worst-case tco               | N/A   | None          | 10.345 ns   |
| 3                       | Worst-case th                | N/A   | None          | -2.930 ns   |
| 4                       | Clock Setup: 'CLK'           | N/A   | None          | 213.04 MHz  |
| 5                       | Total number of failed paths |       |               |             |

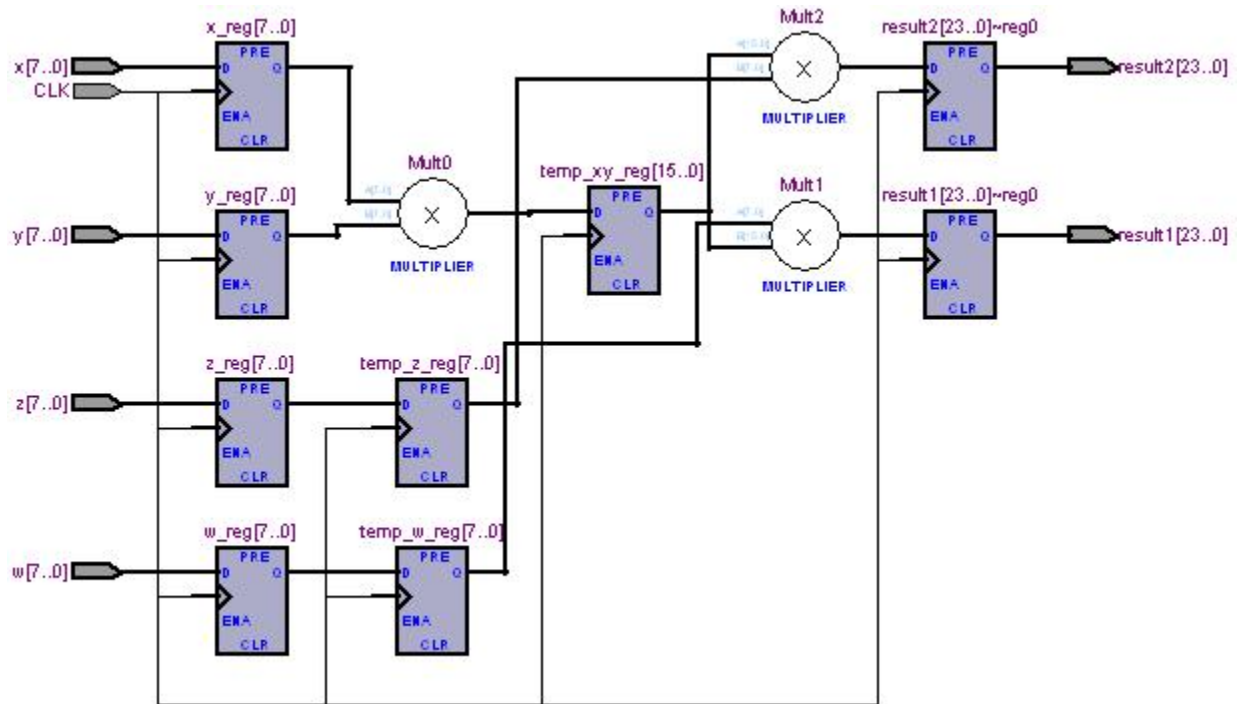12. Open the **RTL Viewer** again to see the new schematic diagram. Compared to the previous schematic diagrams, you can see where the additional registers have been placed.



### Task 3: Preventing Latches

#### 1. Create a New File

Create a new VHDL file, as discussed previously.

Copy and paste the following code into your new vhd file and save it as **Lab3b.vhd**:

#### Lab 3b – Advanced VHDL – State Machine Code

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY Lab3b IS
    PORT (A, B, aclr: IN std_logic;
          CLK: IN std_logic;
          state_data: OUT std_logic_vector(2 DOWNTO 0));
END;

ARCHITECTURE Lab3b_arch OF Lab3b IS
    TYPE State_types IS (S1, S2, S3, S4, S5);

    ATTRIBUTE syn_encoding: STRING;
    ATTRIBUTE syn_encoding OF State_types : TYPE IS
        -- "00001 00010 00100 01000 10000";    -- One-Hot Encoding
        -- "000 001 010 100 110";              -- Minimum Bits
        -- "000 001 011 010 110";              -- Gray Encoding
        -- "000 100 101 111 011";              -- Johnson Encoding
        -- "000 001 010 011 100";              -- Sequential Encoding

    SIGNAL current_state, next_state: State_types;

BEGIN
    state_transitions: PROCESS (aclr, clk)
    BEGIN
        IF aclr = '1' THEN
            current_state <= S1;
        
```

```

        ELSIF rising_edge (clk) THEN
            current_state <= next_state;
        END IF;
    END PROCESS state_transitions;

    State_machine: PROCESS (A, B, current_state, next_state)
    BEGIN
        -- next_state <= current_state;
        CASE current_state IS
            WHEN S1 =>
                IF A='1' THEN
                    next_state <= S2;
                END IF;
            WHEN S2 =>
                IF A='0' THEN
                    next_state <= S1;
                ELSIF A='1' THEN
                    next_state <= S3;
                END IF;
            WHEN S3 =>
                IF A='0' THEN
                    next_state <= S1;
                ELSIF A='1' AND B='1' THEN
                    next_state <= S4;
                END IF;
            WHEN S4 =>
                IF B='1' THEN
                    next_state <= S5;
                ELSE
                    next_state <= S1;
                END IF;
            WHEN S5 =>
                IF (A='0' AND B='1') THEN
                    next_state <= S2;
                ELSIF (A='1' AND B='0') THEN
                    next_state <= S3;
                END IF;
            WHEN OTHERS=>
                next_state <= current_state;
        END CASE;
    END PROCESS;

    Output_Process: PROCESS (current_state)
    BEGIN
        state_data <= (OTHERS => '0');
        CASE current_state IS
            WHEN S1 =>
                state_data <= "001";
            WHEN S2 =>
                state_data <= "010";
            WHEN S3 =>
                state_data <= "011";
            WHEN S4 =>
                state_data <= "100";
            WHEN S5 =>
                state_data <= "101";
            WHEN OTHERS =>
                NULL;
        END CASE;
    END PROCESS;
END Lab3b_arch;

```

2. Select **Project** → **Set as Top-Level-Entity** to specify that **Lab3b.vhd** is now the main file for the design.

Compile that code using the **Start Compilation** button




Click **OK** when compilation is complete.

- Click on the **Warning** tab in the **Messages** pane to view the warnings.



**Warning (10631), Warning: Latch next\_state.S4\_148 has unsafe behavior**, and others are due to unintentional latching conditions caused by not initializing the signals assigned within a case statement.


- Open the **RTL Viewer** to see the complex logic that this unintentional latching creates. Upon simulation the circuit design may also produce unintended results due to these latches.
- Highlight **Line 29** in the Lab3b.vhd code and click the **Uncomment selected text** button . This adds an initialization value at the beginning of the case statement for the next\_state signal.

```

27 State_machine:PROCESS (A, B, current_state, next_state)
28 BEGIN
29 next_state <= current_state;
30 CASE current_state IS
31 WHEN S1 =>


```

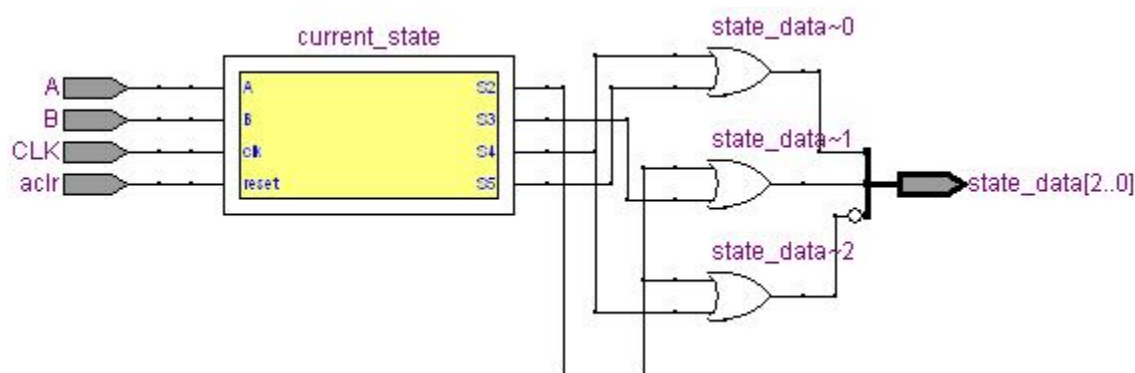- Save the changes and compile the design. Now it can be seen that the only warnings left relate to specifics regarding pin assignments on the physical FPGA device.
- Open the **RTL Viewer** again to see that now the logic is much simplified, and what we intended.




## Task 4: State Machine Encoding

 
1. Double-clicking the yellow **current\_state** box in the **RTL Viewer** will open up the **State Machine Viewer**. This graphically shows the state transitions and their associated conditions. Alternately, the **State Machine Viewer** can be opened by selecting **Tools** → **Netlist Viewers** → **State Machine Viewer**.



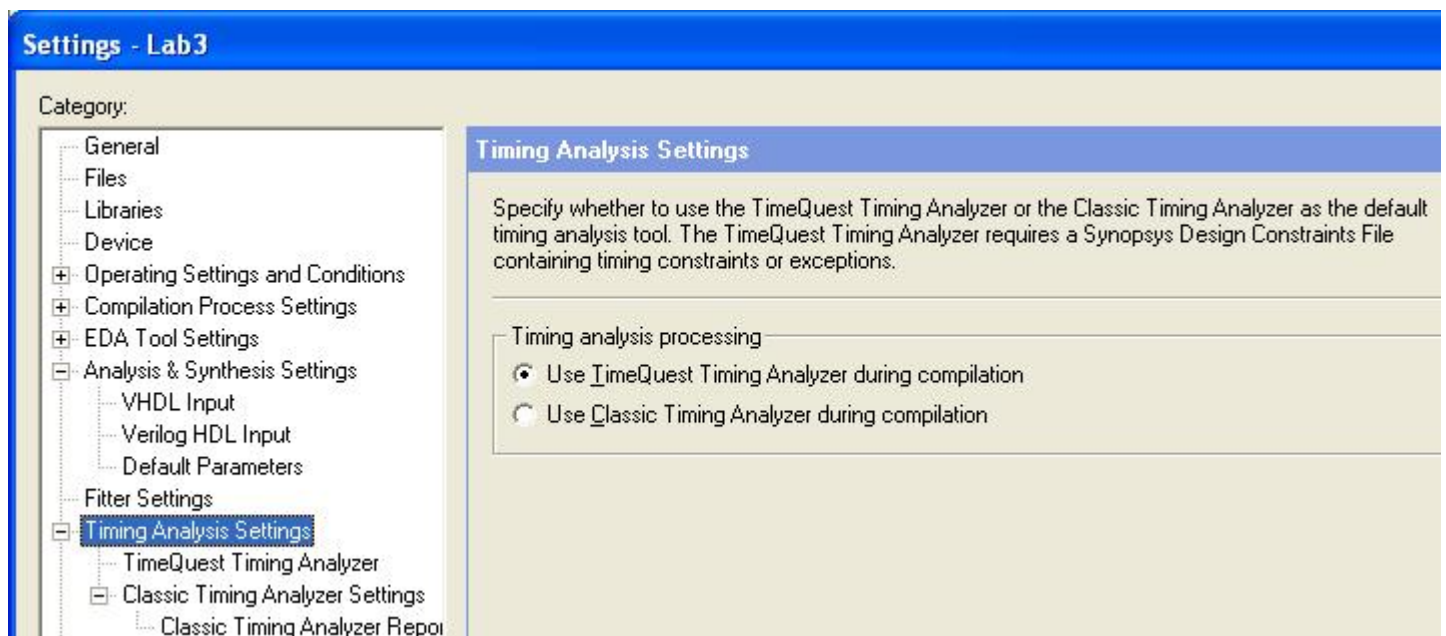2. Go to **Assignments** → **Settings** and select **Timing Analysis Settings**. Select **Use TimeQuest Timing Analyzer during compilation** under the **Timing analysis processing** heading. Click **OK** to close the **Settings** window, then compile the design again.




 3. In the **Compilation Report – Flow Summary**, note the number of **Total logic elements** and **Dedicated logic registers** used. Then under the **TimeQuest Timing Analyzer Summary**, select **Slow Model** and view the maximum clock frequency of the design.



|   | Fmax       | Restricted Fmax | Clock Name | Note                 |
|---|------------|-----------------|------------|----------------------|
| 1 | 693.48 MHz | 420.17 MHz      | CLK        | limit due to minimum |

 4. In the **Compilation Report**, click on **Analysis & Synthesis** and then expand the subheading **State Machines**. This shows the encoding type used by the compiler to identify the different states. The encoding type is currently **User-Encoded** meaning that the VHDL code specifies the encoding used. Alternately the compiler can be configured to use a specific encoding type. The VHDL code currently is using a **Sequential Encoding** scheme to identify the states.



|   | Name             | current_state~6 | current_state~5 | current_state~4 |
|---|------------------|-----------------|-----------------|-----------------|
| 1 | current_state.S1 | 0               | 0               | 0               |
| 2 | current_state.S2 | 0               | 0               | 1               |
| 3 | current_state.S3 | 0               | 1               | 0               |
| 4 | current_state.S4 | 0               | 1               | 1               |
| 5 | current_state.S5 | 1               | 0               | 0               |


5. Select **Line 16** in the **Lab3b.vhd** code and click the **Comment selected text** button. Then select **Line 14** and click the **Uncomment selected text** button. This changes the encoding type to **Gray Encoding**. Save the changes to Lab3b.vhd and compile the design to see the results of changing the state machine encoding.

```

10  ATTRIBUTE syn_encoding: STRING;
11  ATTRIBUTE syn_encoding OF State_types : TYPE IS
12  -- "00001 00010 00100 01000 10000"; -- One-Hot Encoding
13  -- "000 001 010 100 110"; -- Minimum Bits
14  "000 001 011 010 110"; -- Gray Encoding
15  -- "000 100 101 111 011"; -- Johnson Encoding
16  --"000 001 010 011 100"; -- Sequential Encoding

```

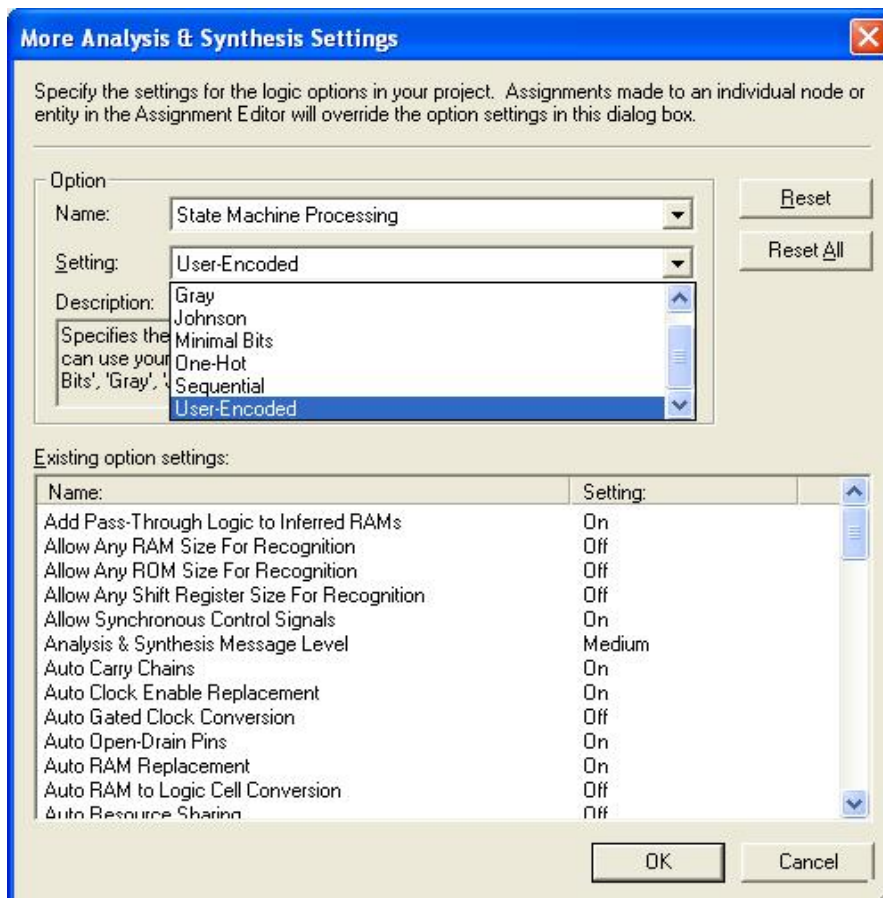6. Again look at the **Flow Summary** of the **Compilation Report**, and **Fmax Summary** under the **Slow Model** in the **TimQuest Timing Analyzer** section of the **Compilation Report**. Compare the current values to the previous results.
7. **Lines 12** through **16** in the **Lab3b.vhd** file each contain a different encoding type which can be selected by uncommenting the desired line and then compiling the design again and comparing the changes to the number of design components used and the clock speed.
8. Alternately, the encoding type can be set by the Quartus II software by selecting **Assignments** → **Settings** and then selecting the **Analysis & Synthesis** heading and clicking the **More Settings...** button to open the **More Analysis & Synthesis Settings** window. Then select **State Machine Processing** in the drop down menu for **Name**. In the drop down menu for **Setting** select the desired state machine encoding then click **OK** in the **More Analysis & Synthesis Settings** window and in the **Settings** window to save the changes.



# Lab 4

---

## VHDL Testbenching

## Lab 4 – VHDL Testbenching

This lab will show how to write testbench files to test your circuit designs using the ModelSim software.

---

### Task 1: Create a New Project

1. **Start the ModelSim software.**

From the Windows Start Menu, select:

**All Programs → Altera → ModelSim-Altera 6.5b (Quartus II 9.1) Starter Edition → ModelSim-Altera 6.5b (Quartus II 9.1) Starter Edition**


2. Select **File → New → Project** to open the **Create Project** window.

For the **Project Name** type **Lab4**


For the **Project Location** type **H:/Altera\_Training/Lab4**

Then click **OK**.

 Click **OK** again if you are asked to create the project directory.




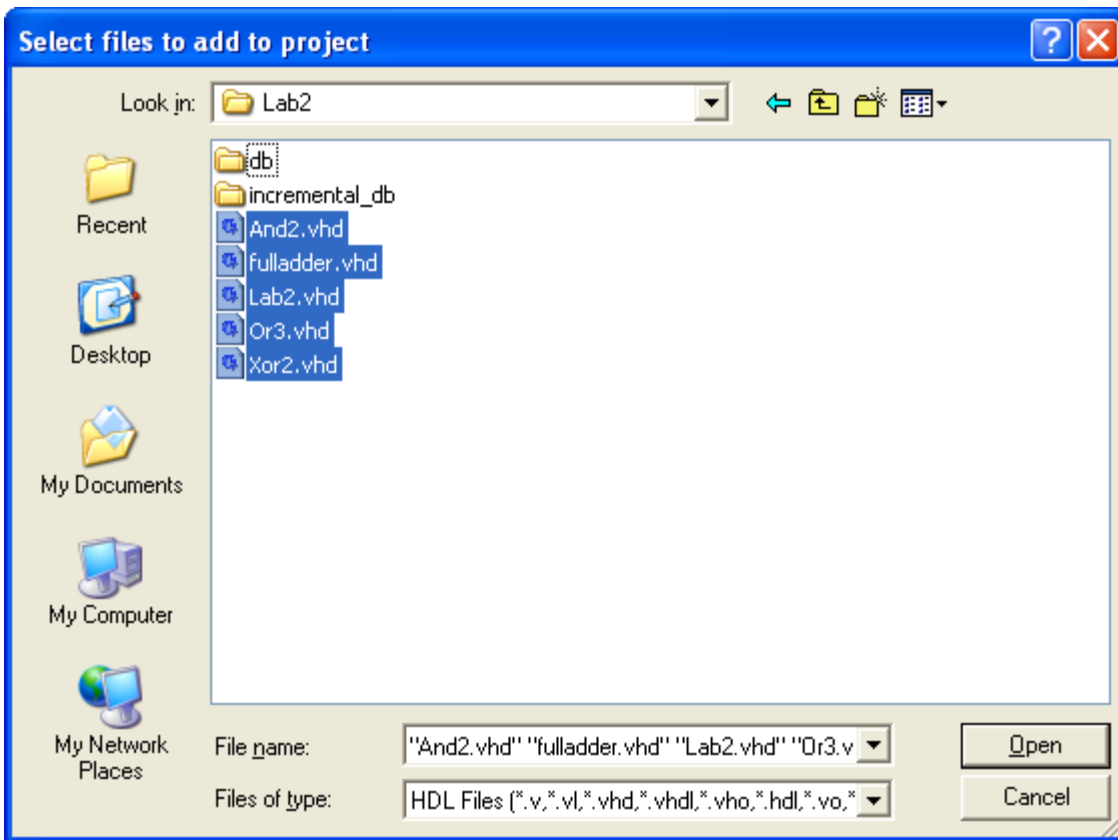3. In the **Add items to the Project** window click **Add Existing File**.  
Click **Browse...** on the **Add file to Project** window and browse to **H:/Altera\_Training/Lab2**  
Select all of the **.vhd** files and click open.



Then click **OK** in the **Add file to Project** window.

 4. Click **Create New File** in the **Add items to the Project** window.  
Type **Lab4** in the **Create Project File** window and click **OK**.



Click **Close** in the **Add items to the Project** window to close it.

5. Double-click on **Lab4.vhd** in the project window of ModelSim to open an editor pane. Copy and paste the following code into the editor pane:

Lab 4 – Testbenching – Testbench Code

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Lab4 IS
END Lab4;

ARCHITECTURE TBarch OF Lab4 IS
  COMPONENT Lab2 IS
    PORT (A: IN std_logic_vector(3 DOWNTO 0);
          B: IN std_logic_vector(3 DOWNTO 0);
          Sel: IN std_logic;
          Sum: OUT std_logic_vector(3 DOWNTO 0);
          Cout: OUT std_logic);
  END COMPONENT;

  SIGNAL A_s, B_s, Sum_s: std_logic_vector(3 DOWNTO 0);
  SIGNAL Sel_s, Cout_s, clk: std_logic;

  BEGIN
    CompToTest: Lab2
      PORT MAP (A_s, B_s, Sel_s, Sum_s, Cout_s);


    clk_Process: PROCESS
    BEGIN
      clk <= '0';
      WAIT FOR 10 ns;
      clk <= '1';
      WAIT FOR 10 ns;
    END PROCESS;

    Adder_Process: PROCESS
    BEGIN
      A_s <= "0000"; B_s <= "0000"; Sel_s <= '0';
      WAIT FOR 10 ns;
      A_s <= "0011"; B_s <= "0001"; Sel_s <= '1';
      WAIT FOR 10 ns;
      A_s <= "0100"; B_s <= "0010"; Sel_s <= '0';
      WAIT FOR 10 ns;
      WAIT;
    END PROCESS;
  END TBarch;
```


6. Save the changes to **Lab4.vhd** by clicking the **Save** button  on the toolbar. Compile all the files by selecting **Compile** → **Compile All** from the menu bar.

## Task 2: Simulating the Circuit

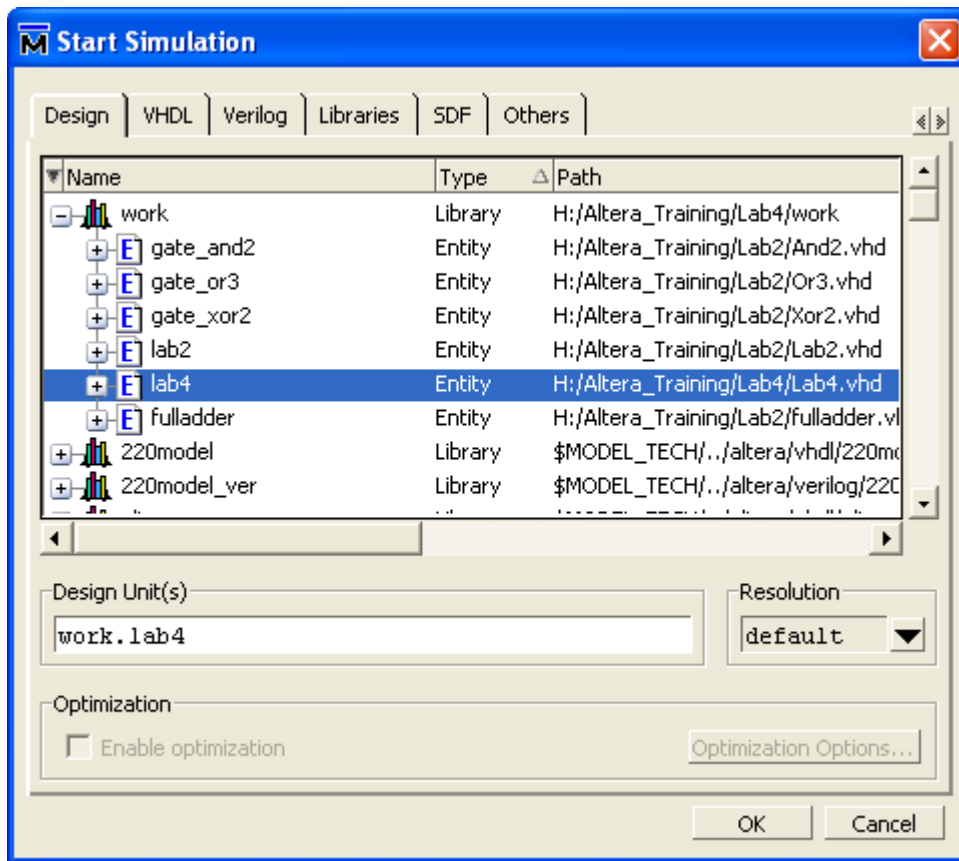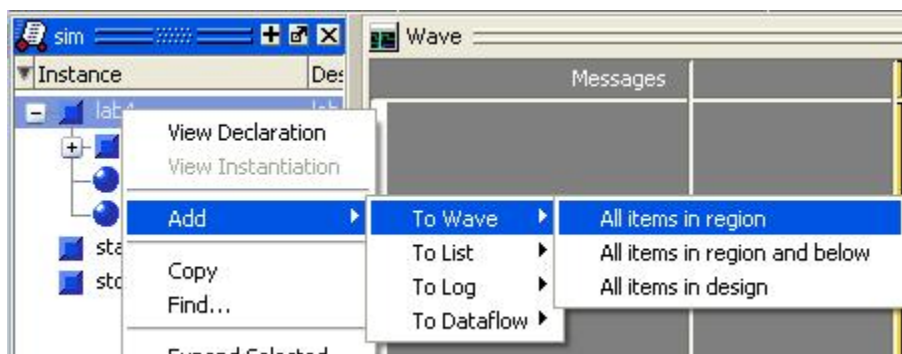
 
1. Select **Simulate** → **Start Simulation** from the menu bar to open the **Start Simulation** window. Expand the **work** directory, select **lab4**, and click **OK**.



2. In the **sim** pane, right-click on **lab4** and select **Add** → **To wave** → **All items in region**. This adds the signals from the test bench file to the waveform so we can see their values when the simulation runs. You may need to play around with the window sizing some in order to expand the waveform window to a reasonable size.




3. Change the simulation **Run Length** to **50 ns** by typing it into the entry box on the toolbar

 Then click the **Run** button  to start the simulation.

Press the **minus key**  to zoom out to an appropriate size. To zoom in, press **shift +** 

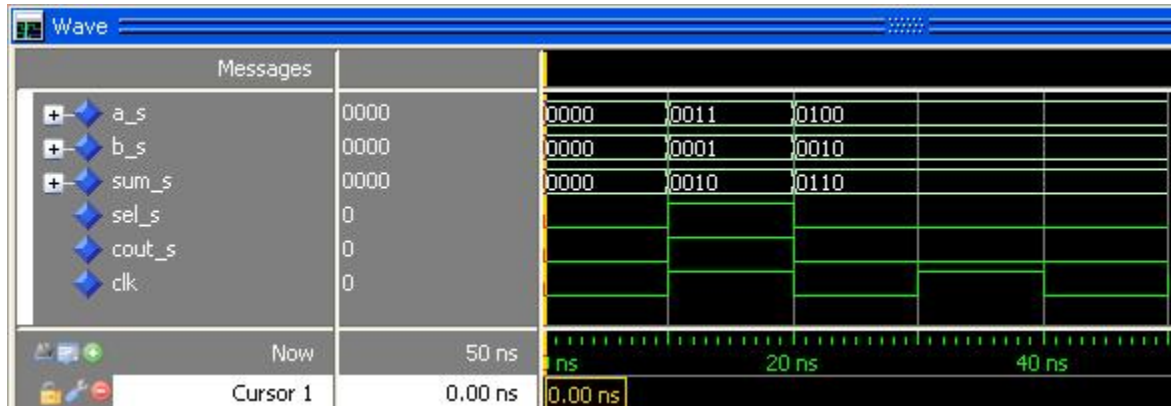The resulting waveform should be similar to the image below:



### Task 3: Editing the Test Bench


1. Look at the **Adder\_Process** of the **lab4.vhd** code, here is where the values for the two four-bit numbers are assigned, as well as where the add/subtract selection is made. More input combinations can be created to test additional input scenarios. To see what output an overflow condition would generate, add the following on **lines 33 and 34**:


```
A_s <= "1100"; B_s <= "0100"; Sel_s <= '0';
  WAIT FOR 10 ns;
```



The resulting Adder\_Process should look similar to the image below:


```
25  Adder_Process: PROCESS
26  BEGIN
27    A_s <= "0000"; B_s <= "0000"; Sel_s <= '0';
28    WAIT FOR 10 ns;
29    A_s <= "0011"; B_s <= "0001"; Sel_s <= '1';
30    WAIT FOR 10 ns;
31    A_s <= "0100"; B_s <= "0010"; Sel_s <= '0';
32    WAIT FOR 10 ns;
33    A_s <= "1100"; B_s <= "0100"; Sel_s <= '0';
34    WAIT FOR 10 ns;
35  END PROCESS;
```

This will cause our adder/subtractor to add **12** (1100) with **4** (0100) which would give us the result of **16** (10000), but because of the four-bit limit for our **sum\_s** signal, an overflow condition will result.

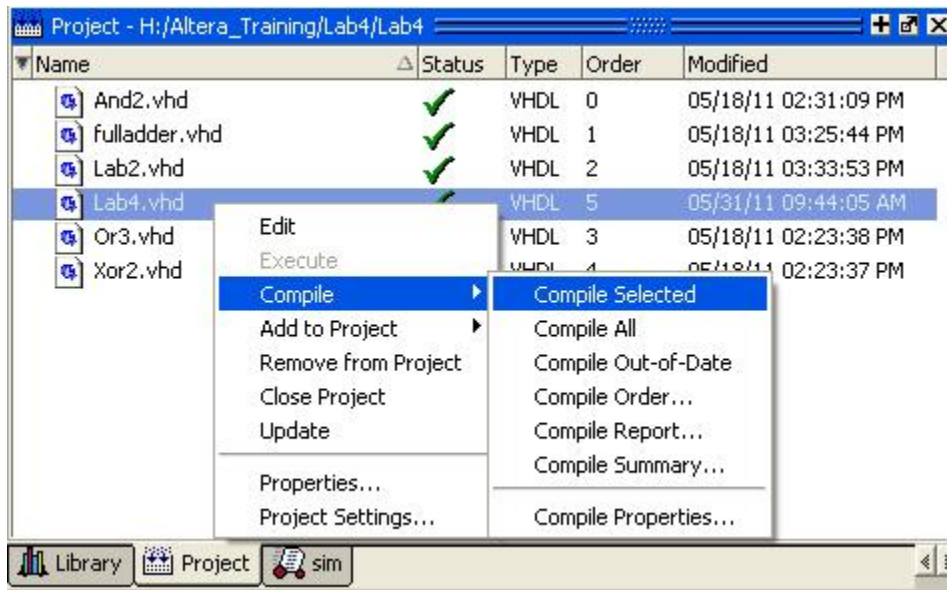- Save the changes to **Lab4.vhd** by clicking the **Save** button  on the toolbar, then select the **Project** tab and right-click **Lab4.vhd** and select **Compile** → **Compile Selected**.



  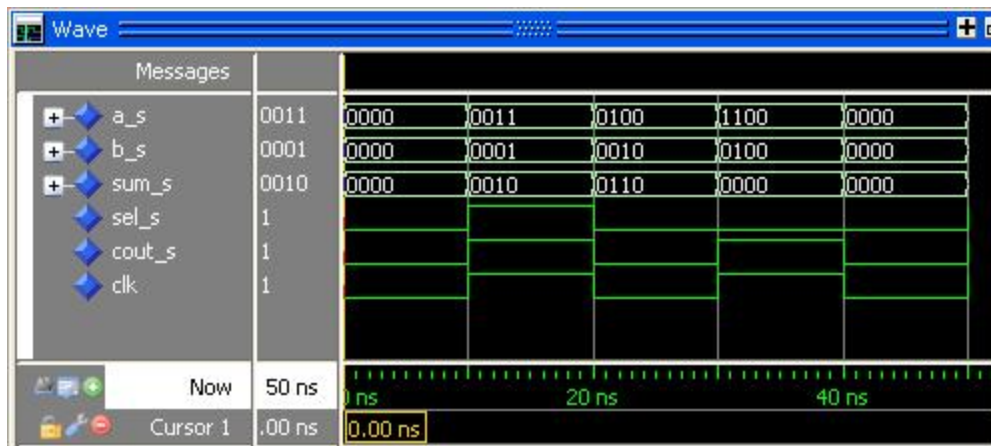- Once the compilation is complete, click the **Restart** button  to restart the simulation, then click **Run**  to run the simulation again.
- Now it can be seen that the testing condition we added to the test bench file occurs from **30 to 40 ns** and the result is as expected, **cout\_s** is high indicating overflow and **sum\_s** is all low.



# Lab 5

---

A VHDL Reaction Timer

## Lab 5 – A VHDL Reaction Timer

This lab will combine many advanced VHDL techniques including timers, seven segment display drivers, packages and functions, and state machines to create a simple game that to test a person's reaction time.

### Task 1: Create a New Project

#### 1. Start the New Project Wizard

Create a new project using the same procedure from the previous labs.

Set the **Working Directory**, **Project Name**, and **Top-Level Design Entity** as seen in the table below:

|                         |                         |
|-------------------------|-------------------------|
| Working Directory       | H:\Altera_Training\Lab5 |
| Project Name            | Lab5                    |
| Top-Level Design Entity | Lab5                    |

*Note: After clicking **Next**, a window may pop up stating that the chosen working directory does not exist. Click **Yes** to create it.*

Continue With the New Project Wizard using the same settings as before.

#### 2. Create a New File

Create a new VHDL file, as discussed previously.

Copy and paste the following code into your new vhd file and save it as **Lab5.vhd**:

#### Lab 5 – A VHDL Reaction Timer – Reaction Timer Code

```
library IEEE;
use IEEE.std_logic_1164.all;
USE IEEE.std_logic_unsigned.ALL;
USE work.bin_to_7seg.ALL;

ENTITY Lab5 IS
    PORT(
        -- 50Mhz clock signal from the DE2 board
        clk: IN std_logic;

        -- KEY3 and KEY0 on the DE2 board
        push_button, reset: IN std_logic;

        -- Outputs for the LEDS
        LEDR, LEDG: OUT std_logic_vector(7 DOWNTO 0);

        -- 7 segment display outputs
        digit1, digit2, digit3, digit4: OUT std_logic_vector(6 DOWNTO 0));
END;

ARCHITECTURE Lab5_beh of Lab5 IS

    -- Type definition for the four states used for the state machine
    Type Timer_State IS (idle, countdown, timing, score);

    -- Signals of type Timer_State used to control the state machine
    SIGNAL current_state, next_state : Timer_State := idle;

    -- 16-bit binary value of the elapsed time in milliseconds
    SIGNAL elapsed_time: std_logic_vector(15 DOWNTO 0):= (OTHERS => '0');

    -- Flag that indicates the status of the countdown
    SIGNAL countdown_done: std_logic := '0';
```

```

-- Flag that indicates a good input signal and the desire to change states
SIGNAL state_change: std_logic := '0';

-- Sample pulse generated by the SampleGen process used by the Debounce
-- process to either increment the counter or signal a state change
SIGNAL sample: std_logic;

-- Maximum number of good input pulses needed to qualify as clean input
CONSTANT PULSE_COUNT_MAX: integer := 20;

-- Counter used to record the number of good input pulses
SIGNAL counter: integer range 0 to PULSE_COUNT_MAX;

-- The KEY0-3 push buttons on the DE2 board are active low, so sync is the
-- inverse of the KEY3 push button's value
SIGNAL sync: std_logic;

```

BEGIN

----- SampleGen Process -----

```

-- A counter that sends a signal to sample the input button
-- when the maximum count is reached.
SampleGen : process(clk)

```

```

    -- Sample_counter is a counter used to control the sample frequency
    -- sample frequency = clock frequency / (sample_counter(max)+1)
    variable sample_counter: integer range 0 to 24999;

```

begin

```

    if rising_edge(clk) then
        if (reset='0') then
            sample <= '0';
            sample_counter := 0;
        else
            if (sample_counter = 24999) then
                sample_counter := 0;
                sample <= '1';
            else
                sample <= '0';
                sample_counter := sample_counter + 1;
            end if;
        end if;
    end if;

```

```

end process;

```

----- Debounce Process -----

```

-- A counter that is incremented every sample pulse while the
-- input button is pressed, when the switch is not pressed the
-- counter is reset to zero. if the counter is at its maximum,
-- the debouncer output is high, otherwise its low.
Debounce : process(clk)

```

```

    begin
        if rising_edge(clk) then
            if (reset='0') then
                sync <= '0';
                counter <= 0;
                state_change <= '0';
            else
                sync <= NOT push_button;
                if (sync='0') then
                    counter <= 0;
                    state_change <= '0';
                    -- Button not pressed
                elsif (sample = '1') then
                    -- Button pressed
                    if (counter=PULSE_COUNT_MAX) then
                        state_change <= '1';
                    else
                        counter <= counter + 1;
                    end if;
                end if;
            end if;
        end if;
    end if;

```

```

        end if;
    end process;

----- Timer_State_Machine Process -----
-- Sets the next_state for the state machine. The next
-- desired state is stored on the next_state signal, which is
-- used in the State_Transitions process to change the current
-- state.
Timer_State_Machine: PROCESS (clk)
    BEGIN
        next_state <= current_state;
        CASE current_state IS

            -- If the state_change flag is set and the push_button is pushed then the
            -- next desired state is the countdown state
            WHEN idle =>
                IF state_change = '1' AND push_button = '1' THEN
                    next_state <= countdown;
                END IF;

            -- When the countdown_done flag is high the next desired state is the timing
            -- state
            WHEN countdown =>
                IF countdown_done = '1' THEN
                    next_state <= timing;
                END IF;

            -- If the state_change flag is high and the push_button is pushed then the
            -- next desired state is the score state.
            WHEN timing =>
                IF state_change = '1' AND push_button = '1' THEN
                    next_state <= score;
                END IF;

            -- Stay in score state. Pressing reset will override this
            WHEN score =>
                next_state <= score;

            -- In case of entering any undefined states, next desired state is idle
            WHEN OTHERS =>
                next_state <= idle;

        END CASE;
    END PROCESS Timer_State_Machine;

----- State_Transitions Process -----
-- Loads the next_state onto the current_state, or resets the
-- state to idle if the reset button is pressed.
State_Transitions: PROCESS (reset, clk)
    BEGIN
        IF reset = '0' THEN
            current_state <= idle;
        ELSIF rising_edge (clk) THEN
            current_state <= next_state;
        END IF;
    END PROCESS state_transitions;

----- Output_Process Process -----
-- This process is what controls the LED the outputs as seen
-- by the user.
Output_Process: PROCESS (current_state, clk)

    -- Two 16-bit countdown counters to create a delay for the countdown state
    variable countdown_count1, countdown_count2: integer range 0 to 65535;

    -- A delay counter used to delay the incrementing of timing_count so that
    -- timing_count is in milliseconds
    variable timing_counter: integer range 0 to 49999;

    -- 16-bit binary value of the time count in milliseconds
    variable timing_count: std_logic_vector(15 DOWNTO 0);

```

```

BEGIN
  IF rising_edge(clk) THEN
    CASE current_state IS
      -- Reset everything in idle mode
      WHEN idle =>
        LEDG <= (OTHERS => '0');
        LEDR <= (OTHERS => '0');
        elapsed_time <= (OTHERS => '0');
        timing_count := (OTHERS => '0');
        timing_counter := 0;
        countdown_count1 := 0;
        countdown_count2 := 0;

      -- Turn red LEDs on and begin countdown counter, when countdown counter
      -- is done, countdown_done is high.
      WHEN countdown =>
        LEDG <= (OTHERS => '0');
        LEDR <= (OTHERS => '1');

        countdown_count1 := countdown_count1 + 1;
        IF countdown_count1 = 65535 THEN
          countdown_count2 := countdown_count2 + 1;
          countdown_count1 := 0;
        END IF;
        IF (countdown_count2 = 763) THEN
          countdown_done <= '1';
          countdown_count2 := 0;
        END IF;

      -- Turn green LEDs on and begin counting in milliseconds. Set countdown_done
      -- to low.
      WHEN timing =>
        LEDG <= (OTHERS => '1');
        LEDR <= (OTHERS => '0');

        IF (timing_counter = 49999) THEN
          timing_count := timing_count + 1;
          timing_counter := 0;
        ELSE
          timing_counter := timing_counter + 1;
        END IF;
        elapsed_time <= timing_count;
        countdown_done <= '0';

      -- Turn all LEDs on, set timing counters to 0
      WHEN score =>
        LEDG <= (OTHERS => '1');
        LEDR <= (OTHERS => '1');

        timing_count := (OTHERS => '0');
        timing_counter := 0;

      -- Turn all LEDs off
      WHEN OTHERS =>
        LEDG <= (OTHERS => '0');
        LEDR <= (OTHERS => '0');
    END CASE;
  END IF;
END PROCESS Output_Process;

----- Time_Display Process -----
-- This process displays the time value on four of the seven
-- segment displays on the DE2 board. The functions bin_to_bcd
-- and bcd_to_7seg are called from the included bin_to_7seg.vhd
Time_Display_Process: PROCESS (elapsed_time)
  -- 20-bit binary variable that holds 5 4-bit BCD values, only 4 are used to
  -- display on the 4 7-segment displays
  variable bcd_time: std_logic_vector(19 DOWNTO 0);

  BEGIN

```

```
-- First then elapsed time must be converted from binary to BCD using the
-- bin_to_bcd() function and stored on to the bcd_time variable.
-- Next, the BCD values are fed out to the four 7-segment displays by using
-- the bcd_to_7seg() function. The first four bits of bcd_time correspond
-- to digit1, the next four to digit2, and so on.
```

```
    bcd_time := bin_to_bcd(elapsed_time);
    digit1 <= bcd_to_7seg(bcd_time(3 DOWNTO 0));
    digit2 <= bcd_to_7seg(bcd_time(7 DOWNTO 4));
    digit3 <= bcd_to_7seg(bcd_time(11 DOWNTO 8));
    digit4 <= bcd_to_7seg(bcd_time(15 DOWNTO 12));
```

```
END PROCESS;
```

```
END Lab5_beh;
```

### 3. Create another New File

Create another new VHDL file.

Copy and paste the following code into your new vhd file and save it in the project directory as **bin\_to\_7seg.vhd**, make sure the **Add file to current project** box is checked in the **Save As** window:

#### Lab 5 – A VHDL Reaction Timer – Reaction Timer Code

```
library IEEE;
use IEEE.std_logic_1164.all;
USE IEEE.std_logic_unsigned.ALL;
use ieee.numeric_std.all;

PACKAGE bin_to_7seg IS

    -- Bin_to_BCD takes in a 16 bit binary number and returns a 20-bit BCD
    -- representation of it. This would be the equivalent of a 5-digit integer
    -- with 5 groups of 4-bits, each representing 1 digit.
    FUNCTION Bin_to_BCD (bin :std_logic_vector(15 DOWNTO 0)) return
std_logic_vector;

    -- BCD_to_7seg takes a 4-bit BCD value and returns a 7-bit value that
    -- represents the desired segments to turn on for a 7-segment display
    FUNCTION BCD_to_7seg (bcd :std_logic_vector(3 DOWNTO 0)) return
std_logic_vector;

END;

PACKAGE BODY bin_to_7seg IS

    ----- Binary to BCD Conversion Function -----
    FUNCTION Bin_to_BCD (bin :std_logic_vector(15 DOWNTO 0)) return
std_logic_vector IS
        variable i : integer:=0;
        variable bcd : std_logic_vector(19 downto 0) := (others => '0');
        variable bint : std_logic_vector(15 DOWNTO 0) := bin;

        BEGIN

            for i in 0 to 15 loop
                bcd(19 downto 1) := bcd(18 downto 0);
                bcd(0) := bint(15);
                bint(15 downto 1) := bint(14 downto 0);
                bint(0) := '0';

                if(i < 15 and bcd(3 downto 0) > "0100") then
                    bcd(3 downto 0) := bcd(3 downto 0) + "0011";
                end if;

                if(i < 15 and bcd(7 downto 4) > "0100") then
                    bcd(7 downto 4) := bcd(7 downto 4) + "0011";
                end if;
            end loop;
        END;
    END FUNCTION Bin_to_BCD;

    FUNCTION BCD_to_7seg (bcd :std_logic_vector(3 DOWNTO 0)) return
std_logic_vector IS
        variable seg : std_logic_vector(6 downto 0) := (others => '0');
        variable bcd4 : std_logic_vector(3 DOWNTO 0) := bcd;

        BEGIN
            seg(0) := bcd4(0);
            seg(1) := bcd4(1);
            seg(2) := bcd4(2);
            seg(3) := bcd4(3);
            seg(4) := bcd4(0);
            seg(5) := bcd4(1);
            seg(6) := bcd4(2);
        END;
    END FUNCTION BCD_to_7seg;

END PACKAGE BODY bin_to_7seg;
```

```

        if(i < 15 and bcd(11 downto 8) > "0100") then
            bcd(11 downto 8) := bcd(11 downto 8) + "0011";
        end if;

        if(i < 15 and bcd(15 downto 12) > "0100") then
            bcd(15 downto 12) := bcd(15 downto 12) + "0011";
        end if;

        if(i < 15 and bcd(19 downto 16) > "0100") then
            bcd(19 downto 16) := bcd(19 downto 16) + "0011";
        end if;

        END LOOP;

        RETURN BCD;
    END FUNCTION;

----- BCD to 7 Seg Display Conversion Function -----
    FUNCTION BCD_to_7Seg (bcd : std_logic_vector(3 DOWNTO 0)) return
std_logic_vector IS

        variable seg7 : std_logic_vector(6 downto 0) := (others => '1');

    BEGIN
        CASE bcd IS
            WHEN "0000"=>seg7:="1000000"; -- 0 --
            WHEN "0001"=>seg7:="1111001"; -- 1 --
            WHEN "0010"=>seg7:="0100100"; -- 2 --
            WHEN "0011"=>seg7:="0110000"; -- 3 --
            WHEN "0100"=>seg7:="0011001"; -- 4 --
            WHEN "0101"=>seg7:="0010010"; -- 5 --
            WHEN "0110"=>seg7:="0000010"; -- 6 --
            WHEN "0111"=>seg7:="1111000"; -- 7 --
            WHEN "1000"=>seg7:="0000000"; -- 8 --
            WHEN "1001"=>seg7:="0011000"; -- 9 --
            WHEN OTHERS=>seg7:="1111111"; -- X --
        END CASE;
        RETURN seg7;
    END FUNCTION;

END PACKAGE BODY;

```

#### 4. About the Code

The code in **Lab5.vhd** is broken up into a variety of processes.

**SampleGen** and **Debounce** are processes used together to debounce the input signal from the momentary push button (**KEY3**) on the development board. The hardware samples the push button at a rate of 2 kHz, and after 20 consecutive low readings (in this case the push button switches are active low) the hardware considers the button to have been pressed.

The program uses a finite state machine to represent the various states used. These states are **idle**, **countdown**, **timing**, and **score**. **Idle** is when the hardware is waiting for the user to initiate the game. **Countdown** is a timed countdown sequence which adds a delay before the millisecond timer starts counting. **Timing** is when the millisecond timer starts counting how long it takes the user to push the button to stop the counting. **Score** freezes the display to show the user's reaction time.

The process **Timer\_State\_Machine** is what defines the requirements to change from one state to the next. This process stores the next desired state onto the **next\_state** signal, which is then set as the **current\_state** by the **State\_Transitions** process.

The **Output\_Process** contains everything that happens within each of the individual states.

In the **Idle** state within the the green and red LEDs are turned off, and all timers and counters are reset to zero.

In the **Countdown** state the red LEDs are turned on and the countdown timer starts. When the

countdown timer is done, **countdown\_done** is set high.

Once **countdown\_done** is high, the **current\_state** becomes the **Timing** state. Here the millisecond timer starts counting until the user presses the button to stop it.

Finally in the **Score** state, the user's time is displayed in milliseconds.

Pressing the reset button (**KEY1** on the DE2 development board) will return you to the **idle** state at any point.

The **Time\_Display\_Process** takes in the elapsed time in binary format, converts that from binary to BCD, and then to a value suitable to use to display the desired decimal digit on one of four seven segment displays.

The **bin\_to\_7seg.vhd** file contains two functions used by the **Lab5.vhd** code within the **Time\_Display\_Process**.

The first function is **Bin\_to\_BCD**, which uses a double dabble algorithm to convert a 16-bit binary value to five 4-bit BCD values, although only four of these BCD values are used by the **Lab5.vhd** code. The other function, **BCD\_to\_7seg**, converts the BCD values to a 7-bit value that represents each digit for the seven segment displays.

As part of this lab exercise, in the **Lab5.vhd** file, you will need to finish the case statement in the **Timer\_State\_Machine** process, as well as the function calls in the **Time\_Display\_Process** used to display the time. Some hints are provided in the comments in the code.


---


## Task 2: Pin Assignments

### 1. Make the Following Pin Assignments

|    | To          | Location | DE2 Board Description    |
|----|-------------|----------|--------------------------|
| 1  | push_button | PIN_W26  | KEY3                     |
| 2  | reset       | PIN_N23  | KEY1                     |
| 3  | digit1[0]   | PIN_AF10 | Seven Segment Digit 0[0] |
| 4  | digit1[1]   | PIN_AB12 | Seven Segment Digit 0[1] |
| 5  | digit1[2]   | PIN_AC12 | Seven Segment Digit 0[2] |
| 6  | digit1[3]   | PIN_AD11 | Seven Segment Digit 0[3] |
| 7  | digit1[4]   | PIN_AE11 | Seven Segment Digit 0[4] |
| 8  | digit1[5]   | PIN_V14  | Seven Segment Digit 0[5] |
| 9  | digit1[6]   | PIN_V13  | Seven Segment Digit 0[6] |
| 10 | digit2[0]   | PIN_V20  | Seven Segment Digit 1[0] |
| 11 | digit2[1]   | PIN_V21  | Seven Segment Digit 1[1] |
| 12 | digit2[2]   | PIN_W21  | Seven Segment Digit 1[2] |
| 13 | digit2[3]   | PIN_Y22  | Seven Segment Digit 1[3] |
| 14 | digit2[4]   | PIN_AA24 | Seven Segment Digit 1[4] |
| 15 | digit2[5]   | PIN_AA23 | Seven Segment Digit 1[5] |
| 16 | digit2[6]   | PIN_AB24 | Seven Segment Digit 1[6] |
| 17 | digit3[0]   | PIN_AB23 | Seven Segment Digit 2[0] |
| 18 | digit3[1]   | PIN_V22  | Seven Segment Digit 2[1] |
| 19 | digit3[2]   | PIN_AC25 | Seven Segment Digit 2[2] |
| 20 | digit3[3]   | PIN_AC26 | Seven Segment Digit 2[3] |
| 21 | digit3[4]   | PIN_AB26 | Seven Segment Digit 2[4] |
| 22 | digit3[5]   | PIN_AB25 | Seven Segment Digit 2[5] |


|    |           |          |                          |
|----|-----------|----------|--------------------------|
| 23 | digit3[6] | PIN_Y24  | Seven Segment Digit 2[6] |
| 24 | digit4[0] | PIN_Y23  | Seven Segment Digit 3[0] |
| 25 | digit4[1] | PIN_AA25 | Seven Segment Digit 3[1] |
| 26 | digit4[2] | PIN_AA26 | Seven Segment Digit 3[2] |
| 27 | digit4[3] | PIN_Y26  | Seven Segment Digit 3[3] |
| 28 | digit4[4] | PIN_Y25  | Seven Segment Digit 3[4] |
| 29 | digit4[5] | PIN_U22  | Seven Segment Digit 3[5] |
| 30 | digit4[6] | PIN_W24  | Seven Segment Digit 3[6] |
| 31 | clk       | PIN_N2   | 50 MHz on board clock    |
| 32 | LEDG[0]   | PIN_AE22 | LED Green [0]            |
| 33 | LEDG[1]   | PIN_AF22 | LED Green [1]            |
| 34 | LEDG[2]   | PIN_W19  | LED Green [2]            |
| 35 | LEDG[3]   | PIN_V18  | LED Green [3]            |
| 36 | LEDG[4]   | PIN_U18  | LED Green [4]            |
| 37 | LEDG[5]   | PIN_U17  | LED Green [5]            |
| 38 | LEDG[6]   | PIN_AA20 | LED Green [6]            |
| 39 | LEDG[7]   | PIN_Y18  | LED Green [7]            |
| 40 | LEDR[0]   | PIN_AE23 | LED Red [0]              |
| 41 | LEDR[1]   | PIN_AF23 | LED Red [1]              |
| 42 | LEDR[2]   | PIN_AB21 | LED Red [2]              |
| 43 | LEDR[3]   | PIN_AC22 | LED Red [3]              |
| 44 | LEDR[4]   | PIN_AD22 | LED Red [4]              |
| 45 | LEDR[5]   | PIN_AD23 | LED Red [5]              |
| 46 | LEDR[6]   | PIN_AD21 | LED Red [6]              |
| 47 | LEDR[7]   | PIN_AC21 | LED Red [7]              |


2. Click **Save**  to save the pin assignments.

3. **Compile the Design** by clicking on the **Start Compilation** button 

---

### Task 3: Program the DE2 Development Board

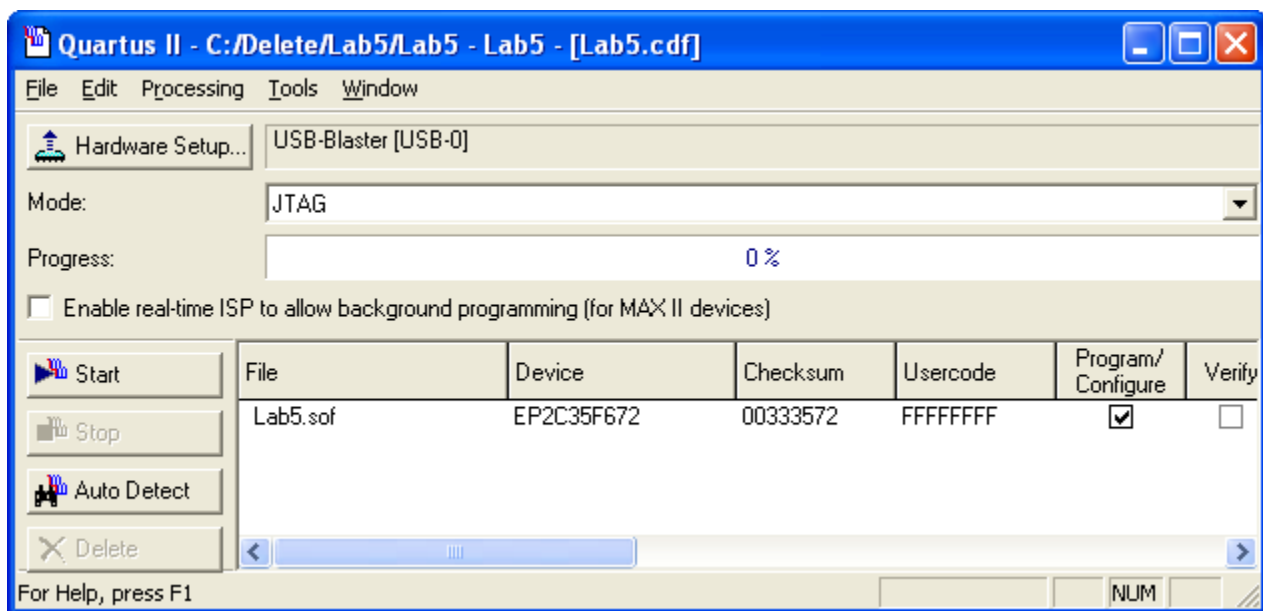1. Plug in and power on the DE2 board. Make sure that the **RUN/PROG Switch for JTAG/AS Modes** is in the **RUN** position.
2. In the Quartus II window click the **Programmer** button on the Toolbar to open the Programmer window   
The **Hardware Setup...** must be **USB-Blaster [USB-0]**. If not, click the **Hardware Setup...** button and select **USB-Blaster [USB-0]** from the drop-down menu for **Currently selected hardware**.  
**Mode** should be set to **JTAG**.  
Make sure that the **File** is **Lab5.sof**, **Device** is **EP2C35F672**, and the **Program/Configure** box is checked.



Then click the **Start** button to program the DE2 board.  
When the progress bar reaches 100%, programming is complete

#### Task 4: Play the Game

1. The game is started by pressing **KEY3** on the development board. This causes the hardware to change states from **idle** to **countdown**, turns on the first eight red LEDs, and begins the countdown to when the timer starts. The countdown is not displayed in order to maintain the element of surprise.
2. When the countdown completes the hardware changes to the **timer** state and begins incrementing the millisecond counter, the red LEDs are shut off, and the first eight green LEDs are turned on. The user must press **KEY3** on the development board as soon as possible after the green LEDs light in order to obtain the quickest reaction time.
3. When the user presses **KEY3** the state is changed to the **score** state where the millisecond display is frozen in order to display the user's reaction time.
4. Pressing the **reset** button (**KEY1**) at this point will return the hardware to the **idle** state where the game can be played again.

National Science Foundation – Advanced Technological Education  
VHDL and FPGA design workshop – (Pre - Course Evaluation)  
Summer 2011

Please take a few minutes to answer the following questions. Your responses will be used to improve this course for future students. Thank you, in advance, for your participation.

**Mastery of Main Course Objectives** (Circle One)

|                                                                                    | Complete<br>Mastery |   |   |   | No<br>Mastery |
|------------------------------------------------------------------------------------|---------------------|---|---|---|---------------|
| Ability to implement basic constructs of VHDL                                      | 5                   | 4 | 3 | 2 | 1             |
| Ability to implement modeling structures of VHDL                                   | 5                   | 4 | 3 | 2 | 1             |
| Ability to use software tools to check the code for correctness and correct errors | 5                   | 4 | 3 | 2 | 1             |

Additional content/topics you would have liked to have had covered \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

**Quality of Instruction** (Circle One)

|                                                                                   | Strongly<br>Agree | Agree | Neutral | Disagree | Strongly<br>Disagree |
|-----------------------------------------------------------------------------------|-------------------|-------|---------|----------|----------------------|
| The instruction was clearly presented                                             | 5                 | 4     | 3       | 2        | 1                    |
| Any questions I asked were properly answered                                      | 5                 | 4     | 3       | 2        | 1                    |
| The materials provided helped me to learn                                         | 5                 | 4     | 3       | 2        | 1                    |
| The pace of the course was appropriate for the amount of material to be learned   | 5                 | 4     | 3       | 2        | 1                    |
| All things taken into consideration, I considered the instruction to be excellent |                   |       |         |          |                      |

Additional comments regarding the teaching of this course or suggestions for improvement

\_\_\_\_\_  
\_\_\_\_\_

## Advanced VHDL Design Technique Learning Objectives (Circle One)

You learned to:

|                                                                              | Strongly Agree | Agree | Neutral | Disagree | Strongly Disagree |
|------------------------------------------------------------------------------|----------------|-------|---------|----------|-------------------|
| Write synthesizable VHDL                                                     | 5              | 4     | 3       | 2        | 1                 |
| Control state machine implementation                                         | 5              | 4     | 3       | 2        | 1                 |
| Optimize a design using operator balancing, resource sharing, and pipelining | 5              | 4     | 3       | 2        | 1                 |
| Create a test bench and run a simulation                                     | 5              | 4     | 3       | 2        | 1                 |

Additional comments regarding the teaching of this material

---

---

## Quartus II Software Design Series: Foundation Learning Objectives (Circle One)

You learned to:

|                                                   | Strongly Agree | Agree | Neutral | Disagree | Strongly Disagree |
|---------------------------------------------------|----------------|-------|---------|----------|-------------------|
| Create a new Quartus II project                   | 5              | 4     | 3       | 2        | 1                 |
| Create design components using MegaWizard manager | 5              | 4     | 3       | 2        | 1                 |
| Compile a design and view results                 | 5              | 4     | 3       | 2        | 1                 |
| Use settings and assignments to control results   | 5              | 4     | 3       | 2        | 1                 |
| Make pin assignments and evaluate                 | 5              | 4     | 3       | 2        | 1                 |
| Use the TimeQuest timing analyzer                 | 5              | 4     | 3       | 2        | 1                 |

Additional comments regarding the teaching of this material

---

---

National Science Foundation – Advanced Technological Education  
VHDL and FPGA design workshop – (Post - Course Evaluation)  
Summer 2011

Please take a few minutes to answer the following questions. Your responses will be used to improve this course for future students. Thank you, in advance, for your participation.

**Mastery of Main Course Objectives** (Circle One)

|                                                                                    | Complete<br>Mastery |   |   |   | No<br>Mastery |
|------------------------------------------------------------------------------------|---------------------|---|---|---|---------------|
| Ability to implement basic constructs of VHDL                                      | 5                   | 4 | 3 | 2 | 1             |
| Ability to implement modeling structures of VHDL                                   | 5                   | 4 | 3 | 2 | 1             |
| Ability to use software tools to check the code for correctness and correct errors | 5                   | 4 | 3 | 2 | 1             |

Additional content/topics you would have liked to have had covered \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

**Quality of Instruction** (Circle One)

|                                                                                   | Strongly<br>Agree | Agree | Neutral | Disagree | Strongly<br>Disagree |
|-----------------------------------------------------------------------------------|-------------------|-------|---------|----------|----------------------|
| The instruction was clearly presented                                             | 5                 | 4     | 3       | 2        | 1                    |
| Any questions I asked were properly answered                                      | 5                 | 4     | 3       | 2        | 1                    |
| The materials provided helped me to learn                                         | 5                 | 4     | 3       | 2        | 1                    |
| The pace of the course was appropriate for the amount of material to be learned   | 5                 | 4     | 3       | 2        | 1                    |
| All things taken into consideration, I considered the instruction to be excellent |                   |       |         |          |                      |

Additional comments regarding the teaching of this course or suggestions for improvement

\_\_\_\_\_  
\_\_\_\_\_

## Advanced VHDL Design Technique Learning Objectives (Circle One)

You learned to:

|                                                                              | Strongly Agree | Agree | Neutral | Disagree | Strongly Disagree |
|------------------------------------------------------------------------------|----------------|-------|---------|----------|-------------------|
| Write synthesizable VHDL                                                     | 5              | 4     | 3       | 2        | 1                 |
| Control state machine implementation                                         | 5              | 4     | 3       | 2        | 1                 |
| Optimize a design using operator balancing, resource sharing, and pipelining | 5              | 4     | 3       | 2        | 1                 |
| Create a test bench and run a simulation                                     | 5              | 4     | 3       | 2        | 1                 |

Additional comments regarding the teaching of this material

---

---

## Quartus II Software Design Series: Foundation Learning Objectives (Circle One)

You learned to:

|                                                   | Strongly Agree | Agree | Neutral | Disagree | Strongly Disagree |
|---------------------------------------------------|----------------|-------|---------|----------|-------------------|
| Create a new Quartus II project                   | 5              | 4     | 3       | 2        | 1                 |
| Create design components using MegaWizard manager | 5              | 4     | 3       | 2        | 1                 |
| Compile a design and view results                 | 5              | 4     | 3       | 2        | 1                 |
| Use settings and assignments to control results   | 5              | 4     | 3       | 2        | 1                 |
| Make pin assignments and evaluate                 | 5              | 4     | 3       | 2        | 1                 |
| Use the TimeQuest timing analyzer                 | 5              | 4     | 3       | 2        | 1                 |

Additional comments regarding the teaching of this material

---

---